

29/9/22

## UNIT-1:

### GENERAL AMPLIFIER CHARACTERISTICS

#### 1. CONCEPT OF AMPLIFIERS

- Concept of Amplifiers
  - Voltage gain
  - Current gain
  - Power gain
  - Input and output resistances
  - Conversion Efficiency
  - Frequency Response
  - Band width
  - Distortion
- BJT AMPLIFIERS**
- Small signal low frequency model of the transistor
  - Analysis of common Emitter, common Base, common collector amplifiers
  - Approximate model analysis
  - Effects of coupling and bypass capacitors on low frequency response
  - Hybrid-II model at high frequencies
  - Calculation of High frequency parameters in terms of low frequency parameters
  - CE short circuit gain
  - CE current gain with resistive load

## UNIT-2:

### FET AMPLIFIERS

- Small signal model
- Analysis of common source
- Common Drain and Common gate amplifiers.
- Comparison of performance of 3 configurations
- High frequency FET circuits
- Common source amplifier at high frequencies
- Common drain amplifier at high frequencies

## - MULTI STAGE AMPLIFIERS

### - Types of coupling

### - Choice of amplifier configuration

### - Overall voltage gain

### - Bandwidth of $n^{\text{th}}$ stage amplifier

### - Darlington Bootstrap circuits

## UNIT-3: FEED BACK AMPLIFIERS

### - Feed back concept

### - Classification

### - Affects of -ve feedback on gain

### - Stability, Noise

### - Distortion, Bandwidth

### - Input resistance & output resistance

### - OSCILLATORS: generators signal without input

### - Review of basic concept

### - Barkhausen criterion

### - RC oscillators (Phase shift, Wien Bridge etc)

### - LC oscillators (Hartley, Colpitt, Clapp)

### - CRYSTAC

## UNIT-4: POWER AMPLIFIERS

### - Series FET class-A power amplifiers

### - Transformer coupled class-A power amplifiers

### - Harmonic Distortion

### - Pushpull amplifiers

### - class-B amplifiers

### - class-AB operation

### - Complementary symmetry, pushpull class-B power amplifiers

### - cross over distortion

## UNIT-5:

- DIFFERENTIAL AMPLIFIER:
- Basic structure and principle of operation
- Calculation of differential gain
- Common mode gain
- CMRR
- Circuit to improve CMRR
- Transfer characteristics
- OPERATIONAL AMPLIFIER:
- Ideal Opamp characteristics
- Opamp internal circuit
- Examples of IC Opamps
- DC and AC characteristics
- Inverting & Non-inverting modes of operation
- Voltage Follower

## TEXT BOOKS:

- "Integrated circuits" by milliman & Halkias - McGrawhi
- "Electronic devices & circuits" by Motter shed - PHI
- "Micro electronics" by J.Milliman & A. Enabbel - MC Graw hill 2nd edition
- "Electronic devices & circuits" by salivahanan - TMH
- "Electronic devices & circuits" by David E bell - PHI
- "Linear integrated circuits" by Ray chowdary and snail Bala Jain - New oil International publishers

29/9/22

## UNIT - I

### \* Classification of Amplifiers: (A) based on broad)

- Based on the transistor configuration:

\* CB Amplifier (from balanced input to output)

\* CE Amplifier (from balanced input to output)

\* CC Amplifier (from balanced input to output)

- stage

- input

- coupling

- Based on mode of operation:

\* class - A Amplifier (constant current characteristics)

\* class - B Amplifier (stability, broad band active devices)

\* class - AB Amplifier

\* class - C Amplifier (from balanced input to output)

- Based on number of stages:

\* Single - stage Amplifier (from balanced input to output)

\* Multi - stage Amplifier (from balanced input to output)

- Based on active devices:

\* BJT Amplifiers (inductor, diode, collector, emitter)

\* FET Amplifiers (diode, gate, drain, source)

- Based on input:

\* small signal Amplifier (from balanced input to output)

\* Large signal Amplifier (from balanced input to output)

- Based on output:

\* voltage Amplifier (from balanced input to output)

\* Power Amplifier (from balanced input to output)

- Based on frequency capabilities:

\* Audio frequency Amplifier (from balanced input to output)

\* Radio frequency Amplifier (from balanced input to output)

\* Intermediate frequency Amplifier (from balanced input to output)

\* UHF and (from balanced input to output)

\* Microwave Frequency Amplifier (from balanced input to output)

- Based on manner of coupling:
  - \* RC coupled Amplifier
  - \* Transformer coupled Amplifier
  - \* Direct coupled Amplifier

- Based on bandwidth:

- \* Narrow band Amplifier

- \* wide band Amplifier

### \* CONCEPT OF AMPLIFIER:

- A circuit that increases the amplitude of the given input signal is an "amplifier". (without any change in frequency).

- The amplifier two port network having 2 input terminals for the

signal that is to be amplified and 2 output terminals for the connection of loads.

- One of the input and output terminals are made generally common which was shown in figure.

- The amplifier contains atleast one active device (BJT/FET) for their operation as an amplifier it requires a source of energy this make it provided by a battery (or) DC source.

NOTE: the process of raising strength of weak signal without any 'change' in its general shape & frequency is known as "Amplification".


QUESTION

ANSWER

QUESTION

ANSWER

## AMPLIFIER NOTATIONS:

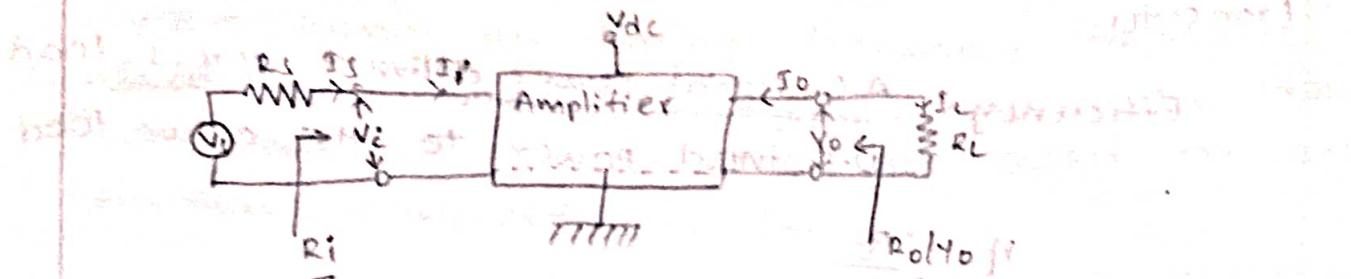

V<sub>s</sub> - Input source

R<sub>s</sub> - Internal resistance of source

I<sub>i</sub> - Input current to amplifier

V<sub>i</sub> - Actual input to amplifier

V<sub>o</sub> - Voltage across load resistance R<sub>L</sub>

I<sub>o</sub> - Output current

I<sub>L</sub> - Load current

$$[I_o = -I_L]$$

R<sub>L</sub> - Load resistance

R<sub>i</sub> - Input resistance of amplifier

R<sub>o</sub> - Output resistance of amplifier ( $R_o = \frac{V_o}{I_o}$ )

V<sub>dc</sub> - DC voltage (to be in active region)

- Current gain is defined as the ratio of output current to input current. (A<sub>i</sub>)

$$A_i = \frac{I_o}{I_i}$$

- Voltage gain is defined as the ratio of output voltage to input voltage. (A<sub>v</sub>)

$$A_v = \frac{V_o}{V_i}$$

- Ratio of output power to input power is power gain (A<sub>p</sub>)

$$A_p = \frac{P_o}{P_i} = \frac{V_o I_o}{V_i I_i} = A_v \cdot A_i$$

- Input resistance,  $R_i = \frac{V_i}{I_i}$

- Output resistance,  $R_o = \frac{V_o}{I_o}$  ( $V_s=0$ )

## CONVERSION EFFICIENCY:

A measure of the ability of an active device to convert the DC power of the supply into the AC power delivered to the load is called the conversion efficiency (or theoretical efficiency).

also called the collector circuit efficiency for a transistor.

Efficiency =  $\frac{\text{A.C signal power delivered across load}}{\text{D.C input power to the active load}}$

$$\eta = \frac{P_o}{P_{dc}}$$

$$\eta = \frac{V_o I_o}{V_{dc} I_{dc}}$$

$$\% \eta = \frac{P_o}{P_{dc}} \times 100$$

### DISTORTION:

The application of sinusoidal signal to the input of an amplifier will result in a sinusoidal output. Generally the output is not replica of the input because of various types of distortions may arise either from non-linearity characteristics of Active devices (BJT/FET) or from the influence of the associated circuit.

- The various types of distortions are:

\* Non-linear / Amplitude / Harmonic distortion

\* Intermodulation distortion

\* Frequency distortion

\* Phase shift distortion

#### Non-linear Distortion:

This type of distortion results from the production of new frequencies in the output, which are not present in the input signal. These new frequencies (or) harmonics are generated, when the transistor operates in the non-linear region of its characteristics. The component with frequency same as input signal is called as "fundamental frequency component".

The additional frequency components present in the output signal are having frequency components which are integer multiples of fundamental frequency components. These components are called Harmonics/Harmonic components.

INTER MODULATION DISTORTION: For a system analysis, we prefer sinusoidal as it has only one frequency component.

It occurs when input signal consists more than one frequency component. (speech, music etc.). It is also a type of non-linear distortion, which generates frequency components not harmonically related to the signal frequencies i.e., if an input signal contains two frequencies  $f_1$  &  $f_2$  the output signal will contain their harmonics  $2f_1, 3f_1, \dots$  and  $2f_2, 3f_2, \dots$ . In addition there would be components  $f_1 + f_2$  &  $f_1 - f_2$  and also the sum & difference of the harmonics. These sum & difference frequencies are called "Intermodulation frequencies". The distortion due to these frequencies is called "Intermodulation distortion".

FREQUENCY DISTORTION:

It occurs even when the device is working in linear region. It is basically due to change in amplifier gain with frequency. i.e., the different input signal frequencies are amplified by different frequencies. But an amplifier should provide same amplification for all frequencies. Generally at lower & higher frequencies there is a loss & gain, which is usually due to the capacitive components associated with the circuit (or) active device itself.

In the case of audio signals the frequency distortion leads to a change in the quality of signal.

PHASE SHIFT DISTORTION: This distortion results from unequal phase shift of signals of different frequencies. The unequal phase shift is due to frequency dependent components, C, I etc., associated with the circuit and the active device of the amplifier.

## FREQUENCY RESPONSE:

$$\text{Ans: } \frac{\frac{V_o}{V_i}}{= A_{VE}} = \frac{R_1}{R_1 - jX_C}$$

$$\text{right-hand side} \Rightarrow \frac{1}{(1-\beta x C)}$$

$$A_V = \frac{1}{1 - \frac{j}{2\pi f C(R)}}$$

$$(AVI) = \frac{1}{\text{Anzahl Städte}}$$

$$(AVI) = \frac{1}{\sqrt{(1+|f|)^2}}$$

$\Delta t = \frac{\sqrt{1 + (fL)^2}}{f}$  and  $f = \frac{1}{\Delta t}$

at  $f_L = t$ ,  $|AV| = \frac{1}{\infty} = 0.707$  (so minimum tone)

$$f_L = \pm 1, \quad (\text{AV}) = \frac{1}{\sqrt{2}} = 0.707$$

2) CPF: no nro 2 2010 → é o documento que identifica o cidadão

$$V_o = V_i + -jX_C \underline{z} \text{ is written as } V_o = V_i + \underline{z} \text{ with } z = -jX_C$$

$$p_{\text{air}, \text{bottom}} = 0.0 \frac{\overline{R_2} \times C_2}{\text{liters}} \text{ liters} \rightarrow \text{mass} \text{ v_i } \text{ molar}$$

$$\frac{V_o + jI_2 \cdot R_2 - jX_{C2}}{V_i} = -\frac{1}{R_2 - jX_{C2}} = \frac{-1}{\frac{R_2}{jX_{C2}} - 1} = \frac{-1}{\frac{j2\pi f C_2}{R_2} - 1} = \frac{1}{1 - \frac{R_2}{j2\pi f C_2}} = \frac{1}{1 + \frac{jR_2}{2\pi f C_2}} = \frac{1}{1 + j\omega_0}$$

$$AV = \frac{1}{1 + jR_2} \cdot \frac{1}{2\pi f C_2}$$

$$BW = f_H - f_L$$

$$1 \text{ bel} = 10 \text{ dB}$$

$$|AV| = \sqrt{1 + \left(\frac{f}{f_m}\right)^2}$$

### Gain in dB:

The gain of an amplifier can be expressed as a number, but it is of great practical importance to assign it a unit. The assigned unit is "bel or dB".

-  $1 \text{ bel} = 10 \text{ dB}$

- The common logarithm of power gain is known as "bell power gain".

- Power gain =  $\log_{10} \frac{P_o}{P_i}$  bel

- Power gain =  $10 \log_{10} \frac{P_o}{P_i}$  dB

- As power is directly proportional to  $V^2 \& i^2 \Rightarrow P \propto V^2; P \propto i^2$   
Therefore, voltage gain & current gain are expressed in dB.

- Voltage gain =  $20 \log_{10} \frac{V_o}{V_i}$  dB

- Current gain =  $20 \log_{10} \frac{I_o}{I_i}$  dB

- The unit dB is a logarithmic unit. Our ear response is also logarithmic i.e., loudness of sound ~~near~~ by ear is not according to the intensity of sound, but according to the log of intensity of sound.

- In multi-stage amplifiers it permits to add individual gains of stages to calculate overall gain (logarithm changes multiplication to addition).

- It allows us to denote both very small as well as very large quantities of linear scale by considerably small figures.

Ex: 0.000001 and 100000  
 $= -140 \text{ dB}$  and  $100 \text{ dB}$ .

Band width: The range of frequencies over which the voltage gain is equal to (or) greater than 70.7% of the maximum gain is known as "Band width".

The human ear is not a very sensitive hearing device, it has been found that if the gain falls to 70.7% of maximum gain, the ear cannot detect the change. However, if the gain falls below 70.7% of the maximum gain the ear will hear clear distortion.

\* C.B:

$$\text{let, } R_i = 20\Omega$$

$$V_i = 200 \text{ mV}$$

$$R_L = 5 \text{ k}\Omega$$

$$\therefore I_C = \alpha I_E + I_{CB0}$$


$$I_E = \frac{200 \times 10^{-3}}{20} = 10 \text{ mA}$$

$$I_C = \alpha I_E = I_E$$

$$\therefore I_C = 10 \text{ mA}$$

$$\therefore V_o = I_C \times R_L \\ = 10 \times 5 \times 10^3 \times 10^{-3}$$

$$V_o = 50 \text{ V}$$

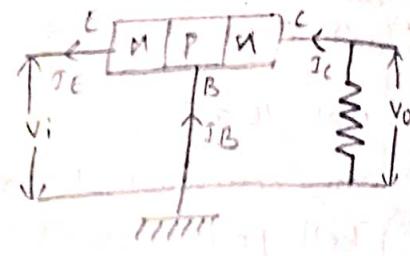

$$A_V = \frac{V_o}{V_i} = \frac{50 \times 10^3}{200} = 250 \quad \text{used for } A_V$$

$$A_I = \frac{I_o}{I_i} = \frac{10 \times 10^{-3}}{10 \times 10^{-3}} = \alpha = 1$$

[A<sub>i</sub><1]

\* C.E.:

$$I_E = I_C + I_B$$

$$I_C = \alpha I_E + I_{CB0}$$


$$I_C = \alpha(I_C + I_B) + I_{CB0}$$

$$\therefore I_C(1-\alpha) = \alpha I_B + I_{CB0}$$

$$I_C = \frac{\alpha}{1-\alpha} I_B + \frac{1}{1-\alpha} I_{CB0}$$

$$I_C = B I_B + (B+1) I_{CB0}$$

$$I_C = B I_B + I_{CEO}$$

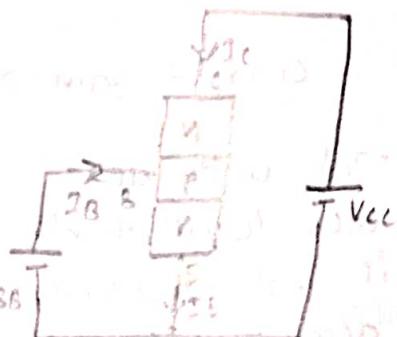

$$I_C = B I_B$$

$$\therefore B = \frac{\alpha}{1-\alpha}$$

$$\therefore \alpha = 0.95$$

$$B = \frac{0.95}{0.05} = 19$$

$$\therefore \alpha = 0.98$$

$$B = \frac{0.98}{0.02} = 49$$

Let  $I_B = 1\text{mA}$  &  $B = 100$

$$\therefore I_C = B I_B = 100 \text{mA} \parallel$$

- The voltage gain of CC amplifier is approximately equal to unity, i.e.,  $A_V = 1$  &  $A_i = B$

$$A = B + 1 = \frac{1}{1 - \alpha}$$

### SMALL SIGNAL ANALYSIS OF BJT:

- In the AC analysis, we will come across small and large signal analysis.

- Large signal amplifiers are called "power amplifiers".

- Small signal is the signal having magnitude sufficiently small to keep the transistor in active region.

- For AC response,

- i) AC equivalent circuit



- ii) Replace transistor with equivalent model / equivalent circuit

- For AC equivalent circuit,

Step-1:- Short circuit all the DC sources.

Step-2:- Short all the capacitors

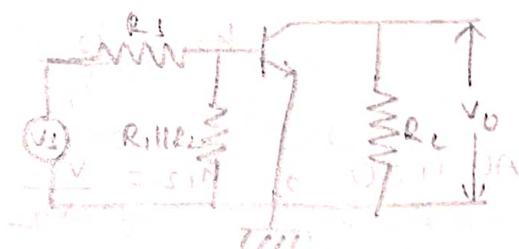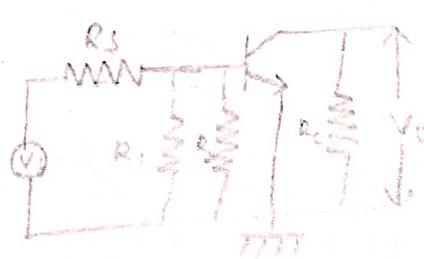Step-3:- Redraw the network removing all the elements which are short circuited in step-1 & step-2.



### EQUIVALENT MODEL:

An equivalent model is a combination of circuit elements ( $R, L, C$ ) properly chosen to best represent the actual behaviour of device under specific operating point.

Hybrid Model

Transistor


$\pi$  Model

Hybrid  $\pi$  Model
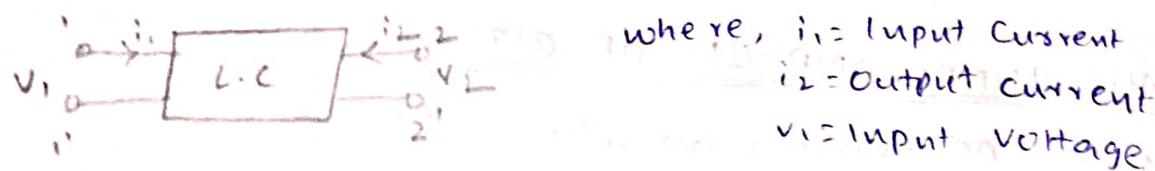
## HYBRID PARAMETERS:

Every linear circuit having input & output terminals can be analysed by four parameters (1 in ohm, 1 in  $\Omega^{-1}$ , 2 are dimension less) called "Hybrid / h-parameters."

NOTE: Hybrid means mixed. Since these parameters have mixed dimensions, they are called 'hybrid parameters.'



-The terminal behaviour of any two port network can be specified by the two-port voltages, terminal currents  $v_1, v_2$  &  $i_1, i_2$  respectively as shown in figure.

-Out of these '4' variables, two can be selected as independent variables and remaining '2' can be expressed in terms of these 2 variables.

-If the current  $i_1$ , voltage  $v_2$  as independent, then we can write,  $i_2$  as function of  $(i_1, v_2)$  and  $v_1$  as function of  $(i_1, v_2)$

$$v_1 = h_{11} i_1 + h_{12} v_2$$

$$i_2 = h_{21} i_1 + h_{22} v_2$$

-The four hybrid parameters  $h_{11}, h_{12}, h_{21}, h_{22}$  are defined as follows:

$$\text{At } v_2 = 0, \quad h_{11} = \frac{v_1}{i_1} \quad \text{[Input resistance]}$$

$$h_{21} = \frac{i_2}{i_1} \quad \text{[Forward current gain]}$$

$$\text{At } i_1 = 0 \quad h_{12} = \frac{v_1}{v_2} \quad \text{[Forward voltage gain/transfer]}$$

$$h_{22} = \frac{i_2}{v_2} \quad \text{[Output admittance]}$$

-Dimensions of h-parameters are as follows:

$$h_{11}: \Omega \quad \text{[Dimension of resistance]}$$

$$h_{22}: \Omega^{-1} \quad \text{[Dimension of conductance]}$$

$h_{12}, h_{21}$ : dimension less.

The alternative subscript notations recommended by IEEE is:

$11 = i = \text{Input}$

$22 = o = \text{Output}$

$21 = f = \text{Forward Transfer}$

$12 = r = \text{Reverse Transfer}$

$$V_1 = h_{11}i_1 + h_{12}V_2 \quad (1)$$


$$V_2 = h_{21}i_1 + h_{22}V_2$$

(1) & (2) can be rewritten as using notations recommended by IEEE are:

$$V_1 = h_i i_1 + h_o V_2$$

$$V_2 = h_f i_1 + h_v V_2$$

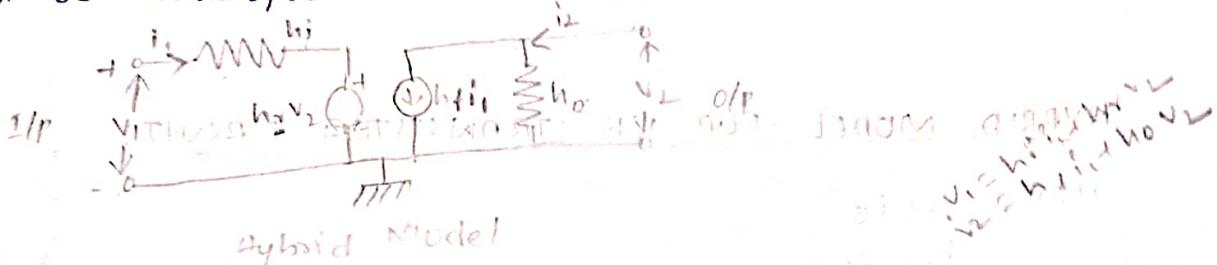- By using h-parameters, the mathematical model for 2 port network known as "Hybrid model or h-parameter mode" can be developed which is shown in figure.



### NOTATIONS USED IN TRANSISTOR CIRCUITS:

S.NO	h-parameter	Notation in CB	Notation in CE	Notation in CC
1.	$h_{11}$	$h_{ib}$	$h_{ie}$	$h_{ic}$
2.	$h_{12}$	$h_{rb}$	$h_{re}$	$h_{rc}$
3.	$h_{21}$	$h_{tb}$	$h_{te}$	$h_{fc}$
4.	$h_{22}$	$h_{ob}$	$h_{oe}$	$h_{oc}$

The use of h-parameters to analyse a transistor have the following advantages:

i, h-parameters are real numbers upto radio frequencies.

ii, They are easy to measure

iii, They can be determined from the transistor static characteristic curves.

iv, They are convenient to use in circuit analysis and design.

v, Easily convertible from one configuration to other.

vi, Readily supplied by manufacturers.

### HYBRID MODEL FOR CE TRANSISTOR CIRCUIT:

Here,  $i_1 = i_b$


$i_2 = i_c$

$v_1 = v_b$

$v_2 = v_c$

$$\therefore v_b = h_{ib} i_b + h_{re} v_c$$

$$i_c = h_{fe} i_b + h_{oe} v_c$$

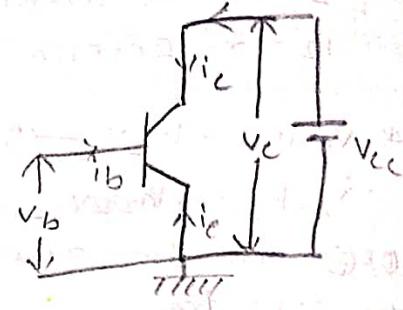

### HYBRID MODEL FOR CB TRANSISTOR CIRCUIT:

Here,  $i_1 = i_e$


$i_2 = i_c$

$v_1 = v_e$

$v_2 = v_L$

$$\therefore v_e = h_{ib} i_e + h_{re} v_L$$
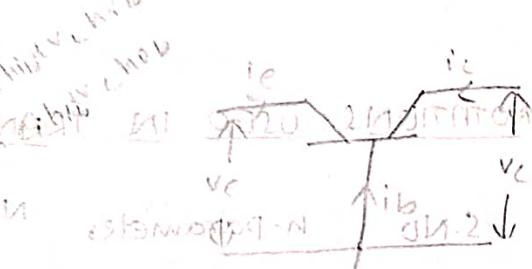
$$\therefore i_c = h_{fe} i_e + h_{oe} v_L$$



### HYBRID MODEL FOR CC TRANSISTOR CIRCUIT:

Here,  $i_1 = i_b$


$i_2 = i_e$


$v_1 = v_b$

$v_2 = v_e$

$$\therefore v_b = h_{ic} i_b + h_{re} v_e$$
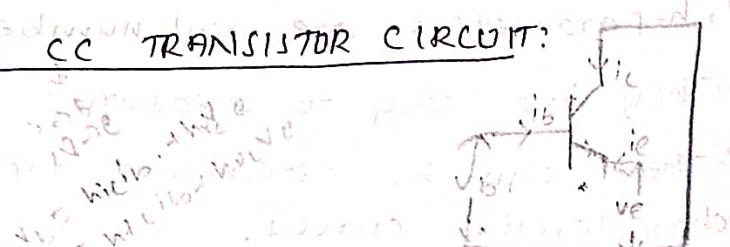
$$\therefore i_e = h_{fe} i_b + h_{oe} v_e$$




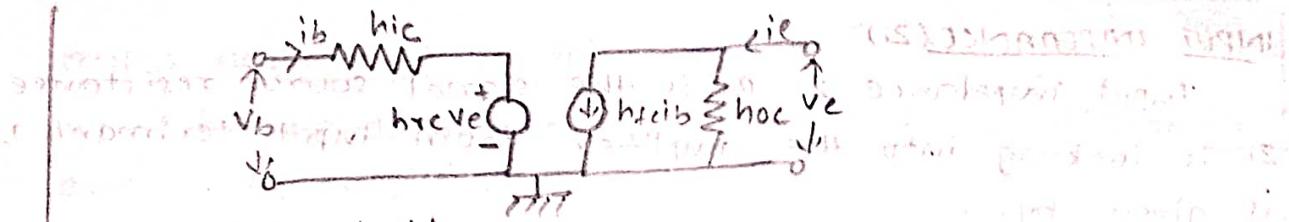


Exact analysis
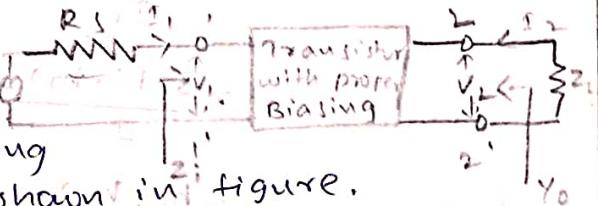
### ANALYSIS OF A TRANSISTOR AMPLIFIER USING h-PARAMETERS

A Transistor amplifier can be constructed by connecting an external load & signal source along with proper biasing, which was shown in figure.



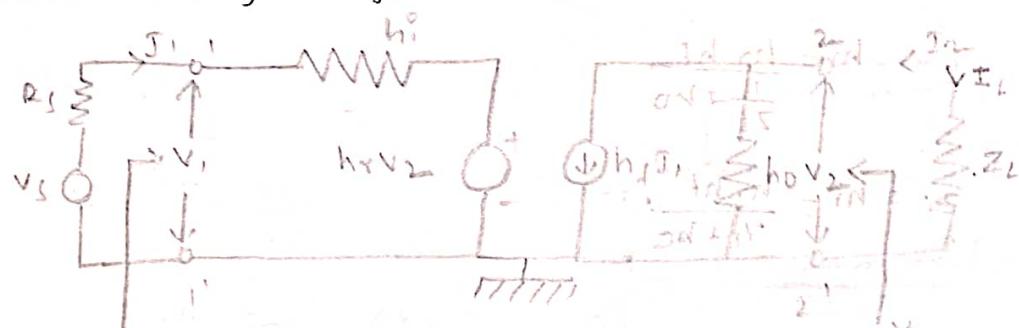- Replace the transistor in any one of it's configuration. The hybrid equivalent circuit is valid for any type of load, whether it is impedance (resistance). Another transistor. It is assumed that h-parameters remain constant over the operating range and the input is sinusoidal.



### (A) CURRENT MULITIPLYING OPERATION

\* Current gain factor:-

$$A_I = \frac{I_L}{I_1} = -\frac{I_2}{I_1}$$

1, 1'  $\rightarrow$  2, 2' terminals  
3, 3'  $\rightarrow$  4, 4' terminals  
5, 5'  $\rightarrow$  6, 6' terminals


$$I_2 = h_f I_1 + h_{ov2}$$

$$I_2 = h_f I_1 - h_{ov2} Z_L$$

$$I_2(1 + h_{ov2} Z_L) = h_f I_1$$

$$\frac{I_2}{I_1} = \frac{h_f}{1 + h_{ov2} Z_L}$$
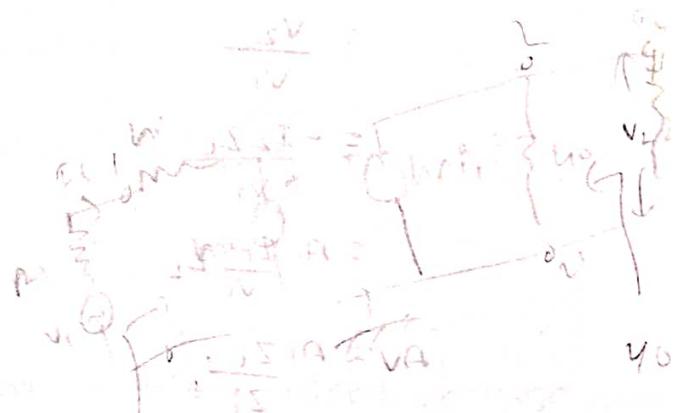
$$\therefore A_I = -\frac{h_f}{1 + h_{ov2} Z_L}$$



46

### INPUT IMPEDANCE ( $Z_i$ ):

Input impedance  $Z_i$ .  $R_s$  is the signal source resistance.  $Z_i$  is looking into the amplifier from input terminals.  $Z_i$  is given by,

$$Z_i = \frac{V_1}{I_1}$$

$$V_1 = I_1 \cdot h_{ie} \cdot V_2$$

$$= I_1 \cdot h_{ie} \cdot V_2$$

$$V_2 = -I_2 Z_L$$

$$= h_{ie} \cdot \frac{V_2}{I_1}$$

$$A_i = \frac{I_2}{I_1} = \frac{Z_L}{Z_L + h_{ie}} = A_{v1}$$

$$= h_{ie} \cdot \frac{-I_2 Z_L}{I_1}$$

or  $Z_i = h_{ie} \cdot \frac{-I_2 Z_L}{I_1}$  at low frequencies self-explains

for higher frequencies  $I_1$  is constant &  $I_2$  is proportional to  $V_2$  so  $Z_i$  is constant

Amplification factor  $= h_{ie} \cdot A_{v1} \cdot Z_L$  depends on the load connected

so  $Z_i = h_{ie} \cdot A_{v1} \cdot \left[ \frac{-h_{re} h_f}{1 + h_{re} Z_L} \right] Z_L$

$$= h_{ie} - \frac{h_{re} h_f}{\frac{1}{Z_L} + h_{re}}$$

$$Z_i = h_{ie} - \frac{h_{re} h_f}{Y_L + h_{re}}$$

### VOLTAGE GAIN / VOLTAGE AMPLIFICATION FACTOR: (AV)

$$A_v = \frac{\text{Op voltage}}{\text{Ip voltage}}$$

$$= \frac{V_2}{V_1}$$

$$= -\frac{I_2 Z_L}{V_1}$$

$$= A_i \frac{I_1}{V_1} Z_L$$


$$A_v = A_i \frac{Z_L}{Z_i}$$

### OUTPUT ADMITTANCE: ( $z_0/y_0$ )

By the definition,  $y_0$  is obtained by setting  $v_s$  to 0 and  $z_L$  to infinity.

$$\begin{aligned} y_0 &= \frac{I_2}{V_2} \\ &= h_f I_1 + h_o V_2 \\ &= \frac{h_f I_1 + h_o}{V_2} \end{aligned}$$
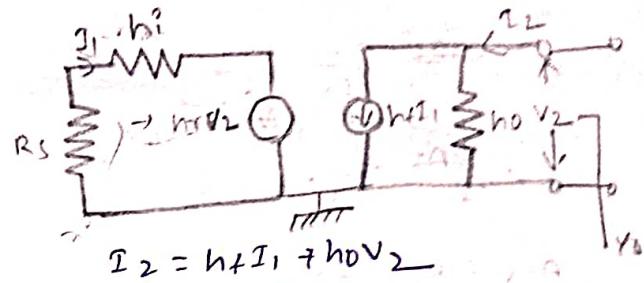
$$y_0 = h_o - h_f h_i \frac{1}{R_s + h_i}$$



$$I_2 = h_f I_1 + h_o V_2$$

$$i_C V_L \Rightarrow R_s I_1 + h_i I_1 + h_o V_2 = 0$$


$$\Rightarrow I_1 = -\frac{h_o V_2}{R_s + h_i}$$

$$z_0 = \frac{1}{y_0}$$
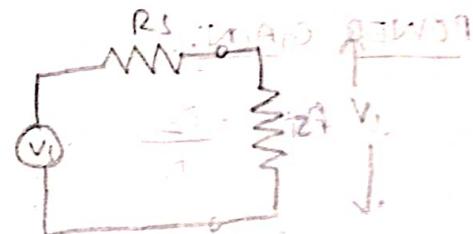
### VOLTAGE GAIN INCLUDING SOURCE (OVERALL VOLTAGE GAIN):

$$\begin{aligned} A_{VS} &= \frac{V_2}{V_s} \\ &= \frac{V_2}{V_s} \cdot \frac{V_1}{V_1} \\ &= A_V \cdot \frac{V_1}{V_s} = A_V \left( \frac{V_1 \cdot Z_i}{Z_i + R_s} \right) \end{aligned}$$

$$A_{VS} = A_V \cdot \frac{Z_i}{R_s + Z_i}$$



$$V_1 = V_s \cdot \frac{Z_i}{R_s + Z_i}$$

$$A_V = A_I \frac{Z_L}{Z_i}$$

$$= A_I \frac{Z_L}{Z_i} - \frac{Z_i}{R_s + Z_i}$$

$$A_{VS} = A_I \frac{Z_L}{R_s + Z_i}$$

- If  $R_s = 0$ , then  $A_{VS} = A_I \cdot \frac{Z_L}{Z_i}$

$$A_{VS} = A_V$$

Then,  $A_V$  is the voltage gain with an ideal voltage source

## OVERALL CURRENT GAIN:

$$A_{IS} = \frac{Z_L}{I_S}$$

$$= \frac{Z_L}{Z_i} \cdot \frac{I_1}{I_S}$$

$$= A_I \cdot \frac{I_1}{I_S}$$

$$A_{IS} = A_I \cdot \frac{R_S}{R_S + Z_i}$$

$$A_{VS} = A_I \cdot \frac{Z_L}{R_S + Z_i}$$

$$\therefore \frac{A_{VS}}{A_{IS}} = \frac{Z_L}{R_S}$$

## POWER GAIN:

$$A_P = + \frac{P_2}{P_1}$$

$$= - \frac{V_2 I_2}{V_1 I_1}$$

$$A_P = A_V A_I$$

$$= A_I \cdot \frac{Z_L}{Z_i} \cdot A_I$$


$$A_P = A_I^2 \cdot \frac{Z_L}{Z_i}$$

## SMALL SIGNAL ANALYSIS OF A TRANSISTOR AMPLIFIER:

$$* A_I = \frac{-h_f}{1+h_{o2}Z_L}$$

$$* A_V = A_I \cdot \frac{Z_L}{Z_i} \quad \text{for small signal operation, } Z_i \ll R_S \text{ and } Z_L \gg R_D$$
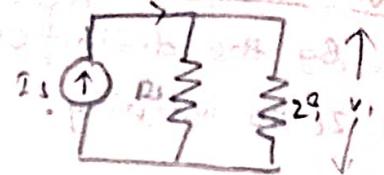
$$* Z_i = h_{iht}, A_I Z_L = h_{i-} - \frac{h_f h_r}{h_{o2} + h_{i-}}, \quad Z_i = \frac{h_{i-} h_{o2} h_r}{h_{o2} + h_{i-}}$$



$$I_1 = I_S \cdot \frac{R_S}{R_S + Z_i}$$

$$A_V = \frac{V_o}{V_i} = \frac{Z_L}{R_S + Z_i}$$

$$A_P = A_V \cdot A_I$$

$$= \frac{V_o}{V_i} \cdot \frac{V_o}{V_i} = \frac{V_o^2}{V_i^2}$$

$$= \frac{V_o^2}{V_i^2} = \frac{P_o}{P_i}$$

$$= \frac{P_o}{P_i} = \frac{V_o^2}{V_i^2}$$

$$= \frac{V_o^2}{V_i^2} = \frac{P_o}{P_i}$$

$$* A_{Vi} = A_I \cdot \frac{Z_i}{R_s + Z_i} = A_I \frac{Z_L}{R_s + Z_i} = A_{Is} - \frac{Z_L}{R_s}$$

$$* A_{Is} = A_I \cdot \frac{R_s}{R_s + Z_i} = A_{Vi} \cdot \frac{R_s}{Z_L}$$

$$* A_P = A_V A_{Is} = A_I^2 \cdot \frac{Z_L}{Z_i}$$

-The above formulas are valid for all the 3 configurations

### Conversion Formulas For Hybrid Parameters:

CC	CB
$h_{ic} = h_{ie}$	$h_{ib} = \frac{h_{ie}}{1+h_{re}}$
$h_{rc} = 1$	$h_{rb} = \frac{h_{ie} h_{re}}{1+h_{re}} - h_{re}$
$h_{fc} = -(1+h_{re})$	$h_{fb} = -\frac{h_{re}}{1+h_{re}}$
$h_{oc} = h_{oe}$	$h_{ob} = \frac{h_{oe}}{1+h_{re}}$

### Typical h-parameter values for a Transistor:

Parameter	CE	CC	CB
$h_{ie}$	$1100\Omega$	$1100\Omega$	$22\Omega$
$h_{re}$	$2.5 \times 10^4$	$1$	$3 \times 10^4$
$h_{re}$	50	-51	-0.98
$h_{oe}$	$24\mu A/V$	$25\mu A/V$	$0.49\mu A/V$
$\frac{1}{h_{ob}}$	$40k$	$40k$	$2.04M$

### COMPARISON OF TRANSISTOR AMPLIFIER CONFIGURATION

The values of  $A_I$ ,  $A_V$ ,  $R_i$ ,  $R_o$  and  $A_P$  are calculated for typical transistor using h-parameters which the values of  $R_L$  &  $R_S$  are  $3k\Omega$ .

PARAMETER	CB	CC	CE
$A_I$	0.98	47.5	-46.5
$A_V$	131	0.989	-131
$R_i$	$22.6\Omega$	$144k\Omega$	$1065\Omega$
$R_o$	$1.72M\Omega$	$80.5\Omega$	$45.5k\Omega$
$A_P$	128.38	46.98	6091.5

FOR CC, phase  
is  $180^\circ$  then  
 $A_I$  is -ve.

FOR oscillatory  
phase shift:  
generating sig

### \* Characteristics of CB Amplifier: (Invertig notes)

- Current gain is less than unity and its magnitude decreases with the increase of 'load resistance'  $R_o$ .
- Voltage gain  $A_V$  is high for normal values of  $R_i$ .
- The input resistance  $R_i$  is the lowest of all the 3 configurations.
- The output resistance  $R_o$  is the highest of all the 3 configurations.

### Applications:

- This is not commonly used for amplification purpose, but is used for buffer performance & load.
- i, Matching a very low impedance source
- ii, As a non-inverting amplifier with voltage gain exceeding unity.
- iii, For driving a high impedance load.
- iv, As a constant current source.

### \* Characteristics of CC Amplifier:

- For low values of  $R_i$ , the current gain  $A_I$  is high and almost equal to that of a CE amplifier.
- The voltage gain is less than unity.
- The input resistance is the highest of all the 3 configurations.
- The output resistance is the lowest of all the 3 configurations.

### Applications:

1. The CC amplifier is widely used as a buffer stage b/w a high impedance source and a low impedance load.
2. CC amplifier is called "the emitter follower".

### \* Characteristics of CE Amplifier:


1. The current gain,  $A_I$  is high for low values of  $R_L$  ( $10 \text{ k}\Omega$ )
2. The voltage gain is high for normal values of  $R_L$ .
3. The input resistance  $R_I$  is medium.
4. The output resistance  $R_O$  is moderately high.

### Applications:

1. CE amplifier provides both voltage gain and current gain
2. The input resistance  $R_I$  & Output resistance  $R_O$  are moderately high. Hence, CE amplifier is widely used for amplification purpose.
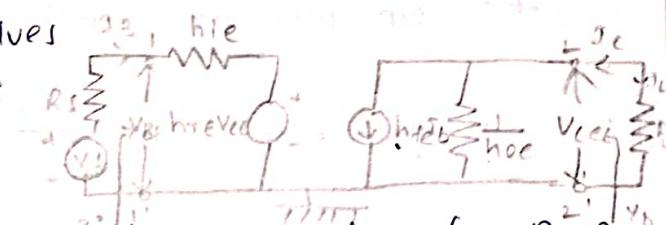
### APPROXIMATE MODEL ANALYSIS / SIMPLIFIED HYBRID MODEL:

As the h-parameters themselves vary widely for the same type of transistor.



i. It is better to make approximations and simplify for the expression for  $A_I$ ,  $A_V$ ,  $R_I$ ,  $R_O$  &  $A_P$ .

- In the above hybrid model  $\frac{1}{h_{OE}}$  is parallel with  $R_I$ , the parallel combination of two unequal impedances i.e.,  $\frac{1}{h_{OE}} + R_L$  is approximately equal to the lower value i.e.  $R_L$ .

- If  $\frac{1}{h_{OE}} \gg R_L \Rightarrow h_{OE} R_L \ll 1$ , the term  $h_{OE}$  may be neglected. If  $h_{OE}$  is omitted the collector current "i\_C = h\_{FE} . I\_B"

- Under this condition the magnitude of voltage generator is,  $h_{RE} V_{CE} = h_{RE} . i_C R_L$

$$= h_{RE} . h_{FE} I_B R_L$$


- Since  $h_{RE} . h_{FE} = 0.01$ , this voltage may be neglected in comparison with voltage drop across  $h_{RE}$  i.e.,  $h_{RE} . I_B$

provided that  $h_{re}R_L \leq 0.1$ , using approximate model we can show that the error deviation is  $< 10\%$ .

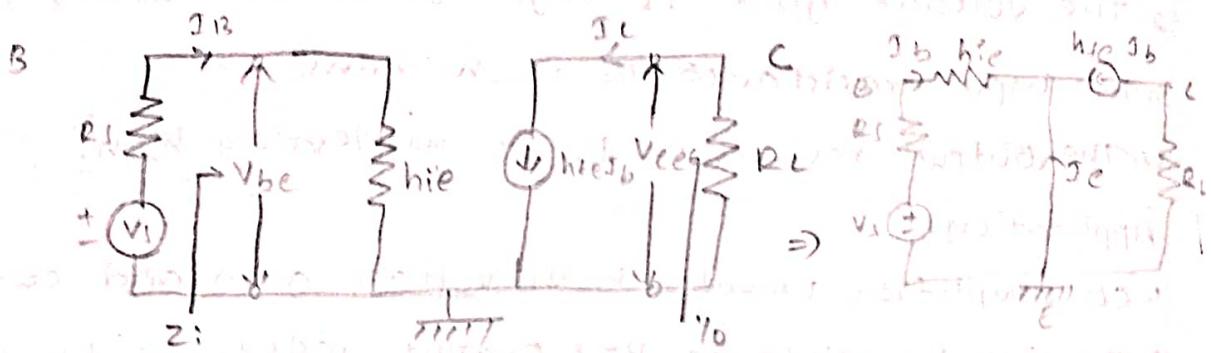
### NOTE:

- If  $h_{re}R_L \leq 0.1$ , using approximate model we can show that the error deviation is  $< 10\%$ .

- If the load resistance  $R_L$  is small, it is possible to neglect the parameters  $h_{re}$  &  $h_{oe}$  then the approximate equivalent circuit is



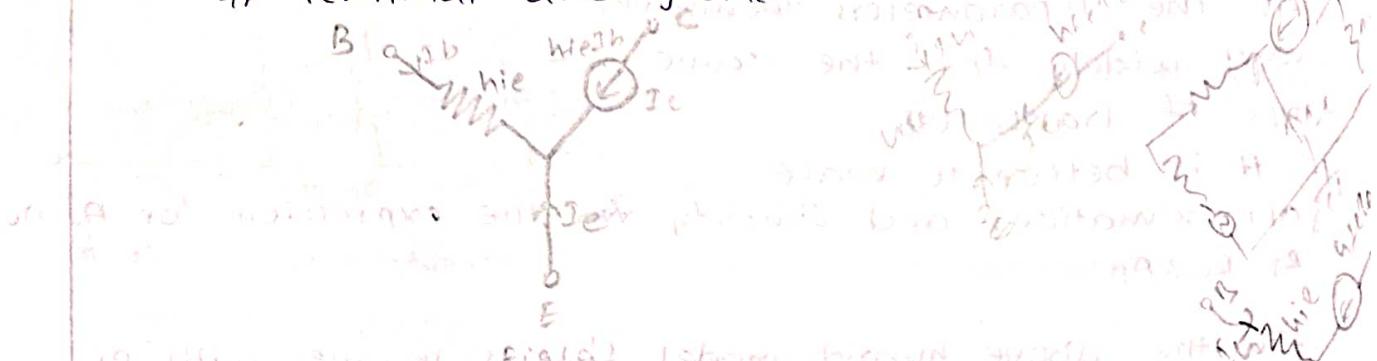- The simplified "hybrid" circuit that can be used for any configuration by simply grounding the appropriate terminal which is shown in fig(a). The signal is connected to the i/p terminal & ground and the load is placed to the o/p terminal and ground.



- The approximate hybrid model used for all the 3 configurations is shown in fig(a).


$$\rightarrow A_I = -\frac{h_{re}}{1 + h_{re}R_L}$$

$$A_I = -h_{re}$$

$$(h_{re}R_L \leq 0.1)$$

$$\rightarrow A_I = \frac{I_C}{I_B} = -\frac{I_C}{I_B}$$

$$= -h_{re} \frac{I_B}{I_B}$$

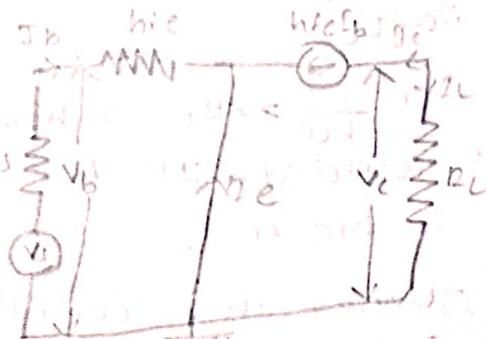

simplified hybrid model

$$A_I = -h_{re}$$

\*  $R_i = h_{ie} + h_{re} A_2 R_L$  (Drop across  $R_i$ )

$$= h_{ie} \left[ 1 + \frac{h_{re}}{h_{ie}} \cdot A_2 R_L \right]$$

$$= h_{ie} \left[ 1 + h_{re} \cdot h_{ie} \cdot \frac{A_2 R_L \cdot h_{oe}}{h_{ie}} \right] \quad [R_L \cdot h_{oe} \approx 0.1]$$

$$\approx 0.5 \quad \text{why?}$$

$$(A_2 = -h_{ie})$$

$$= h_{ie} (1 - 0.5)$$

$\boxed{R_i = h_{ie}}$

(Or)

$$R_i = \frac{V_b}{I_b} = \frac{h_{ie} I_b}{I_b}$$

$\boxed{R_i = h_{ie}}$

\*  $A_V = A_2 \cdot \frac{R_L}{R_i}$

$\boxed{A_V = -\frac{h_{ie}}{h_{re}} \cdot R_L}$

\*  $\gamma_{R_o} = \gamma_o = h_{oe} - \frac{h_{re} h_{ie}}{R_s + h_{ie}}$

$$= 0 - 0 \quad (\text{neglecting } h_{oe} \text{ and } h_{ie})$$

$$\gamma_o = 0$$

$\boxed{R_o = \infty}$

$\boxed{R_o = \frac{V_c}{I_c} = \frac{V_c}{0} = \infty \quad (\because V_c = 0)}$

$\Rightarrow R_o = R_s + h_{ie} + \infty$

$\boxed{R_o = \infty}$

\* Voltage gain along with source,

$$A_{VS} = A_V \frac{R_i}{R_i + R_s}$$

$\boxed{A_{VS} = A_V \cdot \frac{h_{ie}}{h_{ie} + R_s}}$

$\boxed{A_{IS} = A_2 \frac{R_s}{R_s + R_i}}$



## APPROXIMATE HYBRID MODEL FOR COMMON BASE:

① Current gain,

$$A_I = \frac{I_L}{I_e} = -\frac{I_c}{I_e}$$




$$= -\frac{h_{fe} I_b}{I_e}$$

$$\rightarrow I_e = -(I_c + I_b)$$

$$I_e = -I_b(1+h_{fe})$$

$$\therefore A_I = \frac{-h_{fe} I_b}{-I_b(1+h_{fe})}$$

$$A_I = \frac{h_{fe}}{1+h_{fe}}$$

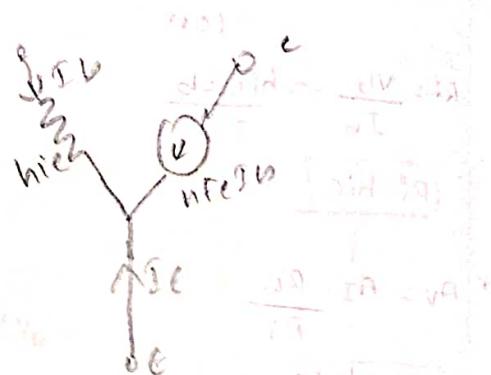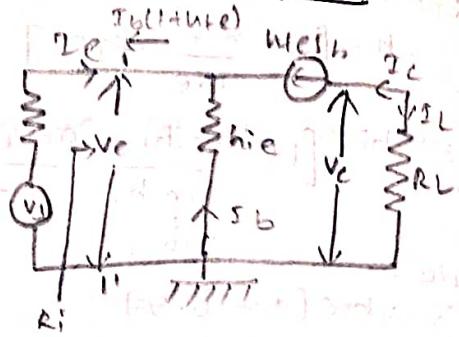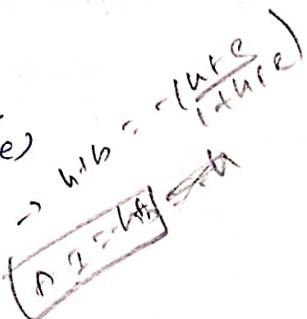

$$R_I = \frac{V_e}{I_e} = \frac{-I_b h_{ie}}{-I_b(1+h_{fe})}$$

$$R_I = \frac{h_{ie}}{1+h_{fe}}$$

$$A_V = A_I \cdot \frac{R_L}{R_I}$$

$$= \frac{h_{fe}}{1+h_{fe}} \cdot \frac{R_L}{h_{ie}}$$

$$A_V = \frac{h_{fe} R_L}{h_{ie}}$$

④

$$R_o = \frac{V_C}{I_C} \mid V_S = 0$$

$$= \frac{V_C}{0}$$

$$R_o = \infty$$

$$R'_o = \alpha R_L$$

$$R'_o = R_L$$


$$\textcircled{3} \quad A_{VS} = A_V \cdot \frac{R_i}{R_i + R_S}$$

$$\textcircled{6} \quad A_{IS} = A_I \cdot \frac{R_S}{R_S + R_i}$$

### APPROXIMATE HYBRID MODEL FOR C.C.

$$\textcircled{1} \quad A_I = \frac{I_L}{I_B} = -\frac{\beta e}{I_B} = I_B(1+h_{fe})$$

$$A_I = 1+h_{fe}$$

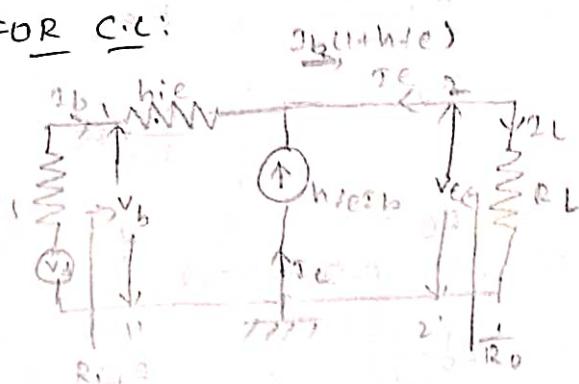

$$\textcircled{2} \quad R_I = \frac{V_b}{I_B}$$

$$\rightarrow V_b = h_{ie} I_B + I_C R_L$$

$$= h_{ie} I_B + I_B(1+h_{fe}) R_L$$

$$\therefore R_I = \frac{h_{ie} I_B + I_B(1+h_{fe}) R_L}{I_B}$$

$$R_I = h_{ie} + (1+h_{fe}) R_L$$

$$\textcircled{3} \quad A_V = A_I \cdot \frac{R_L}{R_I}$$

$$A_V = \frac{(1+h_{fe})}{h_{ie} + (1+h_{fe}) R_L} \cdot R_L$$

$$\therefore A_V = \frac{(1+h_{fe}) R_L}{(1+h_{fe}) R_L + h_{ie}}$$

$$A_V \approx 1$$

$$\textcircled{4} \quad R_O = \frac{V_e}{I_e} = -\frac{I_B(R_S + h_{ie})}{I_B(1+h_{fe})}$$

$$R_O = \frac{R_S + h_{ie}}{1+h_{fe}}$$

$$\textcircled{5} \quad A_{VS} = A_V \cdot \frac{R_i}{R_i + R_S}$$

$$\textcircled{6} \quad A_{IS} = A_I \cdot \frac{R_S}{R_S + R_i}$$

Summary of approximate evaluations of all configurations with the condition "hoe.RL <= 0.1":

Parameter	CE	CC	CB
$A_I$	$-h_{fe}$	$1+h_{fe}$	$\frac{h_{fe}}{1+h_{fe}}$
$R_i$	$h_{ie}$	$h_{ie} + (1+h_{fe})R_L$	$\frac{h_{ie}}{1+h_{fe}}$
$A_V$	$\frac{-h_{fe}}{h_{ie}} R_L$	$\frac{(1+h_{fe})R_L}{h_{ie} + R_L(1+h_{fe})}$	$\frac{h_{fe}}{h_{ie}} R_L$
$R_o$	$\alpha$	$\frac{R_s + h_{ie}}{1+h_{fe}}$	$\alpha$
$R_o'$	$R_L$	$R_o    R_L$	$R_L$

Q: A common emitter amplifier is driven by a voltage source of internal resistance  $R_s = 800\Omega$ , and the load impedance is a resistance  $R_L = 1000\Omega$ , the h-parameters are  $h_{ie} = 1k\Omega$ ;  $h_{re} = 2 \times 10^4$ ;  $h_{re} = 50$ ;  $h_{oe} = 25 \mu A/V$ . Compute the current gain  $A_I$ , input resistance  $R_i$ ,  $A_V$ ,  $R_o$  using exact analysis and using approximate analysis.

SOL: ① EXACT ANALYSIS:

$$A_I = \frac{-h_{fe}}{1+h_{oe}R_L}$$

$$= \frac{-50}{1+0.25}$$

$$= \frac{-50}{1.025}$$

$$A_I = -48.78$$

② APPROXIMATE ANALYSIS:

$$A_I = -h_{ie}$$

$$A_I = -50$$

$$h_{oe}R_L = 25 \times 10^{-6} \times 1000$$

$$h_{oe}R_L = 0.025$$

$$R_i = h_{ie} + h_{re} \cdot A_I \cdot R_L$$

$$= 1k\Omega + 2 \times 10^4 \times -50 \times 10^3$$

$$= 1k\Omega + 100 \times 10^7$$

$$R_i = 1k\Omega + 10^8 = 990.20$$

$$A_V = \frac{A_I \cdot R_L}{R_i}$$

$$= -48.78 \times \frac{10^3}{990.20}$$

$$A_V = -48.77$$

$$R_i = h_{ie}$$

$$R_i = 1k\Omega$$

$$A_V = \frac{-h_{fe}}{h_{ie}} R_L$$

$$= -\frac{50}{1k\Omega} \times 10^3$$

$$\times R_0 = \frac{1}{h_{fe}}$$

$$= \frac{1}{h_{oe} - h_{re}} = \frac{1}{25 \times 10^6 - 10^2}$$

$$\times R_0 = \alpha$$

$$800 + 10^3$$

$$R_0 = 51.42 \text{ k}\Omega$$

Section 2 of which requires additional  $R_0$  to be

$$\times R_0' = R_L \quad \text{and} \quad R_0' = R_0$$

If  $\beta = 100$ ,  $R_0$  is equal to  $R_0'$  and  $R_0$  is minimum

parameters  $25\text{G}, 1\text{VA}, 0.2\text{mA}, 0.01\text{A}$  values are used

- (3) A voltage source of internal resistance,  $R_s = 900\Omega$ , drives a CC amplifier using load resistance,  $R_L = 2000\Omega$ . The CE  $h$ -parameters are  $h_{ie} = 1200\Omega$ ,  $h_{re} = 2 \times 10^{-4}$ ,  $h_{pe} = 60$ ,  $h_{oe} = 2.5 \mu\text{A}/\text{V}$ . Compute  $A_I$ ,  $R_i$ ,  $A_V$ ,  $R_o$  using Exact & Approximate analysis.

(a) EXACT ANALYSIS APPROXIMATE ANALYSIS

$$\begin{aligned} \textcircled{1} \quad A_I &= -\frac{h_{fe}}{1+h_{oe}R_L} \\ &= +\frac{(1+h_{fe})}{1+h_{oe}R_L} \\ &= \frac{1+160}{1+25 \times 10^6 \times 2 \times 10^3} \\ &= \frac{61}{1+5 \times 10^2} \\ &= \frac{61}{1+0.05} \\ A_I &= 58.095 \end{aligned}$$

$$\begin{aligned} \textcircled{1} \quad A_I &= 1+h_{fe} \\ &= 1+60 \\ A_I &= 61 \end{aligned}$$

$$\begin{aligned} \textcircled{2} \quad R_i &= h_{ie} + (1+h_{fe})R_L \\ &= 1200 + (1+60) 2 \times 10^3 \\ &= 1200 + 122 \times 10^3 \\ &= 123200 \\ R_i &= 123.2 \text{ k}\Omega \end{aligned}$$

$$\begin{aligned} \textcircled{3} \quad A_V &= \frac{(1+h_{fe})R_L}{h_{ie} + (1+h_{fe})R_L} \\ &= \frac{61 \times 2 \times 10^3}{123.2 \times 10^3} \end{aligned}$$

$$A_V = 0.9902$$

$$\begin{aligned} \textcircled{2} \quad R_i &= h_{ie} + h_{re} \cdot A_I \cdot R_L \\ &= 1200 + 1 \times 58.095 \times 2 \times 10^3 \\ &= 1200 + 116190 \\ &= 117390 \\ R_i &= 117.39 \text{ k}\Omega \end{aligned}$$

$$\begin{aligned} \textcircled{3} \quad A_V &= A_I \cdot \frac{R_L}{R_i} \\ &= 58.095 \times 2 \times 10^3 \\ &\quad / 117.39 \times 10^3 \\ &= 58.095 \times 0.017 \\ A_V &= 0.987 \end{aligned}$$

$$\begin{aligned} \textcircled{4} \quad R_o &= \frac{R_s + h_{ie}}{1+h_{fe}} \\ &= \frac{900 + 1200}{1+60} \\ R_o &= \frac{2100}{61} \\ R_o &= 34.42 \end{aligned}$$

$$\textcircled{4} \quad R_0 = \frac{1}{Y_0}$$

$$= \frac{1}{h_{oc} - h_{re}h_{tc}} = \frac{1}{\frac{1}{R_s + h_{re}h_{tc}}} = \frac{1}{\frac{1}{25 \times 10^6 - 1.61}} = \frac{1}{\frac{1}{25 \times 10^6 + 0.0290476}} = \frac{1}{25 \times 10^6}$$

$$R_0 = 3.442$$

- \textcircled{3} For a CB transistor amplifier driven by a voltage source of internal resistance,  $R_s = 1200\Omega$ ,  $R_L = 1000\Omega$ , the h-parameters are  $h_{ib} = 22\Omega$ ,  $h_{rb} = 3 \times 10^{-4}$ ,  $h_{fb} = -0.98$ ,  $h_{ob} = 0.5 \mu\text{A}/\text{V}$ . Compute  $A_I$ ,  $R_i$ ,  $A_v$ ,  $R_o$ ,  $A_{IS}$ ,  $A_P$ , using exact and approximate analysis.

SOL:

$$\text{Given, } R_s = 1200\Omega$$

$$R_L = 1000\Omega$$

$$h_{ib} = 22\Omega$$

$$h_{rb} = 3 \times 10^{-4}$$

$$h_{fb} = -0.98$$

$$h_{ob} = 0.5 \mu\text{A}/\text{V}$$

$$h_{ib} : \frac{h_{ie}}{1+h_{fe}}$$

$$h_{rb} : \frac{h_{ie} \cdot h_{re}}{1+h_{fe}} - h_{re}$$

$$h_{fb} : -h_{fe}/1+h_{fe}$$

$$h_{ob} : h_{oe}/h_{ie}$$

### EXACT ANALYSIS:

$$\textcircled{1} \quad A_I = \frac{-h_{fb}}{1+h_{ob}R_L} = \frac{+0.98}{1+0.5 \times 10^6 \times 10^3} = \frac{0.98}{1+0.0005} = \frac{0.98}{0.98} = 0.979$$

$$\rightarrow A_I = \frac{-h_{fb}}{(1+h_{ob})R_L} = \frac{0.98}{(1+0.5) \times 10^3} = 0.98 \times 10^{-3}$$

$$\rightarrow R_i = h_{ib} \cdot h_{re} \cdot R_L = 22 \times 3 \times 10^{-4} \times 10^3 = 66 \Omega$$

$$\rightarrow A_v = A_I \cdot \frac{R_L}{R_i} = \frac{0.98}{0.98} \times \frac{10^3}{66} = 0.261 \Omega$$

$$\rightarrow R_o = \frac{1}{h_{ob} + h_{re}} = \frac{1}{0.5 + 3 \times 10^{-4}} = 333 \Omega$$

$$\rightarrow A_{IS} = \frac{R_L}{R_i + R_o} = \frac{10^3}{66 + 333} = 0.8 \Omega$$

$$\rightarrow A_P = \frac{R_L}{R_i + R_o} = \frac{10^3}{66 + 333} = 0.8 \Omega$$

$$\rightarrow A_{IS} = \frac{R_L}{R_i + R_o} = \frac{10^3}{66 + 333} = 0.8 \Omega$$

$$\textcircled{2} \quad R_i = h_{ib} + h_{rb} \cdot A_I \cdot R_L$$

$$= 22 + (3 \times 10^{-4} \times 0.979 \times 10^3)$$

$$= 22 + 2.937 \times 10^1$$

$$R_i = 22.2937 \Omega$$

$$\textcircled{3} \quad A_v = A_I \cdot \frac{R_L}{R_i} = \frac{0.979 \times 10^3}{22.2937} = 43.913$$

$$= 0.043913 \times 10^3$$

$$A_v = 43.913$$

$$\textcircled{4} \quad R_o = \frac{1}{0.5 \times 10^6 + 3 \times 10^{-4} \cdot 0.98}$$

$$= \frac{1}{0.5 \times 10^6 + 2.94 \times 10^{-4}} = \frac{1}{0.5 \times 10^6 + 2.94 \times 10^{-4}} = 333 \Omega$$

$$R_o =$$

$$R_o = \frac{10^6}{0.7405} = 132013 \text{ kN/mm}^2 \text{ (approx 22 MPa)}$$

$$R_o = 1.35 \times 10^6 \text{ N/mm}^2 \text{ (approx 22 MPa)}$$

$$\Rightarrow y_o = 0.7405 \times 10^6$$

$$\textcircled{5} \quad A_{us} = A_u \cdot \frac{R_i}{R_i + R_o}$$

$$= 43.913 \cdot \frac{22.293}{1222.29}$$

$$= \frac{978.952}{1222.29}$$

$$\boxed{A_{us} = 0.8009}$$

$$\textcircled{6} \quad A_{is} = A_i \cdot \frac{R_s}{R_s + R_o}$$

$$= 0.929 \times \frac{1200}{1222.29}$$

$$= \frac{1174.8}{1222.29}$$

$$\boxed{A_{is} = 0.9611}$$

$$\textcircled{7} \quad A_p = A_v \cdot A_i$$

$$= 0.939 \times 43.913$$

$$\boxed{A_p = 42.99}$$

Approximate analysis

$$R_f = -W_b = +0.98$$

$$R_i = +W_b = 22 \text{ N/mm}^2$$

$$R_o = +W_b = 22 \text{ N/mm}^2$$

$$A_v = \frac{-W_b}{R_i} = \frac{0.98}{22} \times 1000 = \frac{98}{22} = 44.54$$

$$A_{us} = \frac{-W_b}{R_o} = \frac{0.98}{22} \times 1000 = \frac{98}{22} = 44.54$$



$$R_o = d = 44.54 \text{ N/mm}^2$$

$$A_p = A_v \cdot A_i = 0.98 \times 44.54 = 43.64$$

$$A_{us} = A_u \cdot \frac{R_i}{R_i + R_o} = 0.98 \times \frac{22}{22 + 44.54} = 0.298$$

$$A_{is} = A_i \cdot \frac{R_i}{R_i + R_o} = 0.98 \times \frac{1200}{1200 + 44.54} = 0.958$$
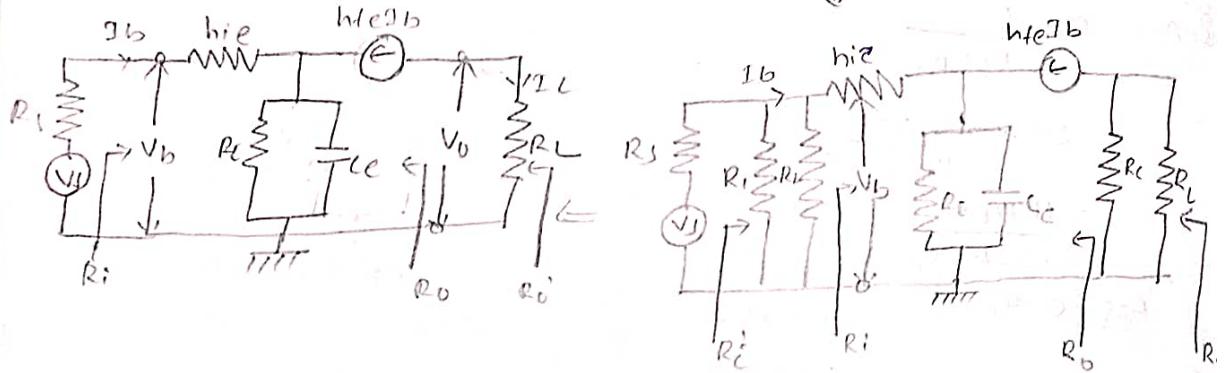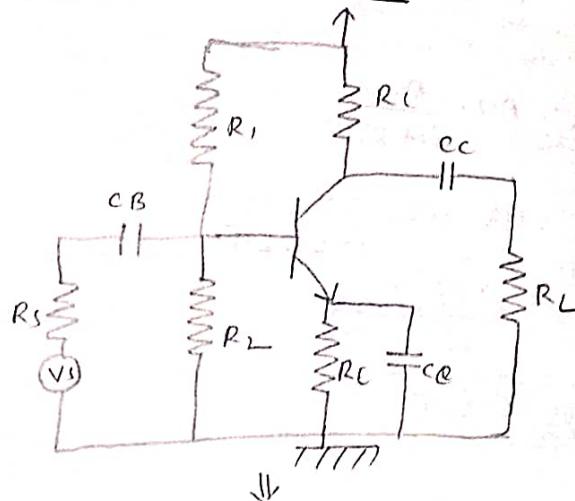
## EFFECT OF BIASS CAPACITOR AND BLOCKING COUPLING CAPACITOR ON LOW FREQUENCY RESPONSE.




The equations which we have obtained for current and voltage gain for a small signal amplifier are applicable in the midband frequency region. Where, it is assumed that reactance of coupling & bypass capacitors is negligible in this region.

Assume that in the low frequency region, the capacitors  $C_B$  &  $C_C$  are sufficiently large so that its reactance is small it doesn't have any effect on the response. Further it is assumed  $R_1, R_2$  is much larger than  $R_L$ .

$$* A_v = \frac{V_o}{V_s}$$

$$\rightarrow V_o = I_L R_L$$



$$V_b = -h_{fe} I_b R_L$$

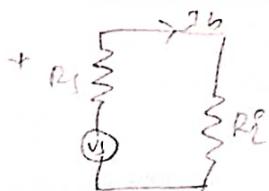

$$I_b = \frac{V_s}{R_s + R_i}$$

$$\rightarrow R_i = \frac{V_b}{I_b}$$
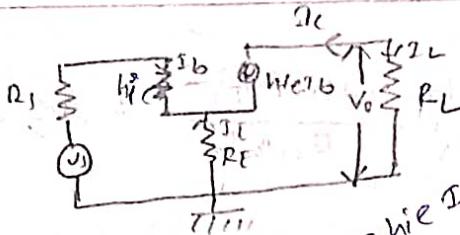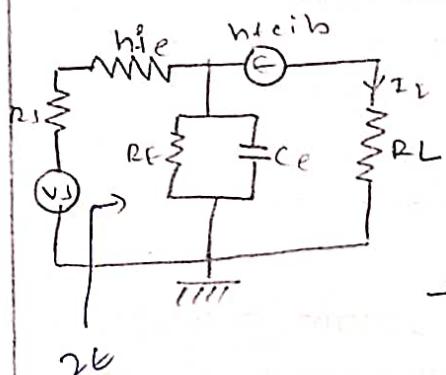
$$V_b = I_b h_{ie} + (1+h_{fe}) I_b \cdot R_E$$



$V_b = h_{ie} I_b + (1+h_{fe}) I_b \cdot R_E$   
 Schaltung (Ausgangsstrom)  
 $\approx I_b h_{ie} + I_b h_{fe} R_E$

$$R_i = \frac{V_b}{I_b} = h_{ie} + (1+h_{fe}) R_E$$

$$R_i = h_{ie} + (1+h_{fe}) Z_E$$

$$\rightarrow Z_E = (R_E || \frac{1}{j\omega C_E})$$

$$= \frac{R_E}{R_E + \frac{1}{j\omega C_E}}$$

$$Z_E = \frac{R_E}{1 + R_E j\omega C_E}$$

$$\therefore R_i = h_{ie} + (1+h_{fe}) \cdot \frac{R_E}{1 + R_E j\omega C_E}$$

$$\therefore I_b = \frac{V_s}{R_s + h_{ie} + (1+h_{fe}) R_E}$$

$$\boxed{AV_{(MF)} \frac{V_o}{V_s} = \frac{-h_{fe} R_L}{R_s + h_{ie} + (1+h_{fe}) R_E}}$$

At midband frequency,  $\omega$  is high. Therefore,  $\frac{(1+h_{fe}) R_E}{1 + R_E j\omega C_E}$  is neglected comparing with  $R_s + h_{ie}$ .

$$\therefore \boxed{AV_{(MF)} = \frac{-h_{fe} R_L}{R_s + h_{ie}}}$$

~~$AV_{(MF)} = \frac{-h_{fe} R_L}{R_s + h_{ie} + (1+h_{fe}) R_E}$~~

$$\therefore \frac{AV_{(LF)}}{AV_{(MF)}} = \frac{R_s + h_{ie}}{R_s + h_{ie} + (1+h_{fe}) R_E}$$

$$= \frac{1}{1 + (1+h_{fe}) R_E} \cdot \frac{1}{R_s + h_{ie}}$$

$$= \frac{1}{1 + (1+h_{fe}) R_E} \cdot \frac{1}{R_s + h_{ie}}$$

$$\text{let } b = \frac{(1+hfe)Re}{R_s + hfe} \quad \& \quad C = \omega R_e C_e$$

$$\therefore \frac{Av(LF)}{Av(MF)} = \frac{1}{1 + \frac{b}{1 + sc}} = \frac{1}{1 + \frac{b(1 - sc)}{1 + sc}}$$

$$= \frac{1}{1 + \frac{b - sbc}{sc}} \quad \because (sc > 1)$$

$$= \frac{1}{1 + \frac{b}{sc} - \frac{sb^2}{sc}}$$

$$\boxed{\frac{Av(LF)}{Av(MF)} = \frac{1}{1 - \frac{sb}{sc}}} \quad \because \left(\frac{b}{sc} \ll 1\right)$$

$$* Av(LF) = \frac{1}{1 - s \left( \frac{f_L}{f} \right)}$$

$$\therefore \frac{f_L}{f} = \frac{b}{c} = \frac{(1+hfe)Re}{R_s + hfe} \cdot \frac{1}{2\pi f R_e C_e}$$

$$f_L = \frac{(1+hfe)}{(R_s + hfe) 2\pi f c_e}$$

$$\therefore C_e = \frac{(1+hfe)}{(R_s + hfe) 2\pi f L_L}$$


\*  $f_L = \frac{1}{2\pi R_{eq} C_B}$

$$f_L = \frac{1}{2\pi [(R_s + R_B) || R_L] C_B}$$



\*  $f_L = \frac{1}{2\pi R_{eq} C_c}$

$$f_L = \frac{1}{2\pi [R_0 || (R_C + R_L)] C_C}$$

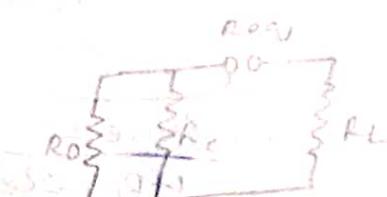

$$R_{eq} = R_0 || (R_C + R_L)$$



## \* HYBRID $\pi$ MODEL / TRANS CONDUCTANCE MODEL:

At high frequencies the capacitive effects of transistor junction and the delay in the response of the transistor caused by the process of diffusion carriers taken into account in determining the high frequency model of a transistor.

- A high frequency  $\pi$  model / aiaoleto model for transistor is shown in figure.

## \* HYBRID $\pi$ MODEL FOR A TRANSISTOR

### IN CE CONFIGURATION:

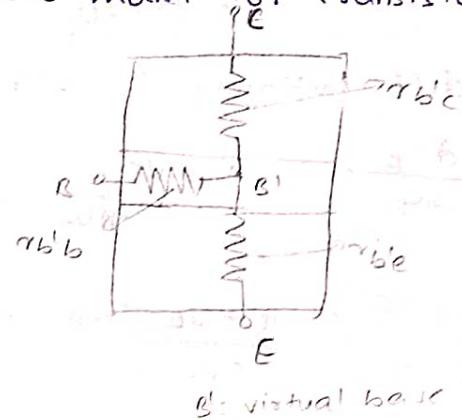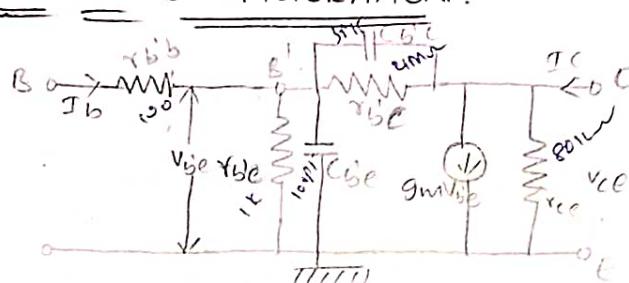

- $r_{bb'}$  :- is a base spreading resistance b/w actual Base 'b' & virtual base 'b''. Its Typical value is 100 $\Omega$ .
- $r_{be}$  :- Resistance b/w virtual base B' and emitter terminal 'E'. Typical value is 1k $\Omega$
- $r_{bc}$  : Resistance b/w virtual base B' and collector terminal 'c'. It has a large value, which is 4M $\Omega$ .
- $C_{be}$  ( $C_d$ ): Diffusion capacitance of the normally forward biased BE junction. Typical value is 700 pF.
- $C_{bc}$  ( $C_f$ ): Transition capacitance of the normally reverse biased CB junction. Typical value is 3pF.
- $g_{mVbe}$  : Output current generator where 'gm' is the trans conductance of the transistor.
- $r_{ce}$  : Output resistance with a typical value of 80k $\Omega$ .

## . Hybrid $\pi$ Conductance In Terms of Low Frequency h-parameters:

$$\rightarrow I_C = I_0 - \alpha I_E$$

$$\Rightarrow \alpha = \frac{I_0 - I_C}{I_E}$$

$$\Rightarrow I_C = -\alpha I_E$$

$I_C = \alpha I_E$

$$\Rightarrow I_E = I_0 e^{\frac{V_E}{nV_T} - 1}$$

$$I_E = I_0 (e^{\frac{V_E}{nV_T} - 1})$$

$$I_E = I_0 e^{\frac{V_E}{nV_T}} - I_0$$

$$\Rightarrow \boxed{I_0 e^{\frac{V_E}{nV_T}} = I_E + I_0}$$

- differentiating ' $I_E$ ' w.r.t ' $V_E$ ',

$$\begin{aligned}\frac{dI_E}{dV_E} &= I_0 \cdot e^{\frac{V_E}{nV_T}} \cdot \frac{1}{nV_T} \\ &= \frac{I_E + I_0}{nV_T}\end{aligned}$$


$$\boxed{\frac{dI_E}{dV_E} = \frac{I_E + I_0}{nV_T}}$$

$$\Rightarrow \text{Trans conductance, } g_m = \frac{dI_C}{dV_E}$$

$$\begin{aligned}&\text{From above, } \frac{dI_E}{dV_E} = \frac{I_E + I_0}{nV_T} \\ &\therefore g_m = \frac{dI_E}{dV_E} \\ &= \alpha \cdot \frac{dI_E}{dV_E} \\ &= \alpha \cdot \frac{I_E + I_0}{nV_T} \\ &\text{In terms of collector current, } I_C = I_E + I_0 \\ &\therefore g_m = \alpha \cdot \frac{I_C}{nV_T}\end{aligned}$$

$$g_m = \frac{-I_C}{nV_T}$$

$$\boxed{g_m = \frac{I_C}{V_T}}$$

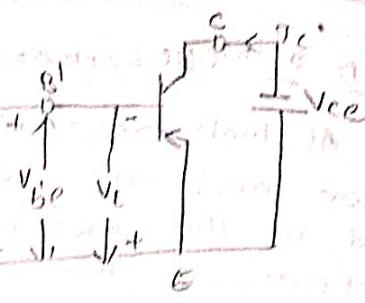

- FOR either type of transistor,  $g_m$  is inv., where break

$$g_m \propto I \quad \& \quad g_m \propto \frac{1}{T}$$

## Hybrid $\pi$ Model at low frequency:

(Neglecting all capacitances).

\* Input Conductance ( $g_{be}$ ):  $B_o \xrightarrow{I_b} r_{be}$

$$V_{be} = I_b r_{be}$$

$$I_c = g_m V_{be}$$

$$V_{be} = \frac{I_c}{g_m}$$


$$\Rightarrow V_{be} = I_b r_{be}$$

$$\frac{I_c}{g_m} = I_b r_{be}$$

$$\frac{I_c}{I_b} = g_m r_{be}$$

$$h_{fe} = g_m r_{be}$$

$$\boxed{g_{be} = \frac{g_m}{h_{fe}}}$$

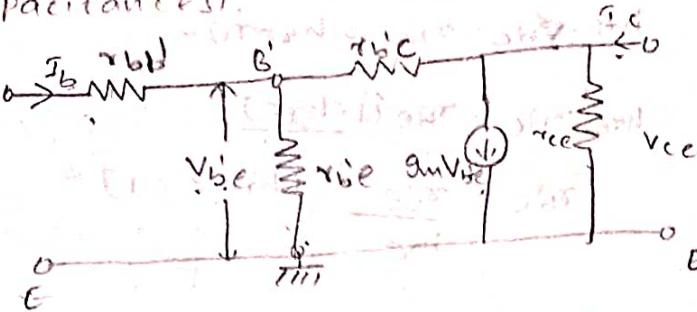

-  $r_{bc}$  is very high  $\Rightarrow$   $I_b$  does not flow

-  $I_c$  also will not flow through  $r_{bc}$

$\boxed{g_{be} = \frac{g_m}{h_{fe}}}$

$$g_{be} = \frac{g_m}{h_{fe}}$$

\* Base spreading resistance ( $r_{bb}$ ):

- Input resistance with the output is short circuited,

$$V_{be} = I_b(r_{bb} + r_{be})$$

$$\frac{V_{be}}{I_b} = r_{bb} + r_{be}$$


$$h_{ie} = r_{bb} + r_{be}$$

$$(\because I_b = h_{fe})$$

$$r_{bb} = h_{ie} - h_{fe}$$

$$r_{bb} = h_{ie} - r_{be}$$
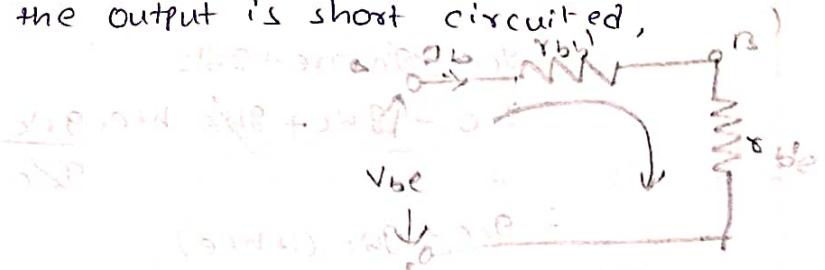
$$\boxed{r_{bb} = h_{ie} - \frac{h_{fe}}{g_m}}$$




\* Feedback Conductance ( $g_{bc}$ )

$$\Rightarrow V_{be} = V_{cc} \cdot \frac{r_{be}}{r_{be} + r_{bc}}$$

$$\frac{V_{be}}{V_{cc}} = \frac{r_{be}}{r_{be} + r_{bc}}$$
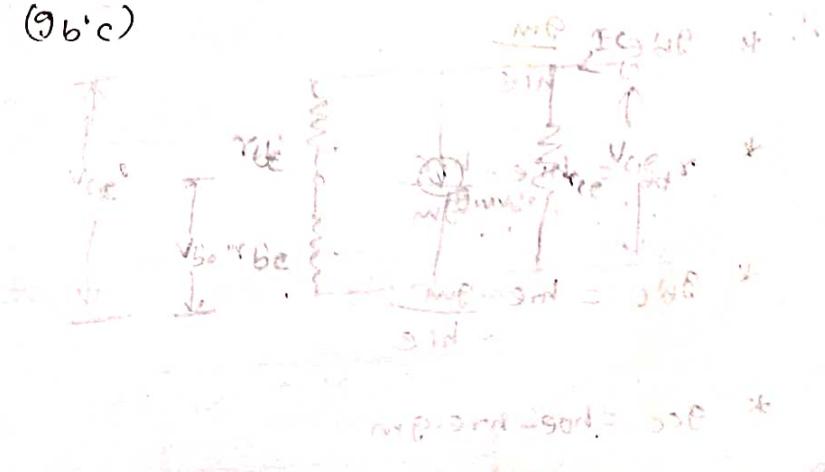
$$h_{re} = \frac{r_{be}}{r_{be} + r_{bc}}$$



$$hre \cdot gbe = \frac{gbe}{hre} - hre \cdot gbe$$

$$hre \cdot gbe = gbe(1 - hre)$$

$$\frac{gbe}{hre} = \frac{gbe}{hre} \quad (\text{hre} \ll 1)$$

$$gbe = hre \cdot gbe$$

$$gbe = hre \cdot \frac{gm}{hre}$$

$$\begin{aligned} gbe &= hre \cdot gbe \\ gbe &= hre \cdot gm \\ gbe &= \frac{hre \cdot gm}{hre} \end{aligned}$$

Output conductance ( $gce$ ):

$$* \quad i_c = \frac{v_{ee}}{r_{ee}} + g_m v_{be} + \frac{v_{cc}}{r_{bb'} + r_{be}}$$

$$\frac{i_c}{v_{ee}} = \frac{1}{r_{ee}} + g_m \cdot \frac{v_{ee} \cdot hre}{v_{ee}} + \frac{1}{r_{be}} \quad [r_{be} \gg r_{bb'}]$$

$$\begin{aligned} hre &= \frac{1}{r_{ee}} + g_m hre + \frac{1}{r_{be}} \\ &= gce + g_m hre + gbe \\ &= gce + gbe + gbe \cdot hre \cdot \frac{gbe}{gbe} \quad [\because hre = \frac{gbe}{gbe}] \\ &= gce + gbe (1 - hre) \end{aligned}$$

$$hre = gce + gbe \cdot hre \quad (\text{hre} \gg 1)$$

$$gce = hre - \frac{gbe}{hre} \cdot hre$$

$$[gce = hre - hre \cdot gm]$$

$$* \quad gbe = \frac{gm}{hre}$$

$$* \quad r_{bb'} = hre - \frac{hre}{gm}$$

$$* \quad gbe = hre \cdot \frac{gm}{hre}$$

$$* \quad gce = hre - hre \cdot gm$$

## CE short-circuit current gain:

$$I_1 = \frac{V_1 - V_2}{R} \quad * I_2 = \frac{V_2 - V_1}{R}$$

$$= V_B \left[ 1 - \frac{V_2}{V_1} \right]$$

$$= V_2 \left( 1 - \frac{V_1}{V_2} \right)$$

$$\frac{I_1}{V_1} = \frac{1-A}{R}$$

$$\frac{I_2}{V_2} = \frac{1-\frac{1}{A}}{R}$$

$$\therefore R_1 = \frac{R}{1-A}$$


$$R_2 = \frac{R}{1-\frac{1}{A}}$$

$$\frac{I_1}{V_1} = \frac{\gamma b' c}{(1-A)}$$

$$R_2 = \frac{RA}{A-1}$$

$$R_1 = \frac{\gamma b' c}{1-A}$$

$$R_2 = \frac{RA}{A-1}$$

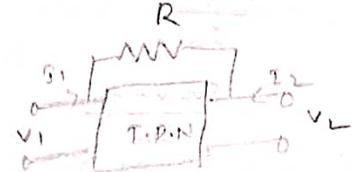

$$-jX_{CM} = -jX_{CC}$$

$$\frac{1}{2\pi C_m f} = \frac{1}{2\pi f X_C (1 + g_m R_L)}$$

$$\therefore [ A_V = \frac{V_{CC}}{V_B e}, R_C = I_L R_L = -j \omega R_L = -9mV_b'e.R_L ]$$

$$[ A_V = \frac{-9mV_b'e \cdot R_L}{V_b'e} ]$$

$$A_V = -9m \cdot R_L$$


(AV = -9mR\_L)

$$C_m = C_C (1 + g_m R_L)$$

$$* X_{CM} = \frac{X_{CC}}{1 - \frac{1}{A}}$$

$$= \frac{X_{CC}}{\left[ 1 - \left( \frac{1}{g_m R_L} \right) \right]}$$
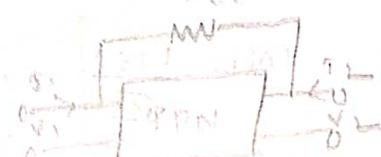
$$= \frac{X_{CC} (g_m R_L)}{g_m R_L + 1} = \frac{X_{CC} (g_m R_L)}{g_m R_L + 1}$$



$$\frac{1}{W \cdot C_m} = \frac{g_m R_L e}{W \cdot C_C (g_m R_L + 1)} = \frac{g_m R_L}{W (g_m R_L + 1)}$$

$$C_m = C_C (g_m R_L + 1)$$

$$\Rightarrow C_m = \frac{C_C (g_m R_L + 1)}{g_m R_L}$$

the transistor high frequency capability can be analyzed by expressing the CE short circuit current gain as a function of frequency.

$$\approx \alpha = \frac{I_C}{I_B}$$


$$= \frac{\beta}{I_B}$$

$$= \frac{g_m V_{BE}}{I_B}$$

$$= g_m \cdot \frac{V_{BE}^2}{I_B}$$

$$= g_m \cdot \frac{V_{BE}^2}{\omega_{CE} L (C_E + C_C) + 1}$$
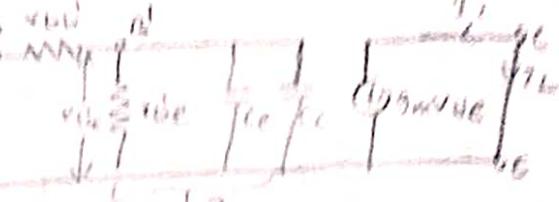
$$= - \frac{g_m \cdot V_{BE}^2}{\omega_{BE} L (C_E + C_C) + 1}$$



$$V_{BE} = I_B Z$$

$$Z = \omega_{BE} L - j \omega (C_E + C_C)$$

$$= \omega_{BE} L \frac{1}{j \omega (C_E + C_C)}$$

$$= \omega_{BE} L \frac{1}{\omega (C_E + C_C) + j \omega}$$


$$Z = \frac{\omega_{BE}^2 L}{\omega (C_E + C_C) + j \omega}$$

$$A_f = \frac{-h_{FE}}{1 + j \left( \frac{f}{f_B} \right)} \quad \left[ f_B = \frac{1}{\omega (C_E + C_C) + \omega_{BE}^2 L} \right] \quad \left( \text{with } \omega = \frac{2\pi f}{\lambda} \right)$$

$$|A_f| = \frac{h_{FE}}{\sqrt{1 + \left( \frac{f}{f_B} \right)^2}}$$

when,  $f = f_B$

$$|A_f| = \frac{h_{FE}}{\sqrt{2}}$$

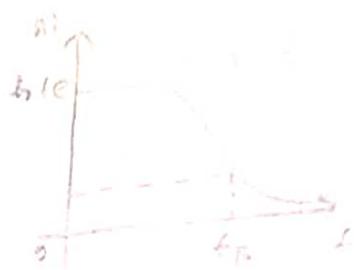

- The frequency range upto  $f_B$  is referred to as the Bandwidth of the circuit.

- The value of  $|Af|$  at  $\omega_{CO}$  is  $\underline{h_{FE}}$ .

$\rightarrow h_{FE}$  is the low frequency short circuit CE current gain.

$\rightarrow f_B$  is the frequency at which a transistor CE short circuit current gain drops  $3DB$  ( $\frac{1}{\sqrt{2}}$ ) times  $h_{FE}$ . From its value at lower mid frequencies.

$\rightarrow f_B$  is also called as "B-cut off frequency".

a. cutoff frequency: A CB amplifier has a much higher 3dB frequency than a CE amplifier with CP short circuited

$$A_i^o = \frac{I_L}{I_B}$$

$$A_i^o = -\frac{h_{fe}}{1 + \frac{f}{f_d} \left( \frac{f}{f_d} \right)}$$

$$h_{fb} = \frac{-h_{fe}}{1 + h_{fe}}$$

$$f_d = \frac{1}{2\pi R_B C_e (1 + h_{fe}) C_B e}$$

$$\approx \frac{h_{fe}}{2\pi R_B C_e C_B e}$$

$$f_d = \frac{h_{fe} f_B (C_B e + C_B c)}{C_B e}$$

$\Rightarrow f_d$  is the 'd' cutoff frequency at which the CB short-circuit current gain drops 3dB from its value at low frequencies.

Parameter ( $f_T$ ) :-

which is defined as the frequency at which s.c. CE current gain attains unit magnitude.

$$A_i^o = \frac{-h_{fe}}{1 + \frac{f}{f_B}}$$

$$|A_i^o| = 1$$

$$1 = \frac{h_{fe}}{\sqrt{1 + \left(\frac{f}{f_B}\right)^2}} \quad \left(\frac{f}{f_B}\right)^2 \gg 1$$


$$\therefore \frac{f_T}{f_B} = h_{fe}$$


$$f_T = h_{fe} \cdot f_B$$

$\Rightarrow f_T$  is gain, Band width product.

- In the case of CB,  $f_T = h_{fb} \cdot f_d$

CE Current gain with resistive load :-

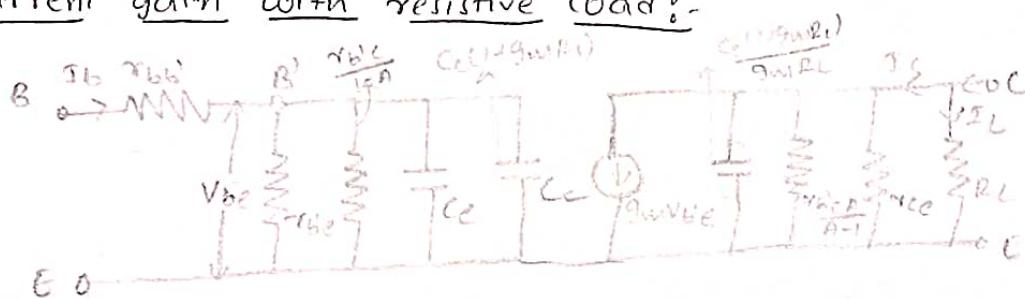

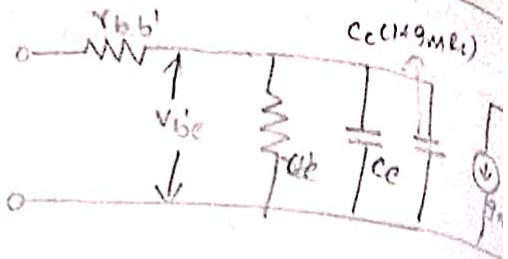

$$A_P = \frac{-h_{ie}}{1 + \beta \left( \frac{f}{f_2} \right)}$$

where,  $f_2 = \frac{1}{2\pi \cdot r_{be} (c_e + C_c (1 + g_m R_L))}$

21/11/2024

## 2. FET AMPLIFIERS

### - Field Effect Transistor

FET Amplifiers provide an excellent voltage gain with the added feature of high input impedance, they have low power consumption with a good frequency range, minimal size & weight. Therefore, FETs are preferable than BJTs. Both JFET & DEPLETION MOSFET devices can be used to design amplifiers having similar voltage gain. The depletion MOSFET circuit has much higher input impedance than a similar JFET configuration.

The common source configuration is the most popular one providing inverted and amplified signal. However, the CD [source follower] circuit provides unity gain with no inversion and CG circuit provides gain with no inversion.

Due to very high  $h_{IP}$  impedance, the  $h_{IP}$  current is generally assumed to be negligible, and it is of the order of few microamps ( $\mu A$ ) and the current gain is an undefined quantity.


### SMALL SIGNAL MODEL OF FET AMPLIFIER:

From the drain and transfer characteristics of the FET, the drain current is a function of drain-source voltage ( $V_{DS}$ ) & ~~gate~~-source voltage ( $V_{GS}$ ). The small signal model of FET can be drawn analogous to BJT.

$$i_d = f(V_{GS}, V_{DS})$$

The change in drain current is given approximately by first 2 terms in the Taylor's series expansion of above equation is,

$$\Delta i_d = \frac{\partial i_d}{\partial V_{GS}} \Big|_{V_{DS}} \Delta V_{GS} + \frac{\partial i_d}{\partial V_{DS}} \Big|_{V_{GS}} \Delta V_{DS}$$

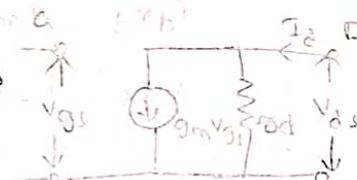

For small signal model notations become, SSM FET in CS

$$\Delta i_d = i_d ; \Delta V_{GS} = V_{GS} ; \Delta V_{DS} = V_{DS}$$

$$i_d = \frac{\partial i_d}{\partial V_{GS}} \Big|_{V_{DS}} \cdot V_{GS} + \frac{\partial i_d}{\partial V_{DS}} \Big|_{V_{GS}} \cdot V_{DS}$$

$$\Rightarrow \frac{\partial i_d}{\partial V_{GS}} \Big|_{V_{DS}} = \frac{\Delta i_d}{\Delta V_{GS}} \Big|_{V_{DS}} = g_m$$

$$\Rightarrow \frac{\partial i_d}{\partial V_{DS}} \Big|_{V_{GS}} = \frac{\Delta i_d}{\Delta V_{DS}} \Big|_{V_{GS}} = \frac{1}{r_d}$$

$$\begin{aligned} \therefore & V = I R \\ & V = IR \\ & I = \frac{V}{R} \\ & \frac{1}{R} = \frac{I}{V} \end{aligned}$$

$$\therefore \left( i_d = g_m V_{gs} + \frac{1}{r_d} \cdot V_{ds} \right)$$

A small signal model for FET in common source configuration is shown in figure-①, it has Norton output circuit with a dependent current generator, whose magnitude is proportional to the gate-source voltage.

- The proportionality factor is trans conductance  $g_m$
- $r_d$  is the internal drain resistance
- The input resistance b/w gate & source is infinite, since it is assumed that the reverse biased gate draws no current.
- The small signal model for CFET can be used for analysing the 3 basic FET amplifier configurations.

① Common Source


② Common Drain / Source Follower

③ Common Gate


- The CS amplifier provides good voltage amplification.
- The CD amplifier with high input impedance and near unity voltage gain is used as a Buffer amplifier.
- The CG amplifier is used as high frequency amplifier.
- The small signal current source model for the FET in CS configuration shown in figure ① is redrawn with the voltage source model (Thevenin's equivalent) is shown in Figure ⑤

$$i_d r_d = g_m v_{ds} + v_{ds}$$

$$v_{ds} = i_d r_d - g_m v_{gs}$$

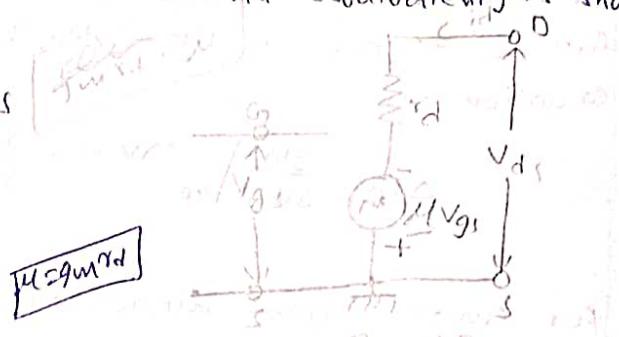

### COMMON SOURCE AMPLIFIER:

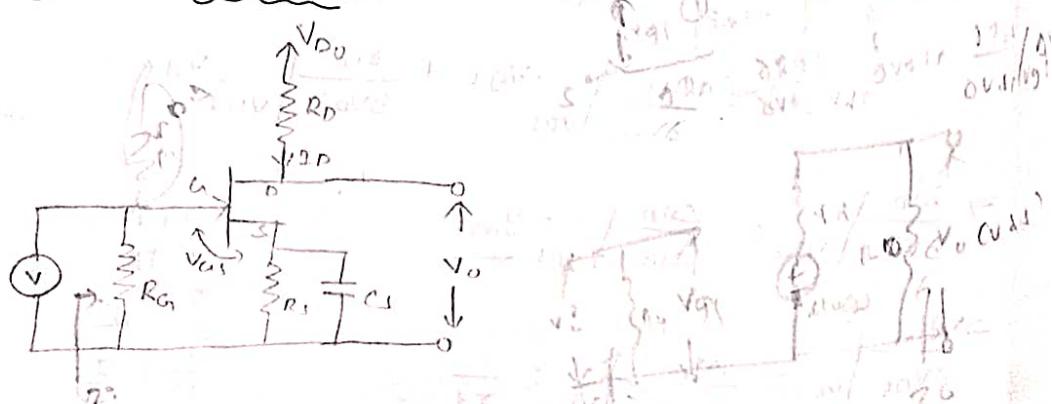

A simple CS amplifier is shown in figure and associated SCC circuit using voltage source model of FET is shown in figure.

#### \* Voltage gain:

It is the ratio of O/P voltage to I/P voltage.

$$A_v = \frac{O/P}{I/P} = \frac{V_{ds}}{V_{gs}}$$

$$\Rightarrow V_{ds} = -\mu V_{gs} \cdot \frac{R_D}{r_d + R_D}$$

$$\frac{V_{ds}}{V_{gs}} = -\mu \cdot \frac{R_D}{r_d + R_D}$$

$$A_v = -\frac{\mu R_D}{r_d + R_D}$$

#### \* Input impedance:

$$Z_i = R_u$$

with voltage divider bias,

$$Z_i = R_u // R_L$$


#### \* Output impedance:

Output impedance is the impedance measured at the o/p terminals with I/P voltage  $V_i = 0$ .

when,  $V_i = 0 \Rightarrow V_{gs} = 0$

$$\therefore \mu V_{gs} = 0$$

$$Z_o = r_d // R_D$$

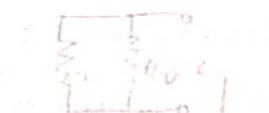

- Q1 In the CS amplifier as shown in figure  $R_D = 5\text{k}\Omega$ ,  $R_u = 10\text{M}\Omega$ ,  $\mu = 50$  &  $r_d = 35\text{k}\Omega$ . Evaluate  $A_v$ ,  $Z_i$ ,  $Z_o$ .

Given:  $R_D = 5\text{k}\Omega$

$R_u = 10\text{M}\Omega$

$\mu = 50$

$r_d = 35\text{k}\Omega$

$$\therefore A_v = -\frac{\mu \cdot R_D}{r_d + R_D}$$

$$A_v = -\frac{(50) \cdot 5}{35 + 5} = -\frac{250}{40} = -6.25$$

$$* Z_i = R_u = 10\text{M}\Omega$$

$$* Z_0 = R_d \parallel r_d$$

$$= 5 \text{ k}\Omega \parallel 35 \text{ k}\Omega$$

$$Z_0 = 5 \text{ k}\Omega$$

- Q) A FET amplifier in CS configuration uses a load resistance of  $500 \text{ k}\Omega$ . The AC drain resistance of the device is Transconductance is  $0.8 \text{ mA/V}$ . Calculate  $A_v$  of amplifier.
- Sol. Given,  $R_L = 500 \text{ k}\Omega$  ( $r_d$ )

$$r_d = 100 \text{ k}\Omega$$

$$g_m = 0.8$$

$$A_v = -80 \times 10^3 \times \frac{500 \times 10^3}{500 \times 10^3 + 100 \times 10^3}$$

$$= -\frac{4 \times 10^6}{600} = -\frac{4}{6} \times 10^4$$

$$= -0.66 \times 10^4$$

$$A_v = -6 \times 10^3$$

=

$$\mu = g_m r_d$$

$$\mu = 0.8 \times 100 \text{ k}\Omega$$

$$\mu = 80 \text{ k}\Omega$$

$$= -\frac{80 \times 500 \times 10^3}{(500+100) \times 10^3}$$

$$= -\frac{4 \times 10^3 \times 10^6}{600 \times 10^3}$$

$$= -\frac{4 \times 10^4}{6.67 \times 10^4}$$

$$= -0.667 \times 10^3$$

$$= -6.67 \times 10^3$$

### \* COMMON DRAIN AMPLIFIER:

$$i_d R_s + (i_d + g_m v_{gs}) r_d = 0$$

$$i_d R_s + i_d r_d - g_m v_{gs} r_d = 0$$

$$i_d R_s + i_d r_d - g_m (v_i - i_d R_s) r_d = 0$$

$$i_d R_s + i_d r_d - g_m v_i r_d + g_m i_d R_s r_d = 0$$


$$i_d [R_s + r_d + g_m R_s] = g_m v_i$$

$$\therefore i_d = \frac{g_m v_i}{r_d + (g_m + 1) R_s}$$




( $\cancel{\text{gm}} = \mu$ )

$$\rightarrow V_o = i_d R_s$$
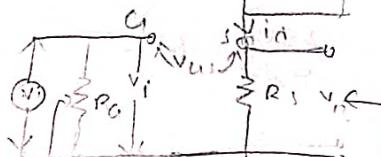
$$V_o = \frac{\mu v_i}{r_d + (\mu + 1) R_s} \cdot R_s$$



$$V_{gs} = V_i - i_d R_s$$

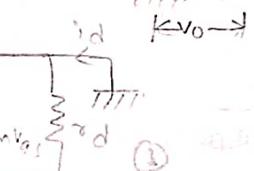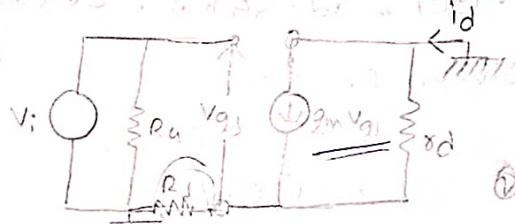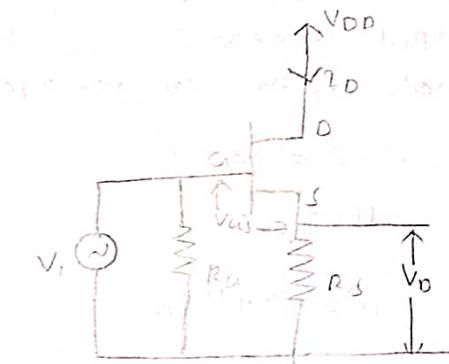

$$\frac{V_o}{V_i} = Av = \frac{\mu \cdot R_s}{R_s + (\mu+1)R_s}$$

$\approx d + (\mu+1)R_s$

$$= \frac{gm \cdot \left(\frac{\gamma d}{\mu+1}\right) R_s}{R_s + \left(\frac{\gamma d}{\mu+1}\right)}$$

$$= \frac{gm \cdot \gamma d \cdot R_s}{R_s + \frac{\gamma d}{\mu+1}} = \frac{gm \gamma d}{\mu+1}$$

$[R_s \gg \frac{\gamma d}{\mu+1}]$

$$Av = \frac{\mu}{\mu+1}$$

$(\mu > 1)$

$$Av = 1$$

$$\frac{V_o}{V_i} = 1$$

$$V_o = V_i$$

### \* Output grayscale:

$$V_o = id R_s$$

$$id = \frac{V_o}{R_s} = \frac{Av \cdot V_i}{R_s}$$

$$= \frac{\mu \cdot V_i \cdot R_s}{\mu+1}$$

$$\left(R_s + \frac{\gamma d}{\mu+1}\right) R_s$$

$$id = V_i \cdot \frac{\mu}{\mu+1}$$


$$R_s + \frac{\gamma d}{\mu+1}$$

$$\therefore Z_o = R_s \parallel \frac{\gamma d}{\mu+1} \quad [V_i = 0]$$

$$Z_o = R_s \parallel \frac{1}{gm}$$

$(\mu > 1)$

$$* Z_o = R_s$$

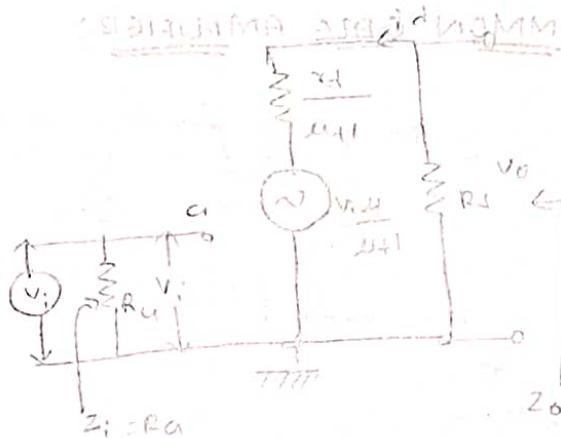

$$\left\{ \begin{array}{l} V_o = \frac{V_i \cdot \frac{\mu}{\mu+1} \cdot R_s}{R_s + \frac{\gamma d}{\mu+1}} \\ D_o = \frac{\gamma d}{\mu+1} \end{array} \right.$$

① The CD amplifier as shown in figure.  $\mu = 50$ ,  $R_s = 41\text{ k}\Omega$ ,  $R_o = 10\text{ M}\Omega$ . Evaluate voltage gain, input impedance & output impedance.

Sol.: Given,  $\mu = 50$

$$r_d = 35\text{ k}\Omega$$

$$R_s = 41\text{ k}\Omega$$

$$R_o = 10\text{ M}\Omega$$

$$AV = \frac{\mu R_o}{r_d + (\mu + 1)R_s}$$

$$= \frac{50 \times 10^6}{35 \times 10^3 + (50 + 1) \times 41 \times 10^3}$$

$$= \frac{50 \times 10^6}{35 \times 10^3 + 51 \times 41 \times 10^3}$$

$$= \frac{200}{17204} = \frac{200}{17204} \times 10^3$$

$$= 0.836 \times 10^3$$

$$\mu = g_m r_d$$

$$g_m = \frac{\mu}{r_d} = \frac{50}{35 \times 10^3}$$

$$= \frac{10 \times 10^6}{7}$$

$$= \frac{10^2}{7} = 0.1428$$

$$g_m = 1.428$$

② Input impedance,  $Z_i = R_s$

$$Z_i = 41\text{ k}\Omega$$

③ Output impedance,  $Z_o = R_s \parallel \frac{1}{g_m}$



$$= 41\text{ k}\Omega \parallel \frac{1}{1.428 \times 10^{-3}}$$

$$= 41\text{ k}\Omega \parallel 0.704\text{ k}\Omega$$

$$= \frac{2.816 \times 10^6}{4.704 \times 10^3} = 0.5918 \times 10^3$$

$$= 591.8\text{ k}\Omega \parallel$$

### \* COMMON GATE AMPLIFIER:

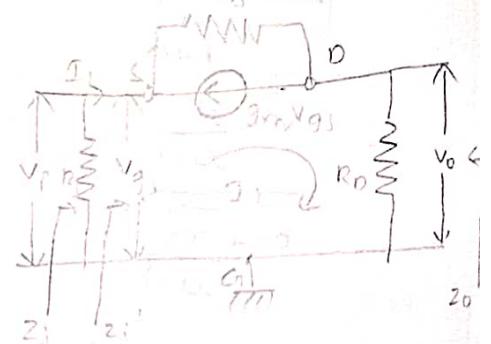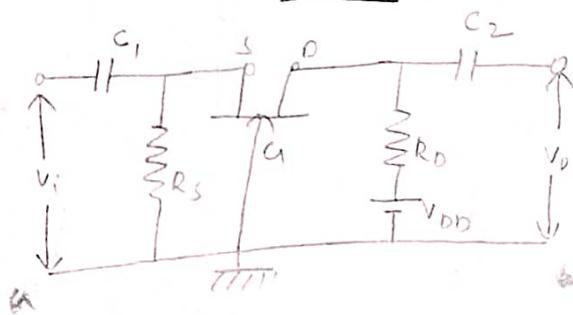

$$\rightarrow V_i = V_s$$

$$V_{gs} = V_g - V_s$$

$$= 0 - V_s$$

$$V_{gs} = -V_s$$

$$V_{gs} = -V_i$$

$$I_1 + g_m V_{GS} = I_{SD}$$

$$I_1 = I_{SD} - g_m V_{GS}$$

$$I_1 = \frac{V_S - I_1 R_D}{r_d} + g_m V_i$$

$$I_1 \left(1 + \frac{R_D}{r_d}\right) = V_S \left(\frac{1}{r_d} + g_m\right)$$

$$\frac{V_i}{I_1} = \frac{1 + \frac{R_D}{r_d}}{\frac{1}{r_d} + g_m}$$

$$Z_i = \frac{r_d + R_D}{1 + g_m r_d}$$

$$Z_i^* = Z_i \parallel R_s$$

$$Z_i = R_s \parallel \frac{r_d + R_D}{1 + g_m r_d}$$

$$= R_s \parallel \frac{r_d}{g_m r_d}$$

$$\begin{cases} r_d > R_D \\ g_m r_d \gg 1 \end{cases}$$

$$Z_i^* = R_s \parallel \frac{1}{g_m}$$


- \*  $Z_o$  is output impedance looking from output terminals with input short circuited.

$$\therefore V_i = 0$$

$$Z_o = r_d \parallel R_D$$

$$Z_o = R_D$$

(if  $r_d \gg R_D$ )

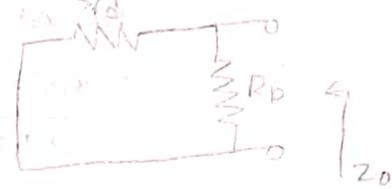

### Voltage gain:

$$V_o = r_d (i_d - g_m V_{GS}) + V_i$$

$$V_o = r_d \left( \frac{V_D}{R_D} - g_m V_{GS} \right) + V_i$$

$$V_o \left[ 1 + \frac{r_d}{R_D} \right] = V_i \left[ 1 + g_m r_d \right]$$

$$\frac{V_o}{V_i} = A_V = \frac{1 + g_m r_d}{1 + \frac{r_d}{R_D}}$$

$$A_V = \frac{R_D (1 + g_m r_d)}{r_d + R_D}$$

Q) Common Gate amplifier as shown in figure  $R_D = 2k\Omega$ ,  $R_S = 1k\Omega$ ,  $g_m = 1.43 \times 10^3$  and  $\tau_d = 35 \text{ nsec}$ . Evaluate  $A_v, Z_o$ .

Sol: Given,  $R_D = 2k\Omega$

$$R_S = 1k\Omega$$

$$g_m = 1.43 \times 10^3$$

$$\tau_d = 35 \text{ nsec}$$

$$\textcircled{1} A_v = \frac{R_D(1 + g_m \tau_d)}{R_D + \tau_d}$$

$$= \frac{2 \times 10^3 [1 + 1.43 \times 10^3 \times 35 \times 10^{-9}]}{2 \times 10^3 + 35 \times 10^3}$$

$$= \frac{2[1 + 1.43 \times 35]}{37} \quad (2.75)$$

$$A_v = 2.759$$

$$\textcircled{2} Z_i = \frac{\tau_d + R_D}{1 + g_m \tau_d} || R_S$$

$$= \frac{35 \times 10^3 + 2 \times 10^3}{1 + 1.43 \times 10^3 \times 35 \times 10^{-9}} || 1 \times 10^3$$

$$= \frac{37 \times 10^3}{1 + 1.43 \times 35} || 1 \times 10^3$$

$$= \frac{37 \times 10^3}{51.05} || 1 \times 10^3$$



$$= 0.724 || 1 \times 10^3$$

$$\textcircled{3} Z_o = \tau_d || R_D$$

$$= 35 \text{ k}\Omega || 2 \text{ k}\Omega$$

$$Z_o = 2 \text{ k}\Omega$$

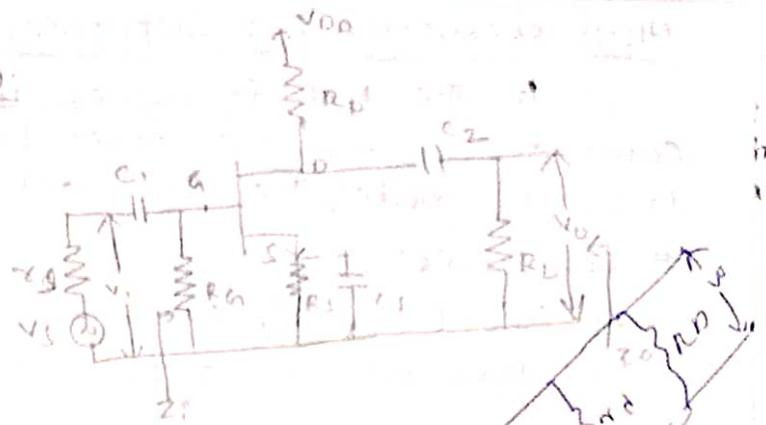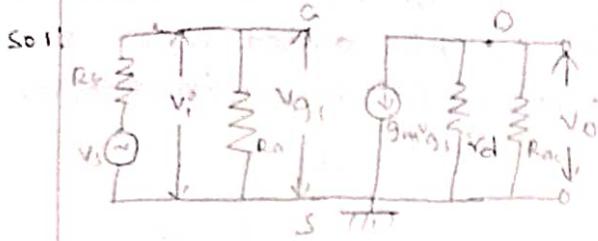(2) Calculate,  $\bar{A}v$ ,  $\bar{Av}_s$ ,  $\bar{z}_1^o$ ,  $\bar{z}_0$ .



$$⑥ v_0 = \sqrt{g_m g_s} [r_d / (R_D)]$$

$$V_D = -g m \cdot v_i^2 \left[ \frac{r_d \cdot R_D}{R_{D-1} \cdot x_d} \right]$$

$$\frac{V_0}{V_i} = -g_m \left[ \frac{\gamma_d R_D}{R_D + \gamma_d} \right]$$

$$Av = -g_m \left[ \frac{2dR_D}{R_D + 2d} \right]$$

$$\textcircled{2} \quad V_{QJ} = V_S \left[ \frac{R_U}{R_S + R_U} \right]$$

$$V_S = V_{GS} \left( \frac{R_S + R_U}{R_U} \right)$$

$$\therefore \text{Ans} = \frac{V_0}{V_1} = \frac{-g m V g / s \left( 2 d / R_D \right)}{V g / s \left[ \frac{R_1 + R_2}{2 a_1} \right]}$$

$$Avs = -g_m \left[ \frac{\frac{3d+RD}{3d+RD}}{\frac{Rs+Ru}{Ru}} \right]$$

$$\textcircled{3} \quad z_1^o = R_G$$

$$\textcircled{4} \quad z_0 = \operatorname{Re} z_1 \approx 1$$


23 - POLLY J

## HIGH FREQUENCY FET AMPLIFIERS:-

In the high frequency model of FET, the ~~charac~~ capacitances b/w the nodes have to be added in the frequency model, the resultant circuit is shown in fig.

\*  $C_{C1}, C_{C2}, C_S$ :

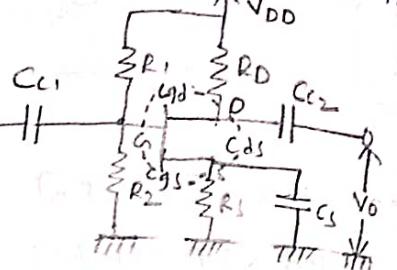→ At low Frequency:  $f \rightarrow 0$  &  $X_C \rightarrow \infty$   
-Capacitors act like a open circuit.




→ At high Frequencies:  $f \rightarrow \infty$  &  $X_C \rightarrow 0$

-At high Frequencies, the capacitors,  $C_{C1}$ ,  $C_{C2}$ , &  $C_S$  will not play any role, simply acts like a short circuit.


\*  $C_{GS}, C_{GD}, C_{DS}$ :

→ At low Frequency:  $f \rightarrow 0$  &  $X_C \rightarrow \infty$   
-Capacitors act like a open circuit.

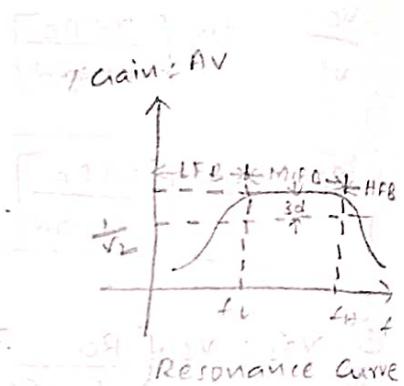→ At high Frequency:  $f \rightarrow \infty$  &  $X_C \rightarrow 0$   
-Capacitors act like a short circuit.



→ Equivalent circuit:

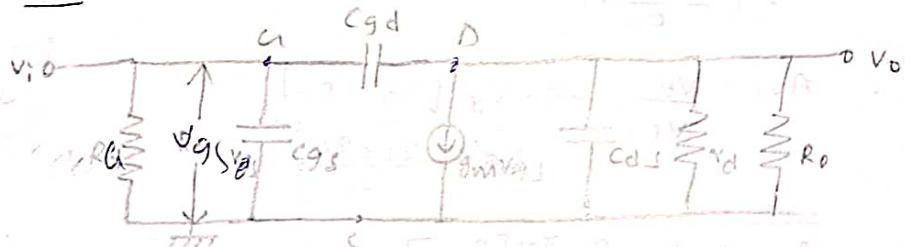

$$\Rightarrow C_{eq} = C_{Gd} + C_{mi}$$

$$f_H = \frac{1}{2\pi R C}$$

$$f_{H^i} = \frac{1}{2\pi R C_{eq}}$$

$$f_{HO} = \frac{1}{2\pi R' C_{eq}}$$

$$C_{mi} = C_{Gd} (1 - A_V)$$

$$C_{mo} = C_{Gd} \left(1 - \frac{1}{A_V}\right)$$

$$\therefore f_H = \min [f_{H^i} + f_{HO}] V_o$$

→  $C_{GS}$  represents the barrier capacitance b/w g & s



→  $C_{GD}$  represents the barrier capacitance b/w gate and drain.

→  $C_{ds}$  is the source capacitance of the channel. [feedback from  $\text{O/P} \times$  These internal capacitances lead to feedback from  $\text{O/P}$  to  $\text{I/P}$  and the voltage amplification decreases at high frequencies.]

The parameters of FET are shown in the table:

Parameter	$g_m$	$\text{Z}_d$	$C_{ds}$	$C_{gs}$	$C_{gd}$	$\text{Z}_{gs}$	$\text{Z}_{gd}$
Range	$0.1-10 \frac{\text{mA}}{\text{V}}$	$0.1-1 \text{M}\Omega$	$0.1-1 \text{PF}$	$1-10 \text{PF}$	$>10^8 \Omega$	$>10^8 \Omega$	$>10^8 \Omega$
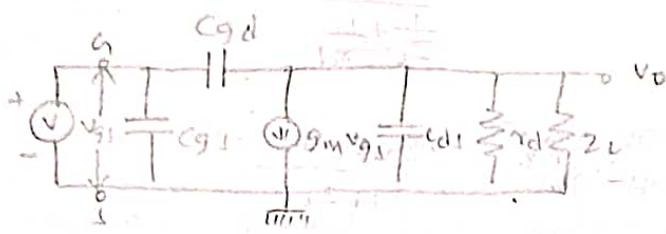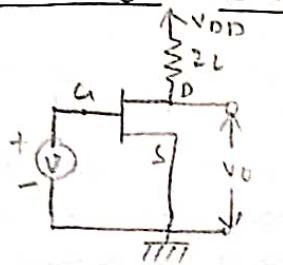
### \* Common Source Amplifier at high Frequency:



small signal equivalent circuit of CS amplifier at high frequencies

→ Admittance at  $\text{O/P}$  point is,

$$Y = \frac{1}{Z} = Y_L + Y_d + Y_{gd} + Y_{ds}$$

where,

-  $Y_L = \frac{1}{Z_L}$  is admittance corresponding to  $Z_L$ .

-  $Y_d = \frac{1}{g_d}$  is conductance corresponding to  $\text{Z}_d$ .

-  $Y_{ds} = j\omega C_{ds}$  is admittance corresponding to  $C_{ds}$ .


-  $Y_{gd} = j\omega C_{gd}$  is admittance corresponding to  $C_{gd}$ .

→ The equivalent circuit to find the short circuit current from drain to source is shown in figure.

$$I = -g_m V_{gs} + \frac{V_i}{j\omega C_{gd}}$$

$$= j\omega C_{gd} V_i - g_m V_i$$
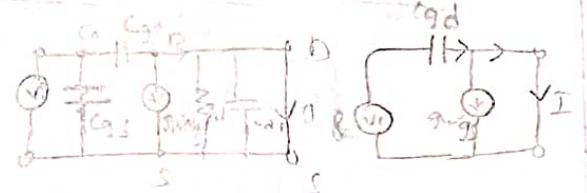
$$\boxed{I = V_i (j\omega C_{gd} - g_m)}$$



$$j\omega C_{gd} = \frac{1}{j2\pi f C_{gd}}$$

$$\therefore A_{vS} = \frac{V_O}{V_I} = \frac{IZ}{V_i} = \frac{I}{V_i Y}$$

$$\therefore A_V = \frac{g_m C_{gd} - g_m}{Y_L + g_d + Y_{ds} + Y_{gd}}$$

$$A_V = \frac{Y_{gd} - g_m}{Y_L + g_d + Y_{ds} + Y_{gd}}$$

- At low frequencies, FET internal capacitances can be neglected and hence,  $Y_{ds} = Y_{gd} = 0$


$$A_V = \frac{-g_m}{Y_L + g_d}$$

$$= \frac{-g_m}{\frac{1}{Z_L} + \frac{1}{g_d}}$$

$$A_V = \frac{-g_m Z_L g_d}{g_d + Z_L}$$

$$A_V = -g_m Z_L' \quad [Z_L' = Z_L || g_d]$$

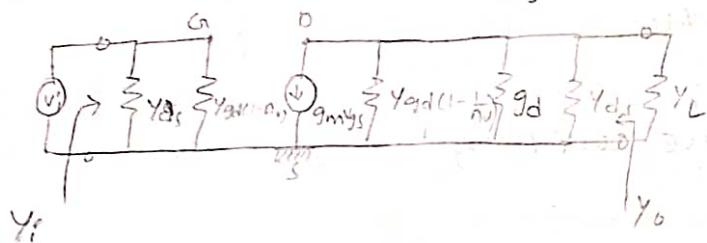
Input Admittance :- Apply Miller's theorem to the circuit, where capacitances are replaced by equivalent admittances. Therefore,




$$\Rightarrow Y_i = Y_{ds} + Y_{gd}(1 - A_V)$$

$$\Rightarrow Y_o = Y_{ds} + g_d + Y_{gd}(1 - \frac{1}{A_V}), \quad V_i = 0$$

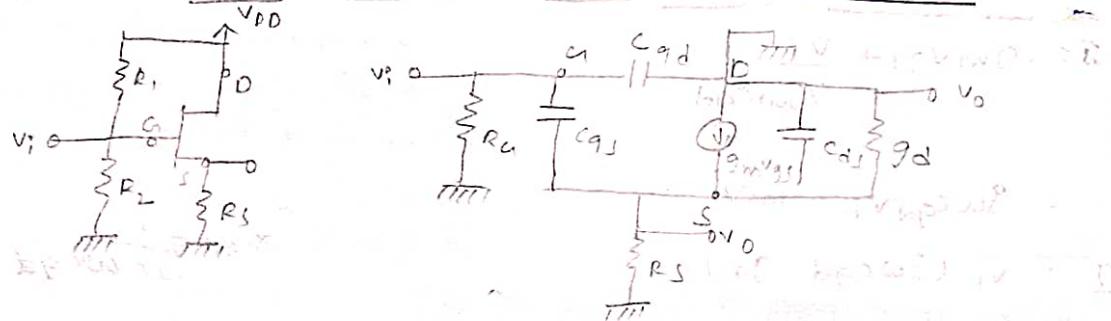\* COMMON DRAIN AMPLIFIER AT HIGH FREQUENCIES:



Common Drain Circuit from CSA circuit.

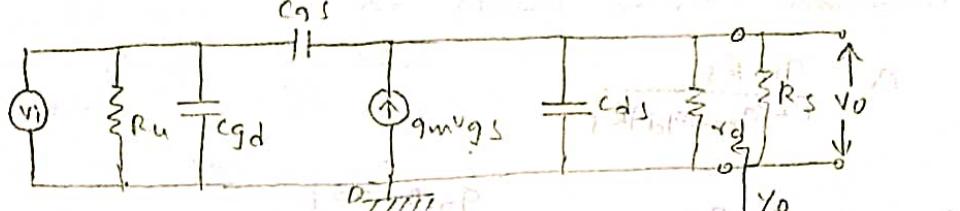

→ The o/p admittance with i/p voltage set to zero is


$$\Rightarrow I_1 = \frac{V_i}{R_d} + \frac{V_i}{Y_{jwcds}} - g_m V_{gs} - \frac{V_{gs}}{Y_{jwcds}} - \frac{V_o}{Y_o}$$
$$I_1 = \frac{V_i}{R_d} + V_i(Y_{jwcds}) + g_m V_i + V_i Y_{gs} + \frac{V_o}{Y_o}$$

$$\frac{I_1}{V_i} = g_d + Y_{jwcds} + g_m + Y_{gs}$$

$$\therefore Y_o = g_d + Y_{jwcds} + g_m + Y_{gs}$$

→ To calculate  $V_o$ , use Norton's theorem, i.e., the o/p voltage  $V_o$  is the product of short circuit current and the impedance b/w the terminals source and ground.
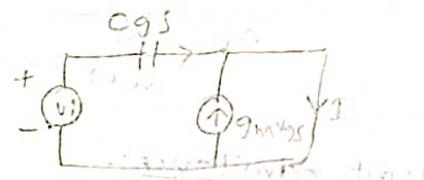
$$\Rightarrow I = g_m V_{gs} + \frac{V_i}{Y_{jwcds}}$$



$$I = g_m V_{gs} + V_i Y_{gs}$$

$$= V_i Y_{gs} + g_m V_i$$

(V\_{gs} = V\_i)

$$I = V_i(Y_{gs} + g_m)$$

$$\Rightarrow V_o = \frac{I}{Y_o + \frac{1}{R_s}}$$

$$V_o = \frac{V_i(Y_{gs} + g_m)}{Y_o + \frac{1}{R_s}}$$

$$\frac{V_o}{V_i} = \frac{Y_{gs} + g_m}{Y_o + \frac{1}{R_s}}$$

$$A_v = \frac{Y_{gs} + g_m}{\frac{1}{R_s} + g_d + Y_{jwcds} + g_m + Y_{gs}}$$

$$A_v = \frac{R_s(Y_{gs} + g_m)}{1 + R_s(g_d + Y_{jwcds} + g_m + Y_{gs})}$$

At low frequencies,  $Y_{gs} = Y_{jwcds} = 0$

$$\therefore AV = \frac{g_m R_s}{(g_m + g_d) R_s}$$

$$= \frac{g_m R_s}{(g_m + g_d) R_s} \quad [g_m R_s \gg 1]$$


$$AV = \frac{g_m R_s}{g_m R_s + g_d R_s}$$

$$AV = \boxed{\frac{g_m}{g_m + g_d}}$$

$$= \frac{g_m}{g_m + \frac{1}{g_d}}$$

$$AV = \boxed{\frac{u}{u+1}}$$

Input Admittance:

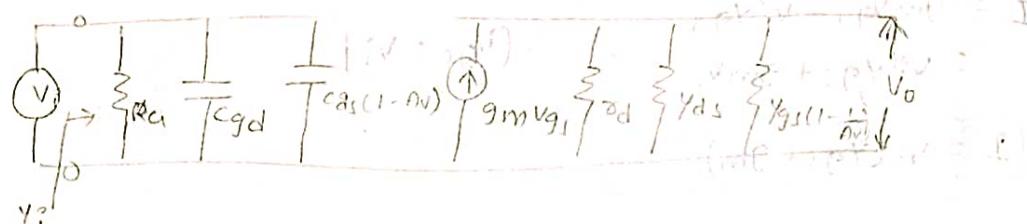

$$\rightarrow Y_i = \frac{1}{R_a} + Y_{gd} + Y_{ds}(1-AV)$$

### \* MULTI STAGE AMPLIFIER:

In practical the o/p of a single stage amplifier is insufficient though they are power and voltage amplifier. Hence they are replaced by multi stage amplifiers.

In multi stage amplifiers, the o/p of first stage amplifier connected to i/p of next stage using a coupling device. This coupling device can be a capacitor or a transformer. This process of joining two amplifiers using a coupling device can be called as "cascading".

The following figure shows the two-stage amplifier connected in cascade.



voltage gain of  
the individual stages.

$$Av = A_1 \times A_2 = \frac{V_2}{V_1} \times \frac{V_O}{V_2} = \frac{V_O}{V_1}$$

where,  $Av$  = Overall gain

$A_1$  = Voltage gain of 1st stage

$A_2$  = Voltage gain of 2nd stage

The purpose of a coupling device are:

- To transfer the AC from output of one stage to the i/p of next stage.
- To block the DC to pass from o/p, which means to isolate the DC conditions.

Types of coupling: There are 3 basic methods of coupling,

### ① Resistance-capacitance coupling

This is the mostly used method of coupling, formed using simple resistor - capacitor combination. The capacitor which allows AC and blocks DC, is the main coupling element used here. The coupling capacitor connects the o/p of one stage to i/p of next stage while blocking the DC components from O/P bias voltages.

### ② Transformer coupling

The coupling method that uses a transformer as coupling device is called as "Transformer coupling".

There is no capacitor used in this method of coupling because transformer itself conveys AC component directly to the base of second stage. The secondary winding of the transformer provides a base return path and hence there is no need of base resistance. This coupling is famous for its efficiency and high current matching & is mostly used.

### ③ Direct coupling

If the previous amplifier stage is connected to the next stage directly, is called as "direct coupling".

The individual stage bias conditions are so designed that the stages can be directly connected with DC insulation.

The direct method is mostly used when the load is connected in series, with the o/p terminal of the active circuit element. ex: Head phones, loud speakers etc.

### → Role of capacitors in Amplifiers

Other than coupling purpose, there are other purposes for which few capacitors are especially employed in amplifiers

→ Input capacitor  $C_{in}$ : It is present at the initial stage of amplifier, couples AC signal to the base of the transistor. If it is not present, the signal source is directly parallel to resistor  $R_2$  and the bias voltage of transistor will be changed.

→  $C_{in}$  allows AC to flow into i/p circuit, without affecting biasing

conditions

→ Emitter Bypass Capacitor  $C_e$ : It is connected in parallel with emitter resistor. It offers a low reactance path to ground with AC signal. In the absence of this capacitor, the voltage developed across  $R_E$  will feedback to input thus decreasing the o/p voltage.

→ Coupling Capacitor  $C_C$ : It connects the two stages and DC interface b/w two stages and controls operating point from shifting. In the absence of coupling capacitor  $R_C$  will come in parallel with resistance  $R_E$  of next stage and changing biasing condition.

### \*Amplifier Consideration!

→ CC Amplifier: -It has unity voltage gain.

-Not suitable for intermediate gains.

→ CB Amplifier: Its voltage gain is less than unity.


-Hence not suitable for cascading.

→ CE Amplifier: -Its voltage gain is greater than unity.


-Voltage is further increased by cascading.

-The characteristics of CE amplifier is such that this configuration is very suitable for cascading in amplifier circuits. Hence most of the amplifier circuits use CE configuration.


### → Two stage CE-CE cascade Amplifier:

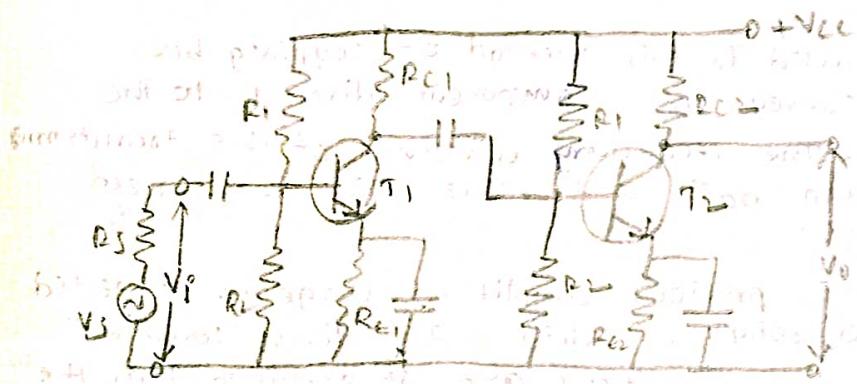


→ h-parameter equivalent circuit:

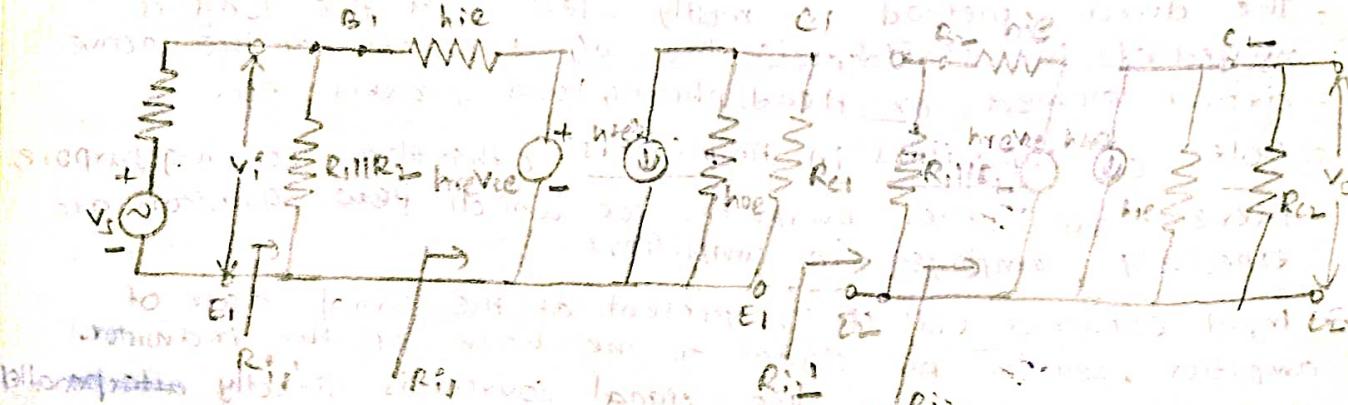

## → CASCODE AMPLIFIER:

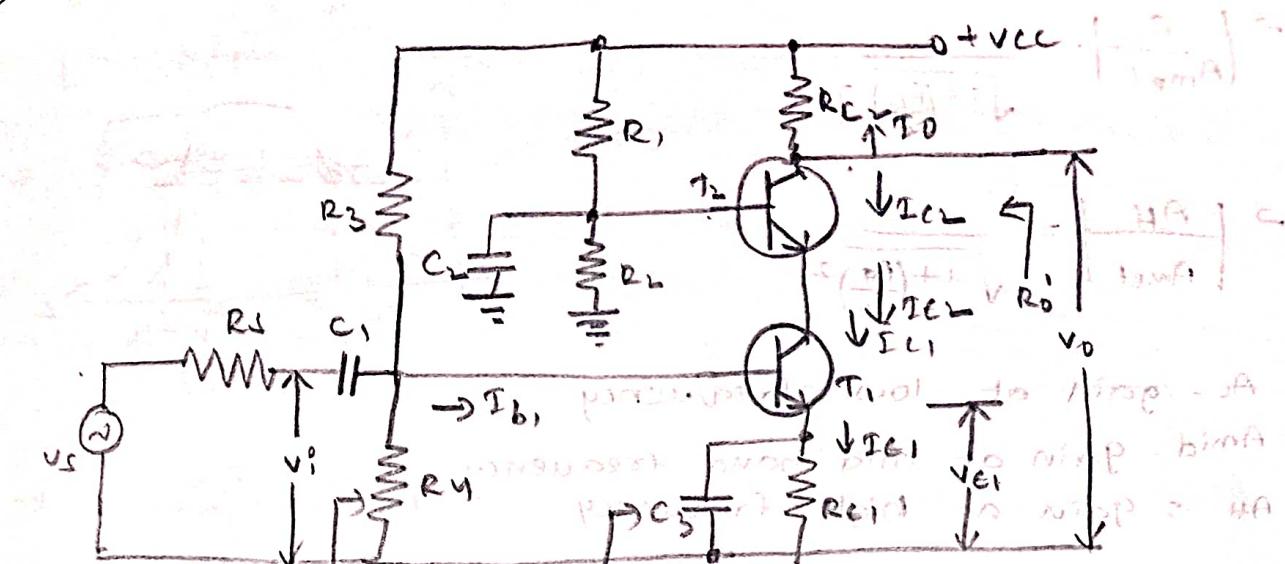

AC Equivalent circuit:

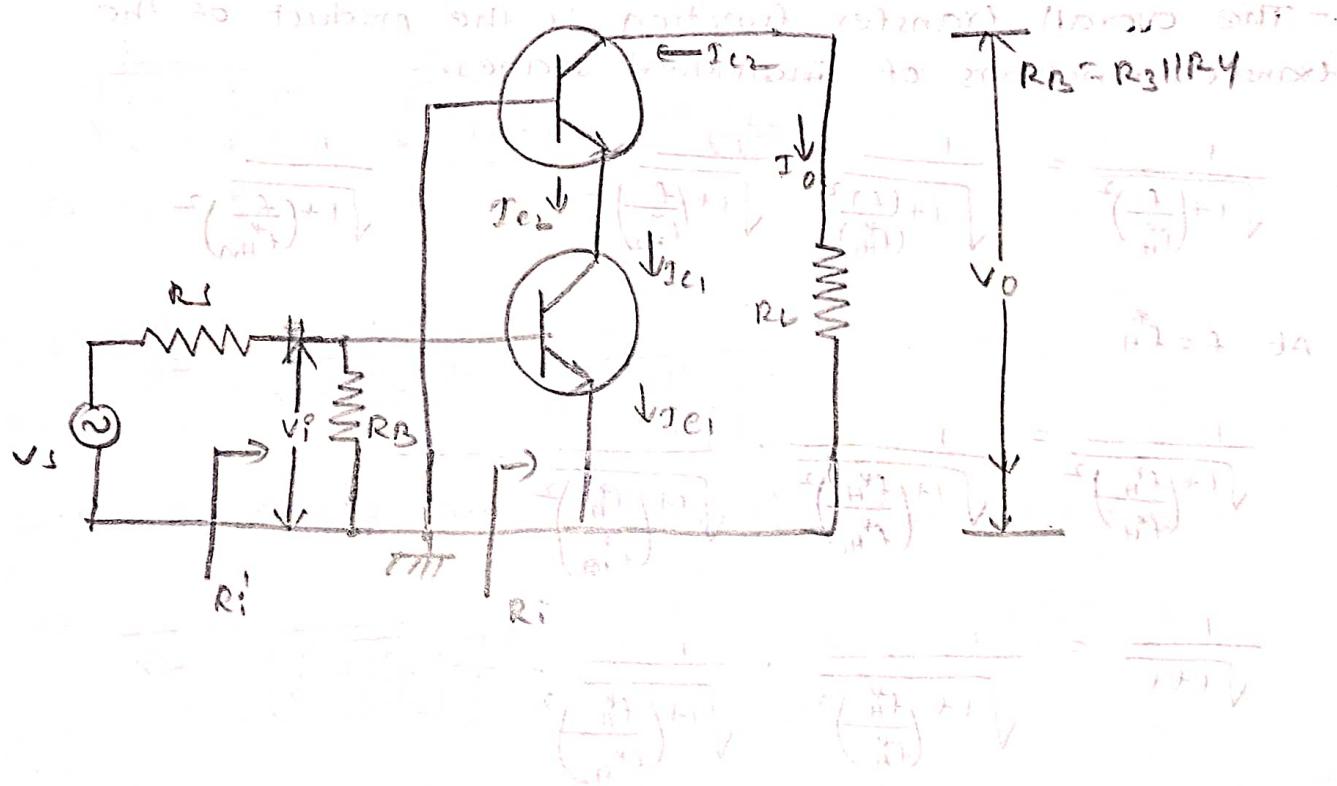

$$A_{v1} = \frac{V_{o1}}{V_{i1}} = -\frac{R_L}{(R_1 + R_{11})}$$

→  $A_{v1} = -\frac{R_L}{(R_1 + R_{11})}$


$$A_{v2} = \frac{V_{o2}}{V_{i2}} = -\frac{R_L}{(R_2 + R_{22})}$$



## Bandwidth of N-stage Amplifier

$$\Rightarrow \left| \frac{A_L}{A_{\text{mid}}} \right| = \frac{1}{\sqrt{1 + \left( \frac{f}{f_H} \right)^2}}$$

$$\Rightarrow \left| \frac{A_H}{A_{\text{mid}}} \right| = \frac{1}{\sqrt{1 + \left( \frac{f_H}{f_L} \right)^2}}$$

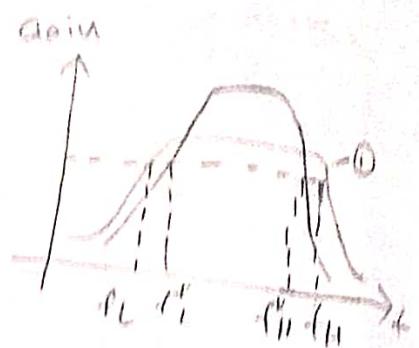

- All gain at low frequency
- Amid: gain at mid band frequency
- All = gain at high frequency

Consider a cascade amplifier with n stages having higher 3dB frequencies of  $f_{1H}, f_{2H}, \dots, f_{nH}$  respectively.

- Let  $f_H^*$  be the higher 3dB frequency of the cascade multi-stage amplifier.
- The overall transfer function is the product of the transfer functions of individual stages.

$$\frac{1}{\sqrt{1 + \left( \frac{f}{f_H^*} \right)^2}} = \frac{1}{\sqrt{1 + \left( \frac{f}{f_{1H}} \right)^2}} \cdot \frac{1}{\sqrt{1 + \left( \frac{f}{f_{2H}} \right)^2}} \cdot \dots \cdot \frac{1}{\sqrt{1 + \left( \frac{f}{f_{nH}} \right)^2}}$$

At  $f = f_H^*$

$$\frac{1}{\sqrt{1 + 1}} = \frac{1}{\sqrt{1 + \left( \frac{f_{1H}}{f_H^*} \right)^2}} \cdot \frac{1}{\sqrt{1 + \left( \frac{f_{2H}}{f_H^*} \right)^2}} \cdot \dots \cdot \frac{1}{\sqrt{1 + \left( \frac{f_{nH}}{f_H^*} \right)^2}}$$

$$\frac{1}{\sqrt{2}} = \frac{1}{\sqrt{1 + \left( \frac{f_{1H}}{f_H^*} \right)^2}} \cdot \frac{1}{\sqrt{1 + \left( \frac{f_{2H}}{f_H^*} \right)^2}} \cdot \dots \cdot \frac{1}{\sqrt{1 + \left( \frac{f_{nH}}{f_H^*} \right)^2}}$$

$$\frac{1}{\sqrt{2}} = \frac{1}{\sqrt{1 + \left( \frac{f_{1H}}{f_{1H}} \right)^2}} \cdot \frac{1}{\sqrt{1 + \left( \frac{f_{2H}}{f_{1H}} \right)^2}} \cdot \dots \cdot \frac{1}{\sqrt{1 + \left( \frac{f_{nH}}{f_{1H}} \right)^2}}$$

- If all stages are equal;

$$f_{1H} = f_{2H} = \dots = f_H$$

$$\therefore \left[ \frac{1}{\sqrt{1 + \left( \frac{f_{1H}}{f_{1H}} \right)^2}} \right]^n = \frac{1}{\sqrt{2}}$$

$$\rightarrow \left[ \sqrt{1 + \left( \frac{f_H^*}{f_H} \right)^2} \right]^n \sqrt{2}$$

$$\rightarrow \sqrt{1 + \left( \frac{f_H^*}{f_H} \right)^2} = (\sqrt{2})^{Y_H}$$

$$\rightarrow 1 + \left( \frac{f_H^*}{f_H} \right)^2 = 2^{Y_H}$$

$$\rightarrow \left( \frac{f_H^*}{f_H} \right)^2 = 2^{Y_H} - 1$$

$$f_H^* = f_H \sqrt{(2^{Y_H} - 1)}$$

$\rightarrow$  similarly,

$$\frac{1}{\sqrt{1 + \left( \frac{f_L^*}{f_L} \right)^2}} = \frac{1}{\sqrt{1 + \left( \frac{f_{L1}^*}{f_L} \right)^2}} \cdot \frac{1}{\sqrt{1 + \left( \frac{f_{L2}^*}{f_L} \right)^2}} \cdots \frac{1}{\sqrt{1 + \left( \frac{f_{Lm}^*}{f_L} \right)^2}}$$

$$\text{At } f = f_L^*$$

$$\Rightarrow \frac{1}{\sqrt{2}} = \frac{1}{\sqrt{1 + \left( \frac{f_{L1}^*}{f_L^*} \right)^2}} \cdot \frac{1}{\sqrt{1 + \left( \frac{f_{L2}^*}{f_L^*} \right)^2}} \cdots \frac{1}{\sqrt{1 + \left( \frac{f_{Lm}^*}{f_L^*} \right)^2}}$$

- If all stages are similar,  $f_{L1}^* = f_{L2}^* = \dots = f_L^*$

$$\Rightarrow \frac{1}{\sqrt{2}} = \left[ \frac{1}{\sqrt{1 + \left( \frac{f_L}{f_L^*} \right)^2}} \right]^n$$

$$\rightarrow \sqrt{2} = \left[ \sqrt{1 + \left( \frac{f_L}{f_L^*} \right)^2} \right]^n$$

$$\rightarrow 1 + \left( \frac{f_L}{f_L^*} \right)^2 = (2)^{Y_L}$$

$$\therefore \frac{f_L}{f_L^*} = \sqrt{2^{Y_L} - 1}$$

$$f_L^* = f_L / \sqrt{2^{Y_L} - 1}$$

$$\Rightarrow A_V = A_{V1} \cdot A_{V2} \cdot \dots \cdot A_{Vm}$$

$$\rightarrow \sqrt{1 + \left(\frac{f_C^*}{f}\right)^2} = \sqrt{1 + \left(\frac{f_{L1}}{f}\right)^2} \cdot \sqrt{1 + \left(\frac{f_{L2}}{f}\right)^2} \dots$$

$$\rightarrow \sqrt{1 + \left(\frac{f_C^*}{f}\right)^2} = \sqrt{1 + \left(\frac{f_{L1}}{f}\right)^2} \cdot \sqrt{1 + \left(\frac{f_{L2}}{f}\right)^2} \dots$$


$$\rightarrow 1 + \left(\frac{f_C^*}{f}\right)^2 = \left[1 + \left(\frac{f_{L1}}{f}\right)^2\right] \left[1 + \left(\frac{f_{L2}}{f}\right)^2\right] \dots$$

$$1 + \left(\frac{f_C^*}{f}\right)^2 = 1 + \left(\frac{f_{L1}}{f}\right)^2 + \left(\frac{f_{L2}}{f}\right)^2 + \left(\frac{f_{L1} \cdot f_{L2}}{f^2}\right)^2 \dots$$

$$f_C^* = \sqrt{(f_{L1})^2 + (f_{L2})^2 + \dots}$$

$$\text{Hence, } f_H = \sqrt{\frac{1}{f_{H1}^2} + \frac{1}{f_{H2}^2} + \dots}$$

### DARLINGTON AMPLIFIER:

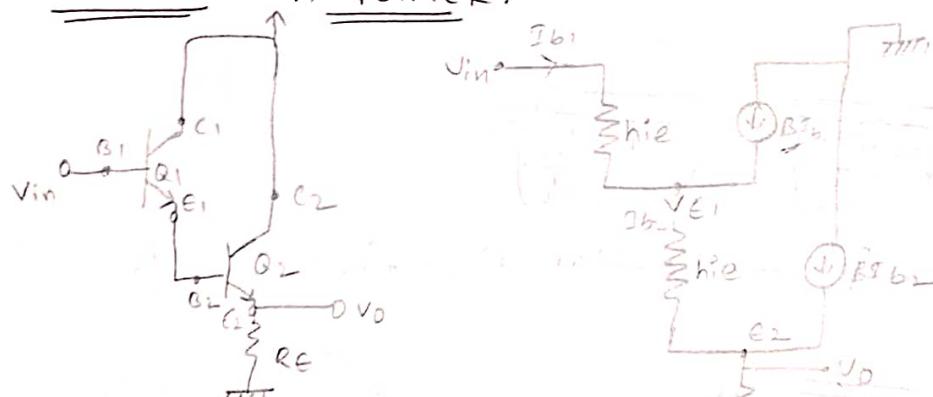

①

$$\rightarrow \text{Current Gain, } A_I = \frac{I_O}{I_{in}}$$

$$- I_{in} = I_{b1}$$

$$\rightarrow I_O = I_{b2} + \beta I_{b2} = I_{b2}(1+\beta)$$

$$\text{where, } I_{b2} = I_{b1}(1+\beta)$$

$$\therefore I_O = I_{b1}(1+\beta)^2$$

$$A_I = \frac{I_O}{I_{b1}} = (1+\beta)^2 \approx \beta^2$$

Equivalent circuit using  
Approximate analysis of transistors

$$\textcircled{2} \quad R_{in} = \frac{V_{in}}{I_{in}}$$

$$\rightarrow I_{in} = I_{b1}$$

$$\rightarrow V_{in} = h_{ie} I_{b1} + h_{ie} \underline{I_{b2}} + I_{ORE}$$

$$V_{in} = h_{ie} I_{b1} + h_{ie} \cdot I_{b1}(1+B) + I_{b2}(1+B)^2 R_E$$

$$\frac{V_{in}}{I_{b1}} = h_{ie}^2(1+B)h_{ie} + (1+B)^2 R_E$$

$$\therefore \boxed{R_{in} = h_{ie} + (1+B)h_{ie} + (1+B)^2 R_E}$$

which gives exact value of current gain.

and  $\boxed{R_{in} \approx R_E}$  ( $\because h_{ie}$  is very very low)

$$\textcircled{3} \quad \text{Voltage gain, } A_V = \frac{V_O}{V_{in}}$$

$$\rightarrow V_O = I_{ORE} = I_{b1}(1+B)^2 R_E$$

$$\rightarrow A_V = \frac{V_O}{V_{in}}$$

$$= \frac{I_{b1}(1+B)^2 R_E}{I_{b1} [h_{ie} + (1+B)h_{ie} + (1+B)^2 R_E]}$$

neglected

$$= \frac{(1+B)^2 R_E}{(1+B)^2 R_E}$$

$$\boxed{A_V = 1}$$

- This amplifier is having very high input impedance.
- Unity voltage gain, very high current gain (super  $B_\beta$ -amplifier).


- It is used as a voltage buffer.

$$\rightarrow R_{in} = B^2 R_E$$

$$R_X = R_1 \parallel R_2$$

$$\therefore R_{in} = R_X \parallel R_{in}$$


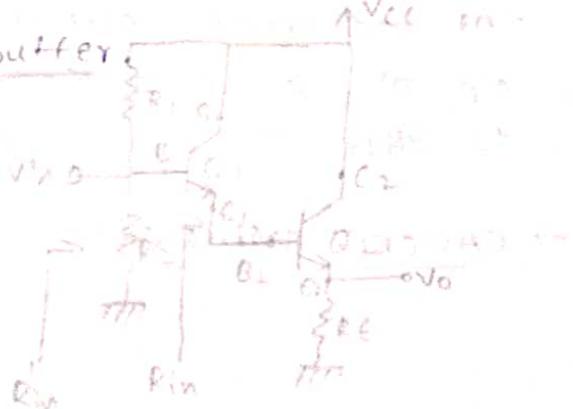
$$\boxed{R_{in} = R_X} \quad (\because R_{in} \text{ very high})$$



The biasing resistance Reduce the i/p resistance of the amplifier.

### → BOOT STRAP BIASING


#### AC ANALYSIS

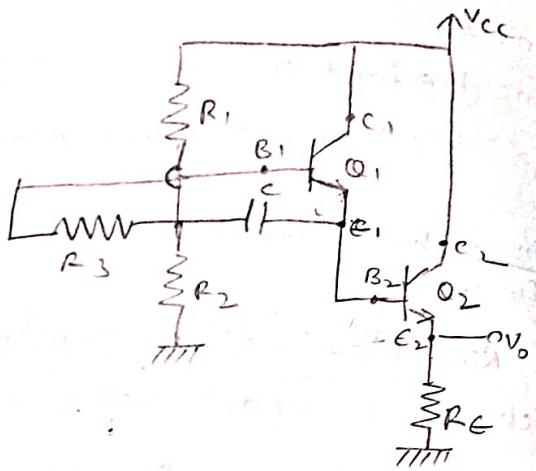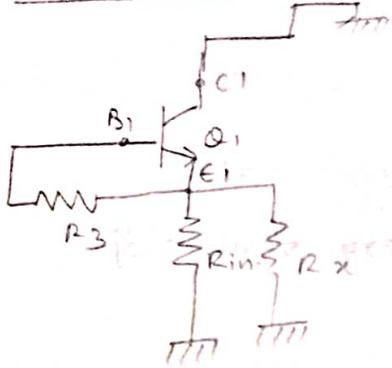

— By miller's theorem,

$$R_{mi} = \frac{R_3}{1 - A_V} = \frac{R_3}{1 - 1} = \frac{R_3}{0} \infty$$
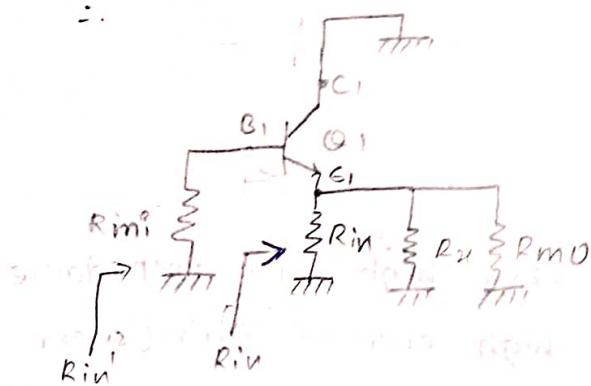
$$R_{mo} = \frac{R_3}{1 - \frac{1}{A_V}}$$




$$R'_{in} = R_{in} \| R_{mi}$$

$$R'_{in} = R^{\infty}_{in}$$

[ $\because R_{mi} = \infty$ ]

— Boot strap circuit is one, where the part of the o/p of an amplifier stage is applied to the i/p so as to alter the i/p impedance of the amplifier.

### → CASCODE AMPLIFIER

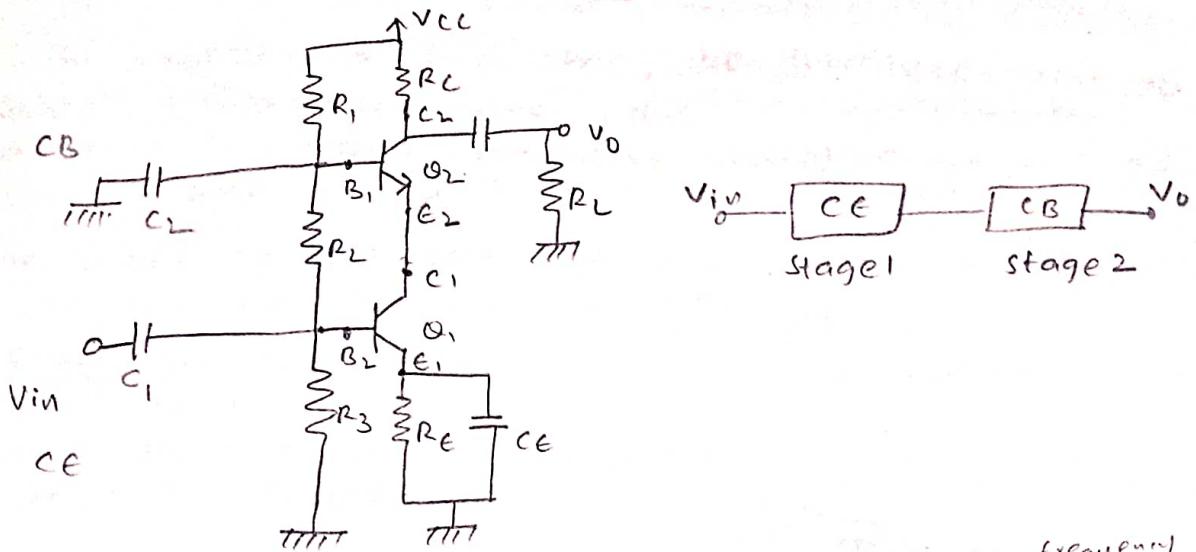


- Transistors in CASCODE amplifiers are linked in parallel.  
 The transistors of CASCADE amplifiers are linked in chain. which the o/p of 1<sup>st</sup> transistor serving as i/p of 2<sup>nd</sup> transistor.

- The transistors in CASCODE amplifier are stacked one on top of the other.
- It has large bandwidth, known as "wide amplifier".
- It is also known CE-CB amplifier.
- It is used as video frequency amplifier. If p resistance is small, current gain is ' $-B$ ' and voltage gain is

$$A_v = \frac{-BRL}{h_{ie}}$$

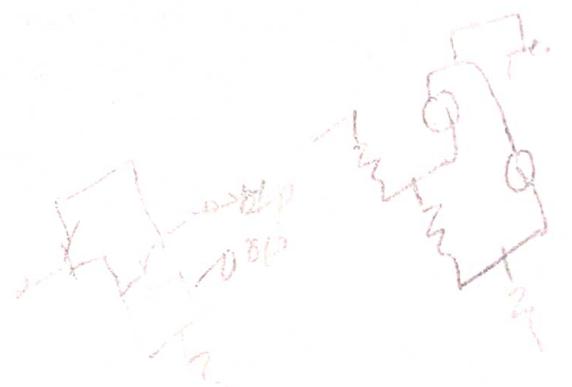- Overall transconductance of CASCODE amplifier is  $\gamma_m$ .




05/01/23

### 3. FEED BACK AMPLIFIERS

In amplifiers, a hum may be introduced due to several temperature changes, due to non-linearity characteristics and parameter variation. We will not get faithful amplification in the midband frequency range.

In order to overcome the above drawbacks we will go for the feedback amplifiers.

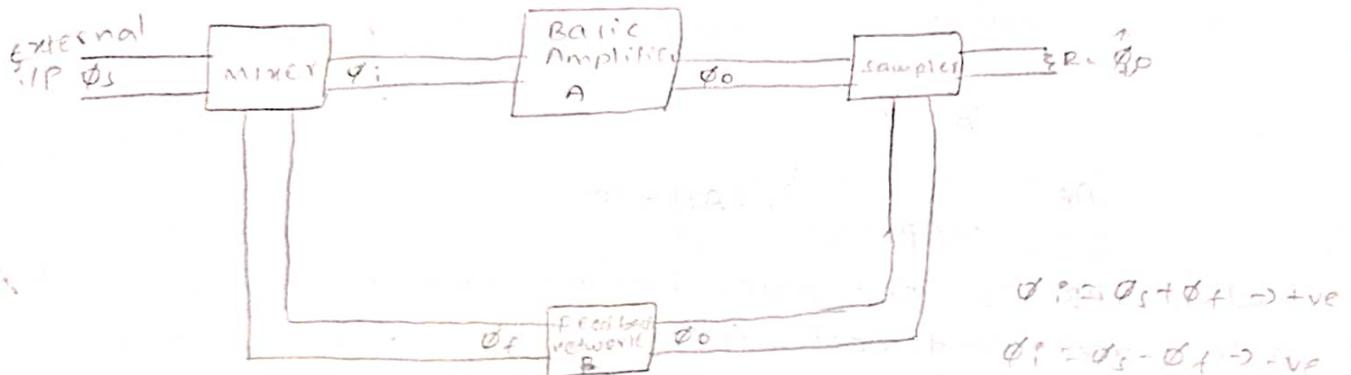Feed Back: The process of injecting a fraction of o/p signal back to the i/p is known as feedback. A block diagram of an amplifier with feedback is shown in Figure.



- $A$  = open load gain of amplifier  $\frac{v_o}{v_i}$
- $B$  = Feed back factor  $\frac{v_{fb}}{v_o}$
- $A_f$  = Gain of feedback amplifier  $\frac{v_{fb}}{v_i}$
- The o/p quantity ( $v_i/v_o$ ) is sampled by a suitable sampler, which is of two types. Namely, voltage sampler and current sampler, and fed to the feedback network. The o/p of feedback network which is a fraction of o/p signal is combined with external source signal ' $v_i$ ' through a mixer and fed to basic amplifier. Mixer is also known as 'comparator' is of two types. Namely, series mixer and shunt mixer.
- There are two types of feedback. One is +ve feedback and -ve feedback.

#### → Positive Feed Back:

- If ' $\phi_f$ ' is in phase with signal ( $\phi_i$ ) is  $0^\circ$  i.e., ' $\phi_f = \phi_f + \phi_i$ ', the net effect of the feedback will increase the i/p signal given to amplifier hence o/p increases. This type of feedback is called +ve

feedback (or) regenerative feedback,

### Chain of the Amplifier with +ve feed back.


$$A_f = \frac{\phi_o}{\phi_s}$$

$$= \frac{\phi_o}{\phi_i - \phi_f}$$

$$= \frac{1}{\frac{\phi_p}{\phi_o} - \frac{\phi_f}{\phi_o}}$$

$$= \frac{1}{\frac{1}{A} - \beta}$$
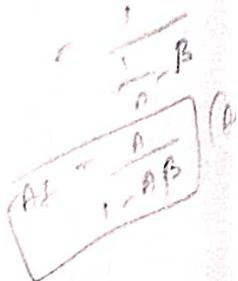
$$\boxed{A_f = \frac{A}{1 - AB}}, (A_f) > 1A$$



where  $AB$  is loop gain, i.e., the product of the open gain and feed back factor.

- If  $|AB|=1$ , then  $A_f = \infty$

- The gain of the amplifier with +ve feedback is inf and the amplifier gives an AC output without AC signal. Thus, the amplifier acts an oscillator. Gain will not depend on  $R_f$ .

- The +ve feedback increases gain, instability, distortion and with noise. Decreases the 'Bandwidth'.

→ Negative Feedback: If the feedback signal  $\phi_f$  is out phase with the i/p signal  $\phi_s$ , then  $(\phi_p = \phi_s - \phi_f)$ . So if voltage apply to the basic amplifier is decreased and correspondingly the o/p is decreased. Therefore the voltage gain is reduced. This type of feedback is known as -ve feedback (or) degenerative feedback.

### Chain of the amplifier with -ve feed back;

$$A_f = \frac{\phi_o}{\phi_s}$$

$$= \frac{\phi_o}{\phi_i + \phi_f}$$

$$= \frac{\phi_o}{\phi_i + \phi_f}$$

$$= \frac{1}{\frac{\phi_i}{\phi_o} + \frac{\phi_f}{\phi_o}}$$

$$= \frac{1}{\frac{1}{A} + B}$$

$$Af = \frac{A}{1+AB}$$

$$|Af| < |A|$$


- If  $|AB| \gg 1$ , then  $A_f = \frac{1}{B}$ .

where  $iB$  is feedback ratio/feedback factor that gain depends less on the characteristics of the transistor.

That gain may be made to depend entirely on the feedback network. If the feedback network contains only stable passive elements, the gain of the amplifier using -ve feedback is stable.
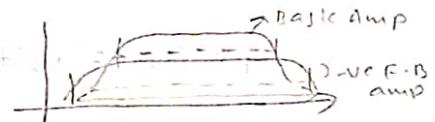
### Advantages of -ve feedback:

- Increases the stability.
- Increases the Bandwidth, less amplitude and less harmonic distortion.
- Less frequency and phase distortion.
- Less noise
- S/p and o/p resistances can be modified as per requirement.



### Disadvantage

- Voltage gain decreases.

### Band width of -ve feedback amplifiers:-

$$\text{w.r.t. A}_f \quad Af = \frac{A}{1+AB}$$

$$Af_{\text{Low}} = \frac{A_{\text{Low}}}{1+A_{\text{Low}}B}$$

$$Af_{\text{Mid}} = \frac{A_{\text{Mid}}}{1+A_{\text{Mid}}B}$$

$$Af_{\text{High}} = \frac{A_{\text{High}}}{1+A_{\text{High}}B}$$

$$\text{and } A_{\text{Low}} = \frac{\text{Amid}}{1 - \beta \left( \frac{f_L}{f} \right)}$$

$$\begin{aligned} A_{\text{Low}} &= \frac{A_{\text{Low}}}{1 + \text{Amid}_B} \\ &= \frac{(1 - \beta \left( \frac{f_L}{f} \right)) \text{Amid}}{1 + (1 - \beta \left( \frac{f_L}{f} \right)) \text{Amid}_B} \end{aligned}$$

$$\begin{aligned} \text{Divide by } 1 + \text{Amid}_B \\ \text{and } A_{\text{Low}} = \frac{\text{Amid}}{1 - \beta \left( \frac{f_L}{f} \right) - \text{Amid}_B} \\ \text{Divide by } 1 + \text{Amid}_B \\ \text{and } A_{\text{Low}} = \frac{\text{Amid}}{1 + \text{Amid}_B - \beta \left( \frac{f_L}{f} \right)} \end{aligned}$$

Divide by with  $1 + \text{Amid}_B$

$$= \frac{\text{Amid} / (1 + \text{Amid}_B)}{1 - \beta \frac{f_L}{f} - \frac{1}{1 + \text{Amid}_B}}$$

$$A_{\text{Low}} = \boxed{\frac{\text{Amid}}{1 - \beta \frac{f_L}{f} - \frac{1}{1 + \text{Amid}_B}}}$$

$$A_{\text{Low}} = \boxed{\frac{f_L}{f} - \frac{1}{1 + \text{Amid}_B}}$$

similarly,

$$A_{\text{High}} = \frac{\text{Amid}}{1 + \beta \left( \frac{f_H}{f} \right)}$$

$$\begin{aligned} A_{\text{High}} &= \frac{A_{\text{High}}}{1 + \text{Amid}_H \cdot B} \\ &= \frac{\text{Amid}}{1 + \beta \left( \frac{f_H}{f} \right) + \text{Amid}_H \cdot B} \end{aligned}$$

$$= \frac{A_{mid}}{1+A_{mid}\cdot\beta}$$

$$= \frac{A_{mid}}{1 + \frac{\beta}{f_H} \cdot \frac{1}{A_{mid}(\beta) + 1}}$$

$$= \frac{A_{mid}}{1 + \frac{\beta}{f_H} \cdot \frac{1}{(1+A_{mid}\beta)}}$$

$$A_{fH} = \frac{A_{mid}}{1 + \frac{\beta}{f_H}}$$

$$f_{Hf} = f_H (1 + A_{mid}\beta)$$

$\rightarrow$  lower cut off frequency with feed back,  $f_{Lf} = \frac{f_L}{1 + A_{mid}\beta}$

$\therefore$  Lower cut off frequency with feed back is less than lower cut off frequency without feed back by a factor  $(1 + A_{mid}\beta)$ .

$\rightarrow$  Upper cut off frequency with feed back is,  $f_{Hf} = f_H (1 + A_{mid}\beta)$

- From the above equation it is clear that the upper cut off frequency with feed back is greater than upper cut off frequency without feedback by a factor  $(1 + A_{mid}\beta)$

$\therefore$  By introducing negative feedback, the bandwidth of the amplifier is  $BW = A_{Hf} - f_{Lf}$

$$BW = f_{Hf} - f_{Lf}$$

$\rightarrow$  Classification of negative feedback amplifiers:

Classification is based on i/p, o/p parameters:

i)  $I_{Ip} = V_o$ ;  $O_{Op} = V_o \Rightarrow \text{Chain AV} = \frac{V_o}{V_i}$



$\rightarrow$  Voltage Amplifier

ii) If i/p is current ( $I_i$ ) and output is current ( $I_o$ ), then the amplifier is known as current amplifier.

$$\text{Chain, } AI = \frac{I_o}{I_i}$$

iii) If i/p is voltage ( $V_i$ ) and output is current ( $I_o$ ), then the amplifier is called as "Trans conductance amplifier".

$$\text{Chain, } Am = \frac{I_o}{V_i}$$

iv) If i/p is current ( $I_i$ ) and o/p is voltage ( $V_o$ ), then the amplifier is called as "Trans resistance amplifier".

$$\text{Chain, } R_m = \frac{V_o}{I_i}$$

## VOLTAGE AMPLIFIER:

$$\rightarrow V_i = \frac{V_s \cdot R_i}{R_s + R_i}$$


① Ideal case,

$$V_i = V_s \quad (\because R_s = 0)$$

Practical case,

$$R_s \ll R_i$$

$$\boxed{V_i \approx V_s}$$

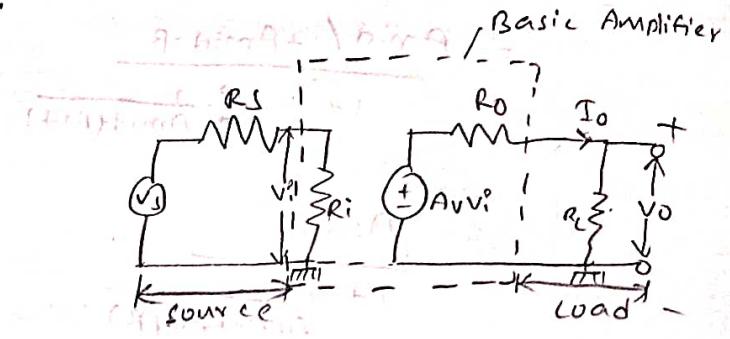

THEVENIN'S EQUIVALENT CIRCUIT OF VOLTAGE AMPLIFIER.

$$A_v = \frac{V_o}{V_i}$$

$$\rightarrow V_o = A_v V_i \cdot \frac{R_L}{R_o + R_L}$$

② Ideal case,

$$V_o = A_v V_i \quad (\because R_L = \infty)$$

② practical case,

$$V_o \approx A_v V_i \quad (\because R_L \gg R_o)$$

$$\boxed{V_o \approx A_v V_s}$$

\* Ideal Amplifier characteristics:

parameter

v.Amp

I. Amp

TC.Amp

TR.Amp

R<sub>i</sub>

~~High input resistance~~  $\Rightarrow$  ~~Low output resistance~~

~~High output resistance~~

R<sub>o</sub>

0

0

0

Parameter  
characteristic

$$V_o = A_v V_s$$

$$I_o = A_i I_s$$

$$V_o = R_m I_s$$

\* CURRENT AMPLIFIER:

→ Ideal case:

$$I_o = \frac{I_s R_o}{R_s + R_o}$$

R<sub>i</sub> = 0

$$\Rightarrow R_i I_o = I_s$$


R<sub>o</sub> = 0

$$\text{and } I_o = A_i I_s$$

→ Practical case:

$$① R_s \gg R_i$$

$$R_o \gg R_L$$

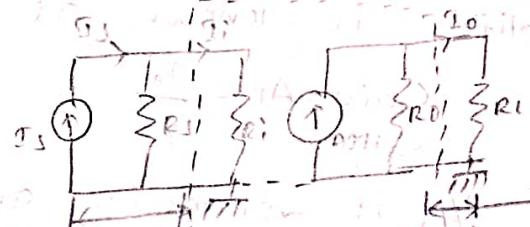

Norton's equivalent circuit for i/p & o/p of current amplifier

$$R_o \gg R_L$$

$$\rightarrow I_P^0 = I_S \cdot \frac{R_S}{R_S + R_I}$$

$$I_O = A_i I_i \cdot \frac{R_O}{R_O + R_L}$$

$$= I_S \cdot \frac{R_S}{R_S}$$

$$= A_i I_i \cdot \frac{R_O}{R_O}$$

$$[I_P^0 \approx I_S]$$

$$I_O \approx A_i I_i$$



$$[I_O \approx A_i I_S]$$

### \* TRANS CONDUCTANCE AMPLIFIER:

$\rightarrow$  Ideal,  $R_i = \infty$

$R_o = 0$
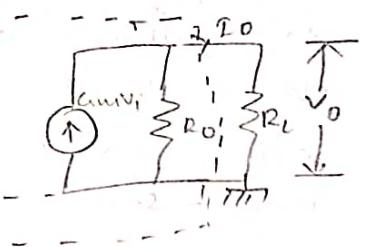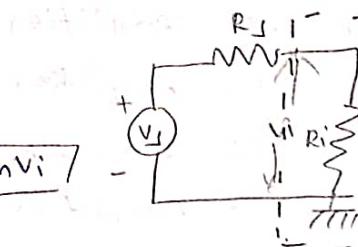
$$\therefore [V_i \approx V_s] ; [I_O = C_{mV} V_i]$$



$\rightarrow$  practical,

$$R_i \gg R_S$$

$$R_o \gg R_L$$

$$\therefore V_i = V_s \cdot \frac{R_i}{R_i + R_S}$$

$$I_O = C_{mV} V_i \cdot \frac{R_o}{R_o + R_L}$$

$$V_i = V_s \cdot \frac{R_i}{R_i}$$

$$= C_{mV} V_i \cdot \frac{R_o}{R_o}$$

$$[V_i \approx V_s]$$

$$I_O \approx C_{mV} V_s$$

$$[I_O \approx C_{mV} V_s]$$

### \* TRANS RESISTANCE AMPLIFIER:


$\rightarrow$  Ideal,  $R_i = 0$ ;  $R_o = 0$

$$\Rightarrow I_O = R_m I_i$$

$$\rightarrow I_P^0 = I_S$$

$\rightarrow$  Practical case

$$\rightarrow R_S \gg R_i$$

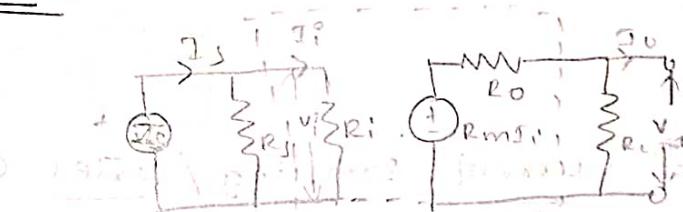

$$\rightarrow R_L \gg R_o$$

$$\therefore I_P^0 = I_S \cdot \frac{R_S}{R_S + R_i}$$

$$V_o = R_m I_i \cdot \frac{R_L}{R_o + R_L}$$

$$= I_S \cdot \frac{R_S}{R_S}$$

$$= R_m I_i$$

$$[I_P^0 \approx I_S]$$

$$[V_o \approx R_m I_S]$$

$$= R_m I_i$$

## TOPOLOGIES FOR -ve FEEDBACK AMPLIFIER:

→ Sampler, Mixer

① Voltage-series -ve FB Amplifier

② Voltage-shunt -ve FB Amplifier

③ Current-series -ve FB Amplifier

④ Current-shunt -ve FB Amplifier.

- ⑤ Nut key
- ⑥ Current shunt
- ⑦ Voltage shunt
- ⑧ Current series

→ Mixer, Sampler

⑨ Series-shunt -ve FB Amplifier

⑩ Shunt-shunt -ve FB Amplifier

⑪ Series-series -ve FB Amplifier

⑫ Shunt-series -ve FB Amplifier

→ Based on i/p & o/p parameters


i) Voltage-voltage -ve FB Amplifier

ii) Current-voltage -ve FB Amplifier


iii) Voltage-current -ve FB Amplifier

iv) Current-current -ve FB Amplifier


### ① Voltage Sampling / shunt Circuit:

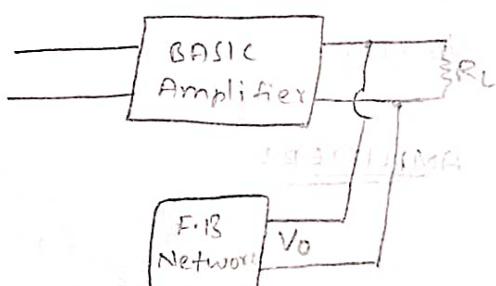


### ② Current Sampling / series Circuit:

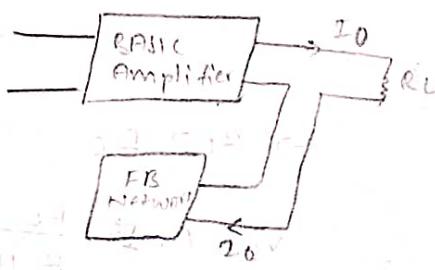

### ③ Voltage Mixing / series Mixing

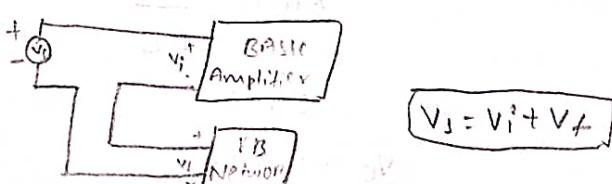


## ④ Current Mixing / Shunt Mixing:

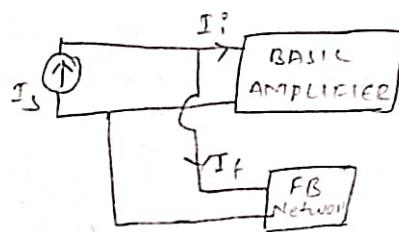

$$I_s = I_i + I_f$$

## \* Voltage-Series -ve Feed Back Amplifier:

### BLOCK DIAGRAM

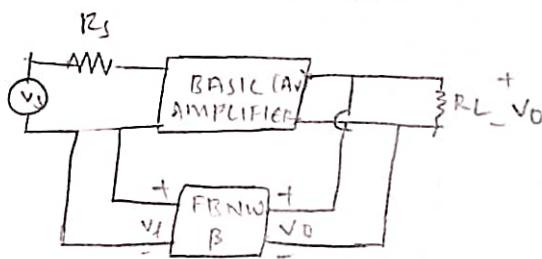

$$\rightarrow A_v = \frac{V_o}{V_i} ; \beta = \frac{V_f}{V_o}$$

$$\rightarrow \text{Voltage gain with FB}, A_v = \frac{V_o}{V_i}$$

$$\rightarrow A_{vf} = \frac{V_o}{V_i}$$

$$= \frac{V_o}{V_i(1 + BAV)}$$

$$V_s = V_i(1 + BAV)$$

$$A_{vf} = \frac{A_v}{1 + BAV} \quad \text{Gain with FB}$$

$$A_{vf} = \frac{A_v}{1 + A_v B}$$

## → Input Impedance with FB:

$$\rightarrow \text{Input resistance without FB}, R_i = \frac{V_i}{I_i}$$

$$\rightarrow \text{Input resistance with FB}, \Rightarrow V_i = R_i I_i$$


$$R_{if} = \frac{V_s}{I_s} = \frac{V_i}{I_i}$$

$$\rightarrow V_s = V_i(1 + A_v B)$$

$$V_s = I_i R_i (1 + A_v B)$$

$$R_{if} = \frac{V_s}{I_i} = R_i (1 + A_v B)$$

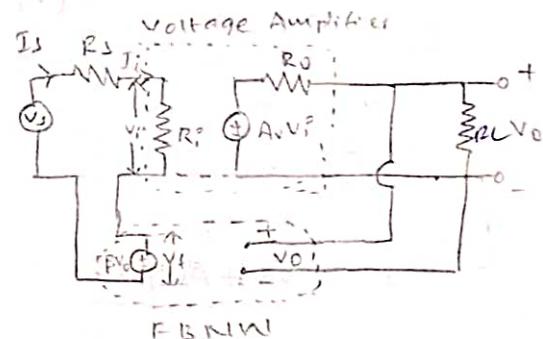Sampled-Voltage-Shunt  
Mixer-Voltage-Series



## Output impedance with FB

$$\rightarrow R_{of} = \frac{V_o}{I_o}$$

$$* I_o = \frac{V_o - A_v V_i}{R_o}$$

and  $V_i = V_s - V_f$

$$V_i + V_f = V_s$$

$$V_i + V_f = 0 \quad \therefore [V_s = 0]$$

$$V_i = -V_f$$

$$V_i = -\beta V_D$$

$$\therefore I_o = \frac{V_o + A_v \beta V_D}{R_o}$$

$$I_o = \frac{V_o (1 + A_v \beta)}{R_o}$$

$$\Rightarrow R_{of} = \frac{V_o}{I_o} = \frac{V_o}{\frac{V_o (1 + A_v \beta)}{R_o}} = \frac{R_o}{1 + A_v \beta}$$


$$R_{of} = \frac{R_o}{1 + A_v \beta}$$

Parameter	w/o FB	w. FB
Gain	$A_v$	$\frac{A_v}{1 + A_v \beta}$
I/p impedance	$R_i$	$R_i (1 + A_v \beta)$
O/p impedance	$R_o$	$\frac{R_o}{1 + A_v \beta}$


\* CURRENT SERIES V-VE FEED BACK AMPLIFIER:

→ Sampling - Current-series

→ Mixing - Voltage-series

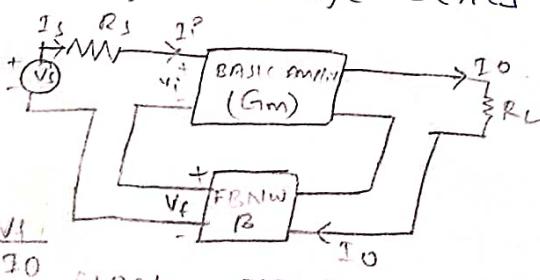

$$A_v = \frac{V_o}{V_i}$$

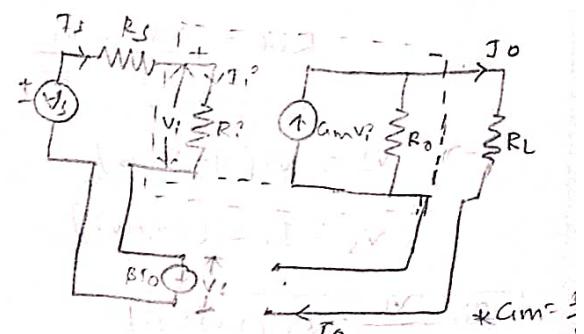

## \* Gain with Feed Back:

$$* A_{mfb} = \frac{I_o}{V_s}$$

$$\rightarrow V_s = V_i + V_f$$

$$= V_i + B I_o$$

$$= V_i + B A_m V_i$$

$$\boxed{V_s = V_i (1 + B A_m)}$$

$$* R_i = \frac{V_i}{I_i} \Rightarrow V_i = I_i R_i$$

$$* R_{if} = \frac{V_s}{I_i}$$

$$V_s = V_i (1 + A_m \beta)$$

$$\boxed{V_s = I_i R_i (1 + A_m \beta)}$$


$$A_{mfb} = \frac{I_o}{V_i (1 + B A_m)}$$

$$A_{mfb} = \frac{A_m}{1 + B A_m}$$

$$* R_{if} = \frac{I_i R_i (1 + A_m \beta)}{I_i}$$

$$R_{if} = R_i (1 + A_m \beta)$$

## \* Output Resistance:

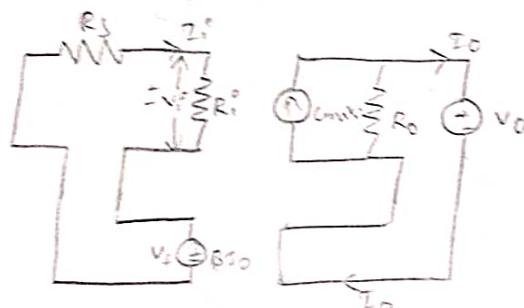

$$\rightarrow R_{of} = \frac{V_o}{I_o}$$

$$\rightarrow I_o = A_m V_i + \frac{V_o}{R_o}$$

$$I_o = -A_m B I_o + \frac{V_o}{R_o}$$

$$\boxed{V_o = I_o R_o (1 + A_m B)}$$

$$* V_s = V_i + V_f$$

$$V_i = -V_f \quad \because (V_s = 0)$$

$$V_i = -B I_o$$

$$\therefore R_{of} = \frac{V_o}{I_o}$$



$$\boxed{R_{of} = R_o (1 + A_m B)}$$

Parameter	w/o FB	w FB
Gain	$A_m$	$(A_m)/(1 + A_m B)$
I/P Resistance	$R_i$	$R_i (1 + A_m B)$
O/P resistance	$R_o$	$R_o (1 + A_m B)$

## \* CURRENT SHUNT - VG FEEDBACK AMPLIFIER:

\* Sampler - Current - ~~shunt~~ series

\* Mixer - Current - shunt

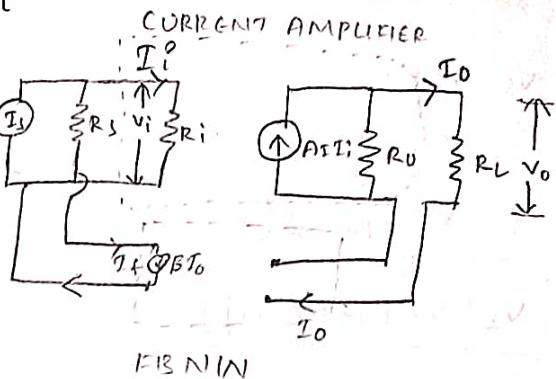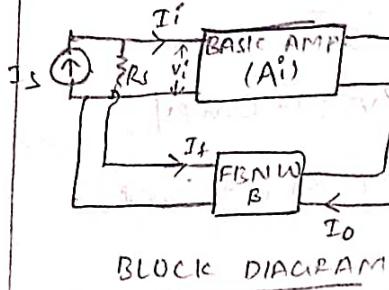

$$A_1 = \frac{I_o}{I_i} ; \beta = \frac{I_f}{I_o}$$

\* Gain with Feedback:

$$\rightarrow A_I = \frac{I_o}{I_i^p}$$

$$\rightarrow A_{If} = \frac{I_o}{I_s}$$

$$I_s = I_i^p + I_f$$

$$= I_i^p + B I_o$$

$$= I_i^p + B A_I I_i^p$$

$$[I_s = I_i^p (1 + A_I B)]$$

$$\therefore A_{If} = \frac{I_o}{I_i^p (1 + A_I B)}$$

$$A_{If} = \frac{A_I}{1 + A_I B}$$

$$I_s = I_i^p (1 + A_I B)$$

$$[I_s = \frac{V_i^p}{R_i} (1 + A_I B)]$$

$$\therefore R_{if} = \frac{V_i^p}{I_i^p}$$

$$\frac{V_i^p (1 + A_I B)}{R_i}$$

$$[R_{if} = \frac{R_i}{1 + A_I B}]$$

\* Output impedance with Feedback:

$$\rightarrow R_o = \frac{V_o}{I_o} \quad \text{① } I_s = 0 \text{ (O.C.)}$$

$$\rightarrow R_{of} = \frac{V_o}{I_o} \quad \text{② } R_L \text{ (O.C.)}$$

$$\rightarrow I_o = A_I I_i^p + \frac{V_o}{R_o} \quad \text{③ } V_o, I_o$$

$$I_o = -A_I B I_o + \frac{V_o}{R_o}$$


$$I_o (1 + A_I B) = \frac{V_o}{R_o}$$

$$I_o = \frac{V_o}{(R_o (1 + A_I B))}$$

$$I_s = I_i^p + I_f$$

$$I_i^p = -I_f$$

$$I_i^p = -B I_o$$


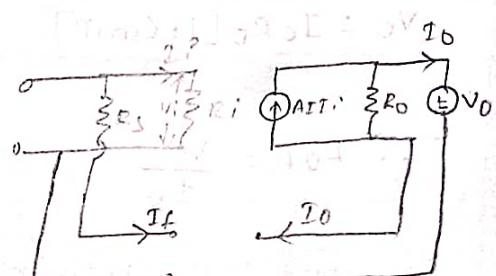


$$[R_{of} = R_o (1 + A_I B)]$$

Parameter	w/o FB	w FB
Gain	$A_I$	$A_I/(1+A_I\beta)$
Input resistance	$R_i$	$R_i/(1+A_I\beta)$
Output resistance	$R_o$	$R_o(1+A_I\beta)$
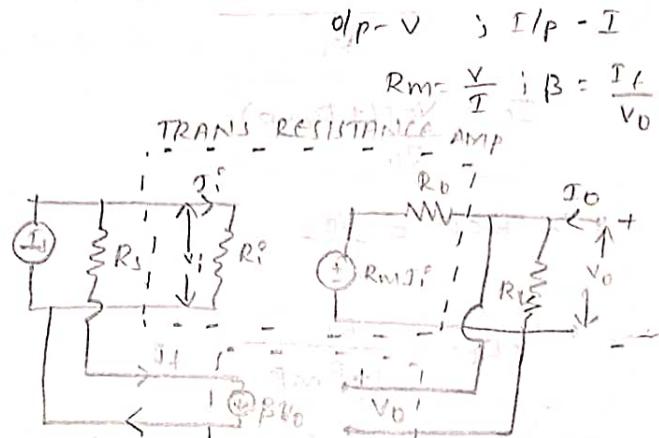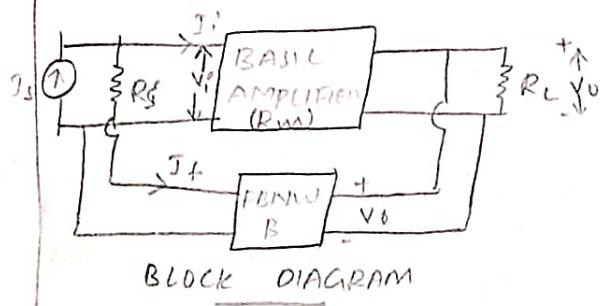
## \* VOLTAGE SHUNT-VEFB AMPLIFIER:

sampler-voltage-shunt  
Mixer-current-shunt



→ Gain with Feedback:

$$\rightarrow R_m = \frac{V_o}{I_i}$$

$$I_s = I_i + I_f$$

$$\rightarrow R_{mI} = \frac{V_o}{I_s} = \frac{V_o}{(A_m + 1)I_o} = I_o + \beta V_o$$

$$= I_o + \beta \cdot R_m I_o$$

$$I_o = \frac{V_o}{I_o(1+R_m\beta)} \quad (1 = I_o(1+R_m\beta))$$

$$R_{mI} = \frac{R_m}{1+R_m\beta}$$

→ Input Resistance with Feedback:

$$R_i = \frac{V_i}{I_i}$$

$$I_s = I_i(1+R_m\beta)$$

$$\rightarrow R_{if} = \frac{V_i}{I_s} = \frac{V_i}{I_i(1+R_m\beta)}$$

$$I_s = \frac{V_i}{R_i} (1+R_m\beta)$$

$$R_{if} = \frac{R_i}{1+R_m\beta}$$

→ Output resistance with FeedBack:

$$\rightarrow I_O = \frac{V_O - R_m I_i}{R_o}$$

$$\rightarrow I_S = I_i + I_f$$

$$I_i + I_f = 0$$


$$I_f = -R V_o$$

$$\therefore I_O = \frac{V_O + R_m B V_o}{R_o}$$

$$I_O = \frac{V_O(1 + R_m B)}{R_o}$$

$$\therefore R_{OF} = \frac{V_o}{I_O}$$

$$R_{OF} = \frac{R_o}{1 + R_m B}$$

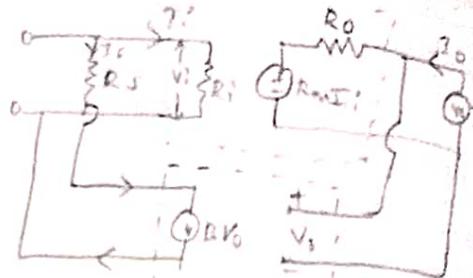

Parameter	w/o FB	w/ FB
Gain	$R_m$	$R_m/(1 + R_m B)$
I/P resistance	$R_i$	$R_i/(1 + R_m B)$
O/P resistance	$R_o$	$R_o/(1 + R_m B)$



	SHUNT-SHUNT	SERIES-SHUNT	SHUNT-SERIES	SERIES-SERIES
MIXER	SHUNT	SERIES	SHUNT	SERIES
SAMPLER	SHUNT	SHUNT	SERIES	SERIES
I/P signal	I	V	I	V
O/P signal	V	V	I	I
AMPLIFIER TRANS. RESISTANCE		VOLTAGE	CURRENT	TRANS. CONDUCTA.
GAIN	$R_m f = \frac{R_m}{1 + R_m B}$	$A_{VF} = \frac{A_v}{1 + A_v B}$	$A_{IF} = \frac{A_i}{1 + A_i B}$	$C_{mif} = \frac{C_m}{1 + C_m B}$
$R_{if}$	$R_i/(1 + R_m B)$	$R_i(1 + A_v B)$	$R_i/(1 + A_i B)$	$R_o(1 + C_m B)$
$R_{of}$	$R_o/(1 + R_m B)$	$R_o/(1 + A_v B)$	$R_o(1 + A_i B)$	$R_o(1 + C_m B)$
Other name	Voltage-shunt Voltage-current	Voltage-series Voltage-Voltage	Current-shunt Current-current	Current-series Current-Volt

## Procedure to identify type of Feed Back:

- Identify feedback element from given circuit.

- If feed back element is directly connected to output node, then it indicates voltage sampling, otherwise it indicates current sampling.

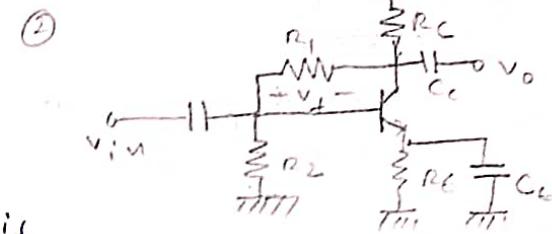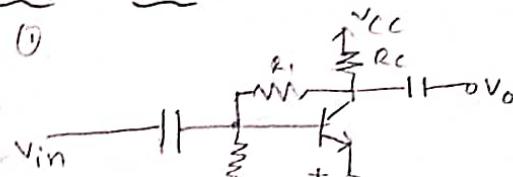- If feed back element is directly connected to input node, then it is shunt mixing otherwise it is series mixing.



(1) I/p Node: BASE

o/p Node: COLLECTOR

f/b E : RE

→ current sampling

→ series mixing

∴ Current-series -ve FB amplifier

(2) I/p Node: BASE


o/p Node: COLLECTOR

f/b E : RI

→ Voltage sampling

→ shunt mixing

∴ Voltage-shunt -ve FB Amp.

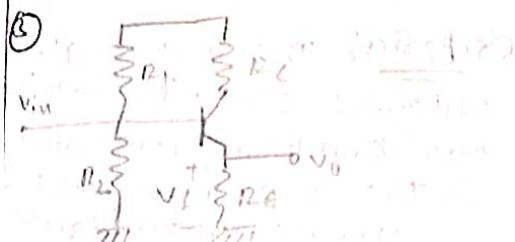

I/p series

O/P shunt

∴ VOLTAGE SERIES -VE FB AMP

## OSCILLATORS

Any circuit which is used to generate AC voltage without AC is called an "oscillator". To generate AC voltage the circuit is supplied energy from a DC source. Oscillators generates sinusoidal and non-sinusoidal signals with constant desired frequency. Oscillators uses the +ve A

- These are 3 types of oscillators:-
- i)  $|AB| < 1$ : ii) UD  
iii) Sustained (Barkhausen)

$$\rightarrow A = 5; \beta = 0.1; V_s = 0.5V, \quad \begin{array}{l} \text{Phase} \\ \text{A} \end{array} \rightarrow t$$

$$\phi = 180^\circ \quad \psi = 180^\circ \quad \begin{array}{l} 0.5V \\ \text{A} \end{array}$$


$$\rightarrow V_o = AV_i = 5 \times 0.5 \quad \begin{array}{l} 2.5V \\ \text{A} \end{array} \rightarrow t$$

$$\rightarrow V_f = BV_o \quad \Rightarrow \quad V_o = AV_i \quad \begin{array}{l} 0.1 \times 2.5 \\ = 5 \times 0.25 \end{array}$$

$$V_f = 0.25V \quad \begin{array}{l} 0.25V \\ \text{A} \end{array} \quad V_o = 0.25V \quad \begin{array}{l} 0.25V \\ \text{A} \end{array}$$

$$\rightarrow V_f = BV_o \quad \Rightarrow \quad V_o = AV_i \quad \begin{array}{l} 0.1 \times 1.25 \\ = 5 \times 0.125 \end{array}$$
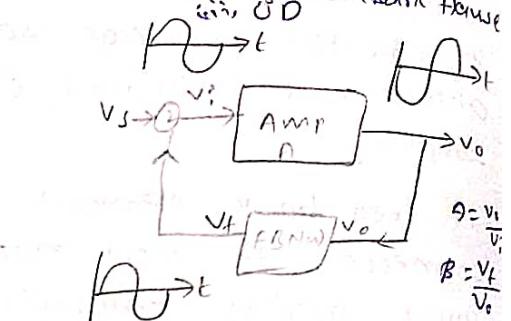
$$V_f = 0.125V \quad \begin{array}{l} 0.125V \\ \text{A} \end{array} \quad V_o = 0.125V \quad \begin{array}{l} 0.125V \\ \text{A} \end{array}$$



\* The oscillator, in which system oscillates at a frequency marginally different than undamped oscillator and the amplitude of signal gradually decreases to zero, is called 'UDO'.

- ii)  $|AB|=1$ :

$$- A = 5; \beta = 0.2; V_s = 0.5V \quad \begin{array}{l} 0.5V \\ \text{A} \end{array}$$

$$\phi = 180^\circ \quad \psi = 180^\circ$$

$$\rightarrow V_o = AV_i \quad \begin{array}{l} 2.5V \\ \text{A} \end{array}$$

$$= 5 \times 0.5 \quad \begin{array}{l} 2.5V \\ \text{A} \end{array}$$

$$V_o = 2.5V \quad \begin{array}{l} 2.5V \\ \text{A} \end{array}$$

$$\rightarrow V_o = AV_i \quad \begin{array}{l} 2.5V \\ \text{A} \end{array}$$

$$= 5 \times 0.5 \quad \begin{array}{l} 2.5V \\ \text{A} \end{array}$$

$$V_o = 2.5V \quad \begin{array}{l} 2.5V \\ \text{A} \end{array}$$

Criterions: The circuit gives sustained oscillations only when two conditions are satisfied:


- i) The loop gain must be greater than equal to unity.

ii) Feed back signal must be phase shifted by  $360^\circ$ .

$$V_f = BV_o \quad \begin{array}{l} 0.5V \\ \text{A} \end{array}$$

$$= 2.5 \times 0.2 \quad \begin{array}{l} 0.5V \\ \text{A} \end{array}$$
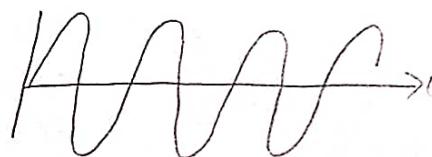
$$V_f = 0.5V \quad \begin{array}{l} 0.5V \\ \text{A} \end{array}$$



BARKHAUSEN CRITERIA

sustained oscillations

(iii)  $(AB \neq 1)$

$$A = 5; B = 0.3; V_s = 0.5 \quad \text{At } t=0$$

$$\rightarrow V_0 = AV_s \Rightarrow V_t = BV_0$$


$$V_0 = 2.5V \quad \text{At } t=0 \quad V_t = 0.75V \quad \text{At } t=0.75V$$

$$\rightarrow V_0 = AV_s \Rightarrow V_t = BV_0$$

$$= 5 \times 0.75$$

$$V_0 = 3.75V \quad \text{At } t=0 \quad V_t = 0.3 \times 3.75 \\ V_t = 1.125V \quad \text{At } t=1.125V$$

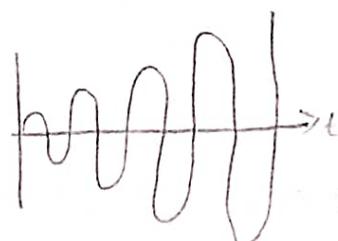When damping force is greater than critical damping force, over damped oscillations are obtained.



Over Damping Oscillations

∴ To get sustained oscillations  $AB = 1$  or  $\phi = 0^\circ$  or  $360^\circ$  Barkhausen criteria.


→ Barkhausen Criteria:

$$AB = 1, \angle AB = 0^\circ$$

sustain oscillations ( $f_0$ )


Types of Oscillators:

- Depending on the nature of the o/p:

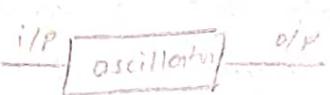


1. Harmonic Oscillator:

- Sinusoidal Oscillator → o/p

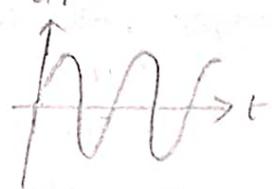

2. Relaxation Oscillator

- Non sinusoidal oscillator

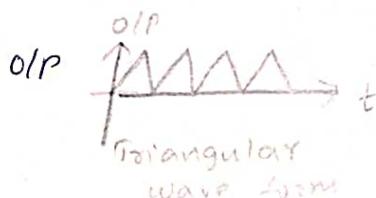



→ It is a nonlinear electronic oscillator circuit that

produces non-sinusoidal, repetitive o/p signal such as triangular, square, sawtooth wave



saw tooth wave such as triangular, square, sawtooth wave

∴

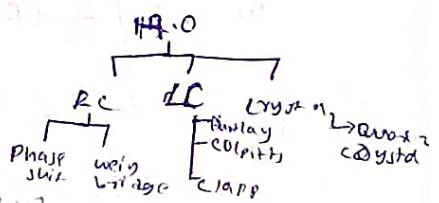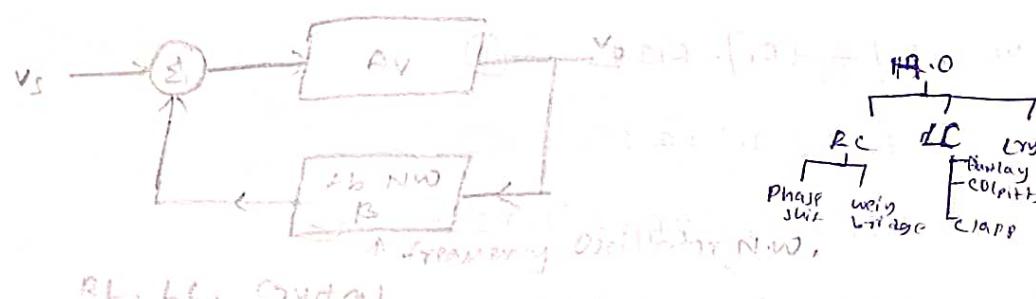

R<sub>L</sub>, L, C, Crystal

Frequency is selected by using R, L, C & crystal elements.

R<sub>C</sub>

(a) phase shift

(b) wien bridge

→ audio frequency signal

C<sub>C</sub>

(a) Hartley Oscillator


(b) Colpitts Oscillator

(c) Clapp Oscillator

Crystal

(d) Quartz crystal oscillator
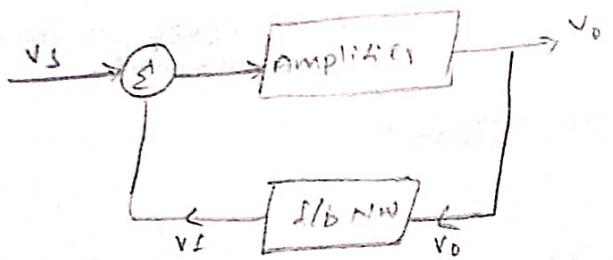
## (+) RC Phase shift oscillator using BJT's



→ A phase-shift oscillator is a linear electronic circuit that produces a sine wave.

→ It consists of an inverting amplifier element with its o/p fed back to i/p through a phase-shift netw consisting of  $R$  &  $C$  in ladder netw.

① - Audio frequency oscillator

② - Amplifier - CE configuration:  $180^\circ$


③ Feed back N.W -  $R$ ,  $C$ , combination =  $180^\circ$

$$\text{Total phase} = 360^\circ$$

$$AB = 1$$

$A = \text{real}$

$B = \text{real} (\text{Imaginary} = 0)$

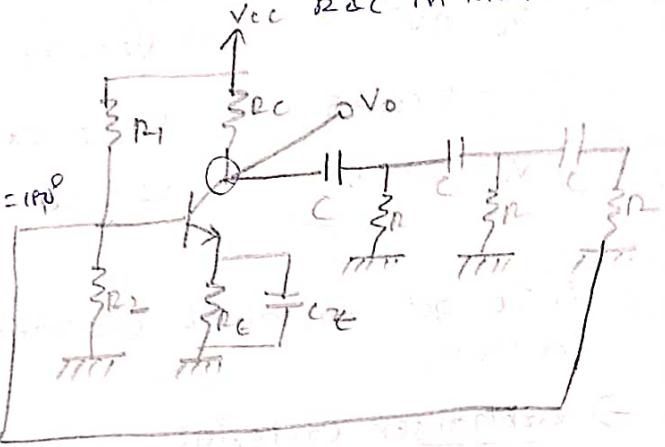

④ Advantages: - No inductor used, hence small size.

- It is well suited for frequency below 10 kHz

$$\cdot \text{Fixed frequency oscillator}, f_0 = \frac{1}{2\pi R(\sqrt{5})}$$

⑤ Disadvantages: - small o/p due to small feed back

. Frequency stability is poor due to temperature, aging.

. Require high gain, practically not possible.

→ Mathematical Analysis of RC phase shift oscillator:

$$AB = 1, A \text{ is always real number}$$

$\therefore B$  also must be real number.

$X_C = \text{Capacitive reactance } (R)$

$$\rightarrow X_C = \frac{1}{sC}; s = j\omega$$

$$V_O = \frac{I_1}{sC} + R_1(I_1 - I_2)$$

$$V_O = I_1 \left[ \frac{1}{sC} + R_1 \right] - R_1 I_2 \quad \text{--- (1)}$$


$$\rightarrow \frac{1}{sC} I_2 + R(I_2 - I_1) + R(I_2 - I_3) = 0$$

$$- R I_1 + I_2 \left[ 2R + \frac{1}{sC} \right] - R I_3 = 0 \quad \text{--- (2)}$$

$$\rightarrow I_3 \cdot \frac{1}{sC} + R I_3 + R(I_3 - I_2) = 0$$

$$0 I_1 - I_2 R + I_3 \left[ 2R + \frac{1}{sC} \right] = 0 \quad \text{--- (3)}$$

→ using cramer's rule:

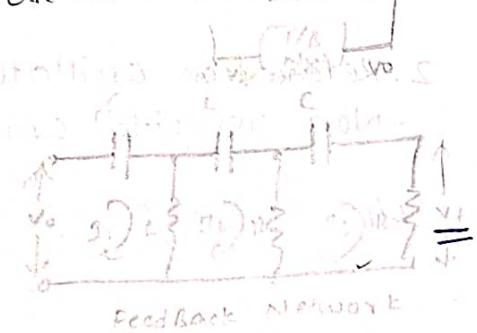

$$\begin{bmatrix} R + \frac{1}{sc} & -R & 0 \\ -R & 2R + \frac{1}{sc} & -R \\ 0 & -R & 2R + \frac{1}{sc} \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \\ I_3 \end{bmatrix} = \begin{bmatrix} V_0 \\ 0 \\ 0 \end{bmatrix}$$

$\rightarrow$  Find  $I_3$ ,  $\therefore V_F = I_3 R$ .

Find determinant of matrix,  $D = \begin{vmatrix} R + \frac{1}{sc} & -R & 0 \\ -R & 2R + \frac{1}{sc} & -R \\ 0 & -R & 2R + \frac{1}{sc} \end{vmatrix}$

$$\begin{aligned} |D| &= \left(R + \frac{1}{sc}\right) \left[\left(2R + \frac{1}{sc}\right)^2 - R^2\right] + R \left[-R(2R + \frac{1}{sc})\right] \\ &= \left(\frac{1+scR}{sc}\right) \left[4R^2 + \frac{1}{s^2c^2} + 4R^2 - R^2\right] - 2R^3 - \frac{R^2}{sc} \\ &= \left(\frac{1+scR}{sc}\right) \left[\frac{4R^2s^2c^2 + 1 + 4R^2sc - R^2s^2c^2}{s^2c^2}\right] - \left(\frac{2R^3sc + R^2}{sc}\right) \\ &= \frac{1 + 4R^2s^2c^2 + 4R^2sc - R^2s^2c^2 + scR + 4R^3s^3c^3 + 4R^2s^2c^2 - R^3s^3c^3}{s^3c^3} \\ &\quad - \frac{2R^3s^3c^3 - R^2s^2c^2}{s^3c^3} \end{aligned}$$

$$|D| = \frac{1 + 6R^2s^2c^2 + R^3s^3c^3 + 5Rcs}{s^3c^3}$$

To find  $I_3$ , find  $D_3$  of matrix,

$$[D_3] = \begin{bmatrix} \frac{1+Rcs}{sc} & -R & V_0 \\ -R & 2R + \frac{1}{sc} & 0 \\ 0 & -R & 0 \end{bmatrix}$$

$$|D_3| = V_0 (R^2)$$

$$\therefore I_3 = \frac{|D_3|}{|D|} = \frac{V_0 R^2 s^3 c^3}{1 + 6R^2 s^2 c^2 + R^3 s^3 c^3 + 5Rcs}$$

$$(s = jw)$$

$$V_F = I_3 R$$

$$B = \frac{V_F}{V_0} = \frac{w^3 R^3 s^3 c^3}{1 + 5Rcs + 6R^2 s^2 c^2 + R^3 s^3 c^3}$$

$$= \frac{-jw^3 R^3 c^3}{1 + 5Rcj - 6R^2 w^2 c^2 - jR^3 w^3 c^3}$$

$$(s = jw), \quad j^2 = -1$$

$$j^3 = -j$$

$$j^4 = 1$$

Ques P

Dividing numerator & denominator by  $-j\omega^3 R^3 C^3$ ,

$$\therefore \beta = \frac{1}{-\frac{1}{\omega^3 R^3 C^3} + \frac{j}{5} \frac{\omega R C}{\omega^3 R^3 C^3} - \frac{6}{\omega^2 R^2 C^2} - \frac{j}{\omega^3 R^3 C^3} - \frac{3}{\omega R^3 C^3}}$$

$$= \frac{1}{1 - \frac{5}{\omega^2 R^2 C^2} + \frac{j}{\omega R C} + \frac{j}{\omega^3 R^3 C^3}}$$

①-Aud

②-AM

③-Circ-

④-F

AS 'R' is real, 'β' must be real,

$$\therefore -6d + d^3 = 0$$

⑤→Adu

$$d(d^2 - 6) = 0$$

$$d^2 = 6$$

$$d = \sqrt{6}$$

$$\therefore \frac{1}{\omega C R} = \sqrt{6}$$

$$\omega = \frac{1}{CR\sqrt{6}}$$

→ Max.

AB

$$\therefore f = \frac{\omega}{2\pi}$$

capacitive,  $\omega = 2\pi f$

$$f = \frac{1}{2\pi R C \sqrt{6}}$$

which is the frequency of oscillator.

→

At this frequency,  $\beta = \frac{1}{1-5d^2}$

$$= \frac{1}{1-5(6)}$$

$$\beta = \frac{1}{-29}$$

→

-ve sign indicates phase of  $180^\circ$ .


$$\therefore |B| = \frac{1}{29}; |AB| \geq 1 / |AB| = 1$$

→

$$|A| \geq 29 //$$

- WIEN BRIDGE OSCILLATOR: electronic ckt produces sine waves.  
 - it is based on a bridge circuit  
 - originally developed for the measurement of impedances.  
 - lead-lag N/w is used as FB N/w. It consists of 4 resistors & 2 capacitors.
- at  $f = f_0$  - no phase introduces.
- at  $f > f_0$  phase lag introduction.
- at  $f < f_0$  phase lead introduction.
- R, C elements are used in FB N/w. (lead-advantage)
- overall gain is high (2 amplifiers)
- provide variable frequency range.
- complex circuit, need to balance bridge.


Circuit and Block Diagram:

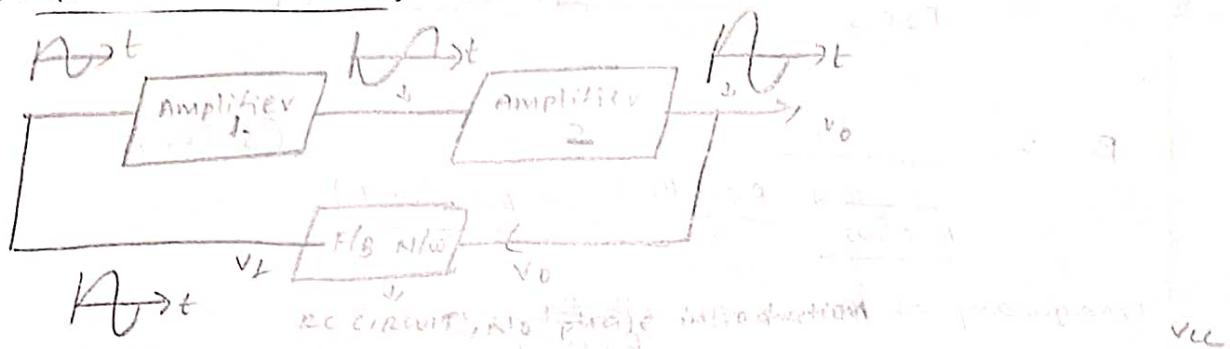

→  $R_3$  &  $R_4$  for voltage divider bias.

- Bridge is balanced means, keep the ammeter between a & b, if  $I=0$ , the bridge is balanced, then we will get sustained oscillations.

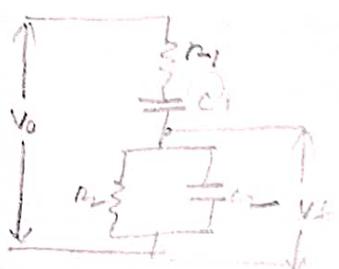→ Mathematical analysis of Wien Bridge oscillator




$$R_1 = R_2$$

$$X_{C1} = \frac{1}{C_1 S} - R_2$$

$$X_{C2} = \frac{1}{C_2 S} - R_1$$

$$R_2 = R_1$$

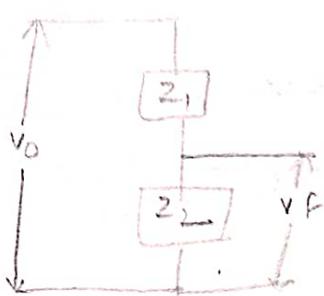

$$Z_1 = R_1 + \frac{1}{C_1 S} = \frac{1 + R_1 C_1 S}{C_1 S}$$

$$Z_2 = R_2 \times \frac{1}{C_2 S} = \frac{R_2}{R_2 C_2 S + 1}$$

$$V_f = V_0 \cdot \frac{Z_2}{Z_1 + Z_2} \quad ; \quad B = \frac{V_f}{V_0} = \frac{Z_2}{Z_1 + Z_2}$$

⑤) RC PI

$$B = \frac{Z_2}{Z_1 + Z_2}$$

$$= \frac{R_2 / 1 + R_2 C_2 s}{\frac{1 + R_1 C_1 s}{C_1 s} + \frac{R_2}{1 + R_2 C_2 s}}$$

① Audi

② Amp

③ Feed

T

④ -A

A

B

⑤) Advc

$$= \frac{R_2 C_1 s}{(1 + R_1 C_1 s)(1 + R_2 C_2 s) + R_2 C_1 s}$$

$$= \frac{R_2 C_1 s}{1 + (R_1 C_1 + R_2 C_2)s + R_1 R_2 C_1 C_2 s^2 + R_2 C_1 s}$$

$$= \frac{1}{\frac{1}{R_2 C_1 s} + \frac{R_1 C_1 + R_2 C_2}{R_2 C_1} + \frac{R_1 R_2 C_1 C_2 s^2}{R_2 C_1 s} + 1}$$

⑥) PI

$$B = \frac{1}{\frac{1}{R_2 C_1 s w} + \frac{R_1 C_1 + R_2 C_2}{R_2 C_1} + R_1 C_2 s w + 1} \quad (s = j\omega)$$

Imaginary of B,  $w R_1 C_2 - \frac{R_2 C_1}{R_2 w C_1} = 0$

$$w^2 = \frac{1}{R_1 R_2 C_1 C_2}$$

$$w = \sqrt{\frac{1}{R_1 R_2 C_1 C_2}}$$

$$f = \frac{1}{2\pi \sqrt{R_1 R_2 C_1 C_2}}$$

$$f = \frac{1}{2\pi RC}$$


→

\* LC oscillators: Hartley oscillator  
Colpitts oscillator  
Clapp oscillator.


→

- used for high-frequency sustained oscillator.
- L/C elements are used in f/b NW.

Block Diagram:

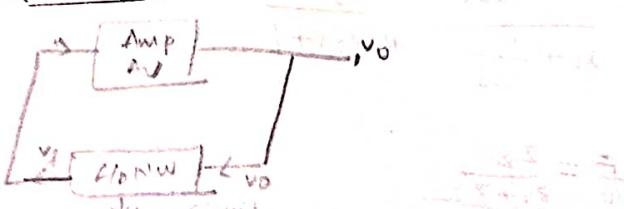

peed back Nivo:

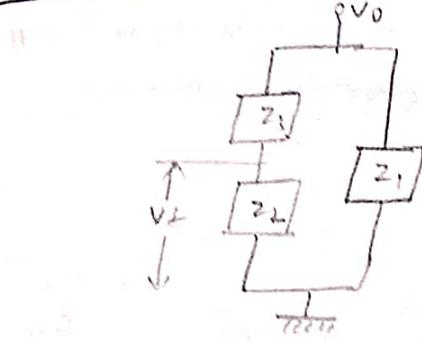

Harmonic oscillator YASTAAN

$$P_{in} \cdot z_1 = -1 \rightarrow z_2, z_3 \rightarrow \text{---}$$

$\Rightarrow$  Heathly oscillator

$$\& \text{if } z_1 \rightarrow \text{---} \rightarrow z_2, z_3 \rightarrow -1$$

$\Rightarrow$  Colpitts oscillator


Amplifier

$$\therefore V_f = \frac{z_2}{z_2 + z_3} \cdot V_o$$

$$\beta = \frac{V_f}{V_o} = \frac{z_2}{z_2 + z_3}$$

$$z_L = \frac{(z_2 + z_3)z_1}{z_1 + z_2 + z_3}$$
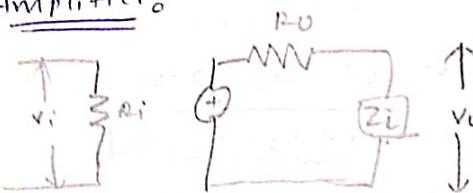
$$\text{gain, } AV = \frac{V_o}{V_i} = \frac{z_L}{z_L + R_o}$$



concept  $AB = 1$ , real

$$\frac{\left( \frac{AV \cdot (z_2 + z_3)z_1}{z_1 + z_2 + z_3} \right) \left[ \left( \frac{z_2}{z_2 + z_3} \right) \right]}{\frac{(z_2 + z_3)z_1}{z_1 + z_2 + z_3} + R_o} = 1 \quad (\text{real})$$

$$\rightarrow \frac{AV z_1 z_2 + AV z_1 z_3}{(z_2 + z_3)z_1 + R_o(z_1 + z_2 + z_3)} = \text{real}$$

$$\rightarrow \frac{AV \cdot z_1 z_2}{z_1 z_2 + z_1 z_3 + R_o(z_1 + z_2 + z_3)} = \text{real} \quad \begin{cases} z_1 = jx_1 \\ z_2 = jx_2 \\ z_3 = jx_3 \end{cases}$$

$$\rightarrow \frac{-AV x_1 x_2}{-x_1 x_2 - x_1 x_3 + R_o(j(x_1 + x_2 + x_3))} = \text{real}$$

$$R_o(x_1 + x_2 + x_3) = 0$$

$$R_o \neq 0; \boxed{x_1 + x_2 + x_3 = 0}$$


Ques

### → HARTLEY OSCILLATOR

radio frequency oscillator

uses 2 inductors & one capacitor in parallel.

Block diagram:

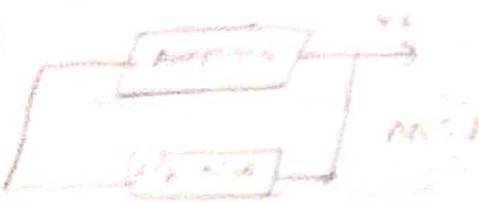

for LC oscillator.

$$X_1 + X_2 + X_3 = 0$$

$X_1 = -Z_1$  (inductive reactance)

$Z_2 = j\omega L_2$

$$L_2 = \frac{1}{\omega^2 C_2} = j\omega L_2$$

$$C = X_2 = \frac{1}{j\omega L_2} = \frac{1}{j\omega C_2} \quad (\text{if } j\omega)$$

$X_1 + X_2 + X_3 = 0$       Advantages:

$$\text{e)} \quad j\omega(C_1 + L_2) + \frac{1}{j\omega C_2} = 0$$


$$\therefore j\omega(L_1 + L_2) - \frac{1}{\omega^2 C_2} = 0$$

$$\omega(L_1 + L_2) = \frac{1}{\omega^2 C_2}$$

$$\omega^2 = \frac{1}{(L_1 + L_2)C_2}$$

$$\text{f)} \quad \omega = \frac{1}{\sqrt{(L_1 + L_2)C}}$$
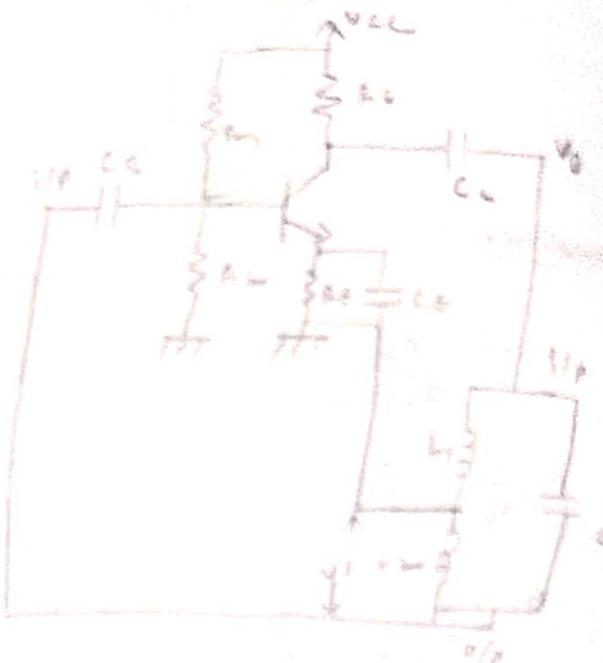
$$\boxed{\omega = \frac{1}{2\pi\sqrt{(L_1 + L_2)C}}}$$



Disadvantages:

- Radio frequency drift

- Adjustable frequency from capacitors

- Use of auto-transformer (single)

Disadvantages:

- Size is very large (2 inductors)

- High cost

- Cannot generate low frequencies

- Poor frequency stability.



### → COLPITTS OSCILLATOR


$$\text{Ans 1} \rightarrow \frac{1}{C_1} = \frac{1}{j\omega L_1} \quad (\text{X}_1)$$

$$j\omega C_2 \rightarrow \frac{1}{C_2} = \frac{1}{j\omega L_2} \quad (\text{X}_2)$$

$$\omega L_2 + \omega L_1 = j\omega L \quad (\text{X}_3)$$

$$X_1 + X_2 + X_3 = 0$$
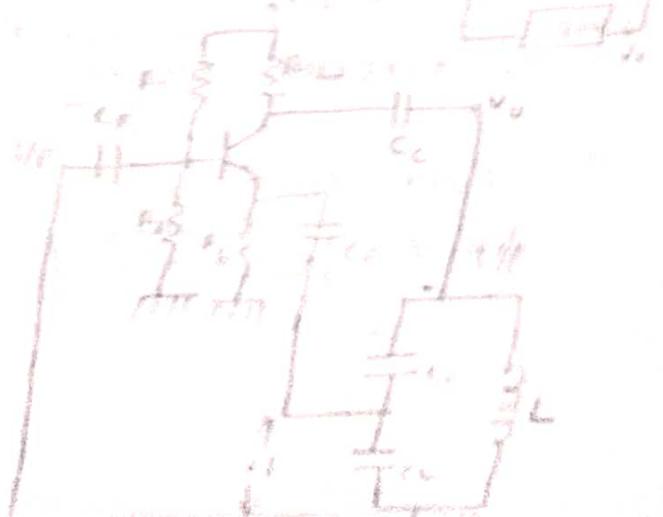
$$\frac{1}{j\omega L_1} + \frac{1}{j\omega L_2} + \frac{1}{j\omega C_2} = 0$$



$$\frac{-j}{\omega C_1} - \frac{j}{\omega C_2} + j\omega L = 0$$

$$j\omega L = \frac{j}{\omega C_1} + \frac{j}{\omega C_2}$$

$$\omega L = \frac{C_1 + C_2}{\omega C_1 C_2}$$

$$\omega^2 = \frac{(C_1 + C_2)}{L C_1 C_2}$$

$$\omega^2 = \frac{1}{L \left( \frac{C_1 C_2}{C_1 + C_2} \right)}$$

$$\omega = \sqrt{\frac{1}{L \left( \frac{C_1 C_2}{C_1 + C_2} \right)}}$$

$$\therefore f = \frac{1}{2\pi \sqrt{L \left( \frac{C_1 C_2}{C_1 + C_2} \right)}}$$

$$\omega^2 = \frac{1}{L} \left( \frac{1}{C_1} + \frac{1}{C_2} \right)$$

$$\omega = \frac{1}{\sqrt{L}} \sqrt{\frac{1}{C_1} + \frac{1}{C_2}}$$

### Advantages:

- Small size as compared to oscillators

### Disadvantages:

- Difficult to design
- Poor isolation.
- It cannot be stable due to internal capacitances of transistors.

### CLAPP OSCILLATOR

→ Provide frequency stability.

→ Uses one extra capacitor.


- LC oscillator.

→ It has internal capacitance and,  $C_{in}$  &  $C_{out}$ .

i.e.,  $C_{in}$  appear in series with  $C_1$  &  $C_{out}$  appear in series with  $C_2$ .

$$\therefore C_1 = C_1 + C_{in}$$

$$C_2 = C_2 + C_{out}$$

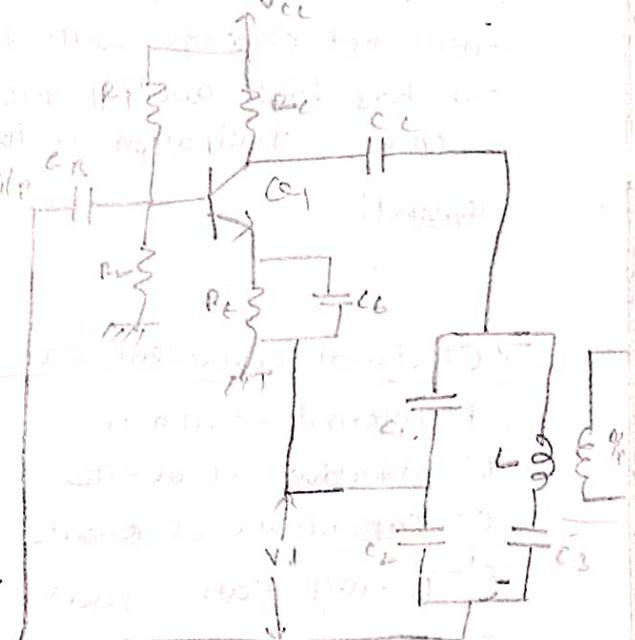

①

RC ph

v

$$\therefore f_0 = \frac{1}{2\pi} \sqrt{\frac{1}{L} \left( \frac{1}{C_1} + \frac{1}{C_2} \right)}$$

$f_0$  is not stable, to eliminate that problem additional  $C_3$  is connected.

$C_3$  is selected to be smaller than  $C_1 + C_2$ .

In LC oscillator,  $x_1 + x_2 + x_3 + x_4 = 0$

① - Audi

② - Amp

③ - Feed

T

$$\Rightarrow \frac{1}{C_3} \gg \frac{1}{C_1} + \frac{1}{C_2}$$

④ - AI

A

B

⑤ - ADC

$$\therefore f_0 = \frac{1}{2\pi} \sqrt{\frac{1}{L} \left( \frac{1}{C_3} \right)}$$

$$f_0 = \frac{1}{2\pi\sqrt{LC_3}}$$

⑥ - DI

★ CRYSTAL OSCILLATOR: -

- It is fixed frequency oscillator.

- Frequency is highly stable

- LC oscillator

- Quartz crystal is used in place of inductor.



→ Quartz → piezoelectric material, converts electrical energy to mechanical energy vice versa.

→ Properties of Quartz material:

- will not change with temperature & time

- it has high quality factor, D  
(power dissipation is low)

→ Symbol:

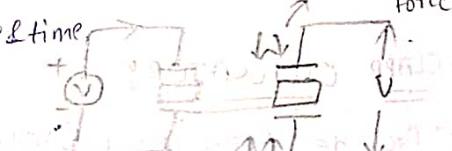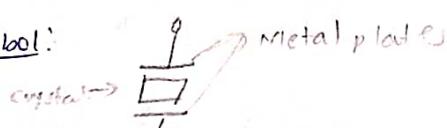

PEE  
Piezoelectric Effect  
IPCE  
Inverse PEE

→ Electrical equivalent circuit:

L = Mechanical Mass

C = Quartz thickness

R = Resistive loss

$C'$  = due to metal plates/electrodes

R: Internal resistance

L: Inductance of Quartz

C: Capacitance of Quartz

$C'$  = parallel plate capacitor

Two metal plates separated by a dielectric crystal slab

$C_{S0} C$ : Series capacitance

$C'_P C$ : parallel capacitance

## OSCILLATOR CIRCUITS


### Behaviour of crystal impedance vs frequency

$\rightarrow f_s$  = series resonance frequency

$\rightarrow f_p$  = parallel resonance frequency

$\Rightarrow$  series resonant condition occurs when  $X_L = X_C$

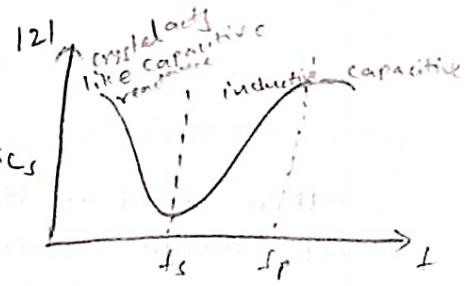(or)  $X_L = X_C$  under this condition the impedance is minimum.





$$f_s = \frac{1}{2\pi\sqrt{LC}}$$

$\rightarrow$  parallel resonant condition occurs when the reactance of series resonant loop equals to the reactance of the mounting capacitor ( $C_p$ ).

$$\text{under parallel resonance, } C_{eqv} = \frac{C_p C_s}{C_p + C_s}$$

$$f_p = \frac{1}{2\pi\sqrt{L C_{eqv}}}$$

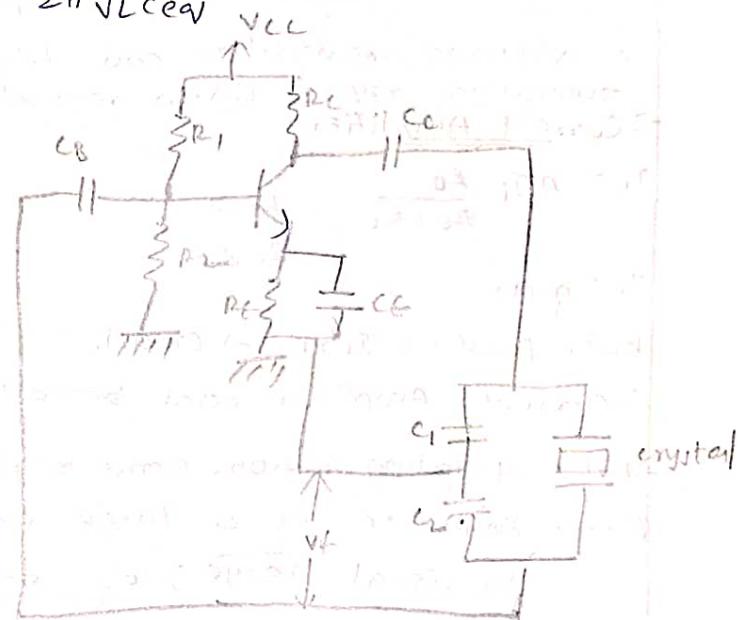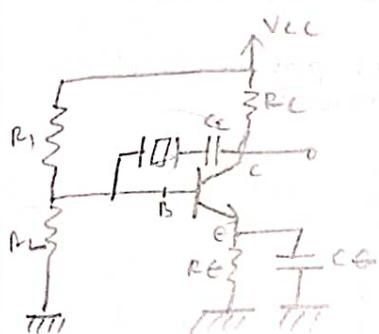

$$f_s < f_p$$

## 2/2/23 4. POWER AMPLIFIERS

① RC P



- It is used to deliver a substantial amount of power to load.
- It should convert DC power into AC power efficiently.
- Power conversion efficiency, power dissipation.
- To get maximum power at load.

② Aud

③ AM


④ Freq

→ Voltage Amplifier:

$$V_L = A_v \cdot V_i \cdot \frac{R_L}{R_L + R_o}$$

$$R_o \ll R_L$$

$$R_L \gg R_o$$

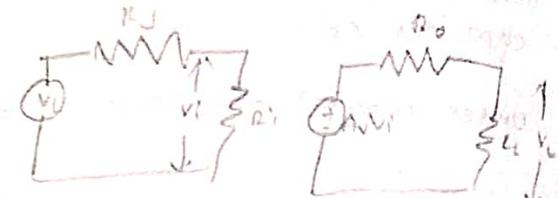


∴  $V_L = A_v V_i$  is large but  $R_o = \frac{V_L^2}{R_L}$  is moderate value.

⑤ → Adi

- ∴ Voltage amplifier can't be used as power amplifier.
- operating region - linear region (active region)

→ Current Amplifier:
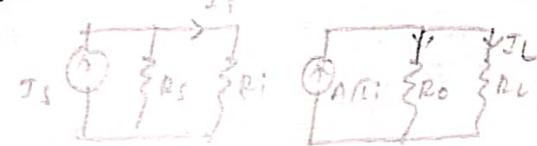
$$I_L = A_i I_i \frac{R_o}{R_o + R_L} \quad R_o \gg \quad R_L \ll$$



$$I_L = \text{max}$$

→ Mo

$$\text{but, power} = I^2 \times R_L \Rightarrow \text{small.}$$

AE

∴ Current Amplifier can't be used as power amplifier.


→ BJT operating region: Active region (linear region)

X power amplifier is a large signal amplifier,

→

∴ I<sub>IP</sub> signal - large; o/p signal - large

large (Not of mv & μV)

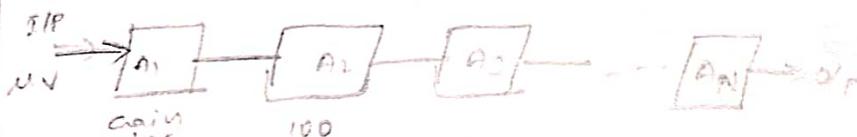

$$\text{o/p of 1st amp} = 1 \times 10^6 \times 100 = 10^4 \text{ V}$$

$$\text{o/p of 2nd amp} = 10^{-4} \times 100 = 10^{-2} \text{ V}$$

$$\text{o/p of 3rd amp} = 10^2 \times 100 = 1 \text{ V}$$

$$\text{o/p of 4th amp} = 1 \text{ V} \rightarrow \text{Power amplifier} \rightarrow \text{o/p}$$

∴ used in speakers.


∴ last stage can be considered as power amplifier.

→ Difference b/w V/I & P amplifiers.

## V,I Amplifiers & Power Amplifiers

- 1. S/I signal strength: small      1. S/I signal strength: large
- 2. Operating region: Active region      2. Operating region: linear & non-linear (linear region)
- 3. Method used:
  - Mathematical, i.e., model, hybrid-B model etc.
  - Graphical
- 4. Parameter analysis:
  - $A_V, A_{VI}, R_L, R_o$
- 5. Types of power Amplifiers:

Basic concept:

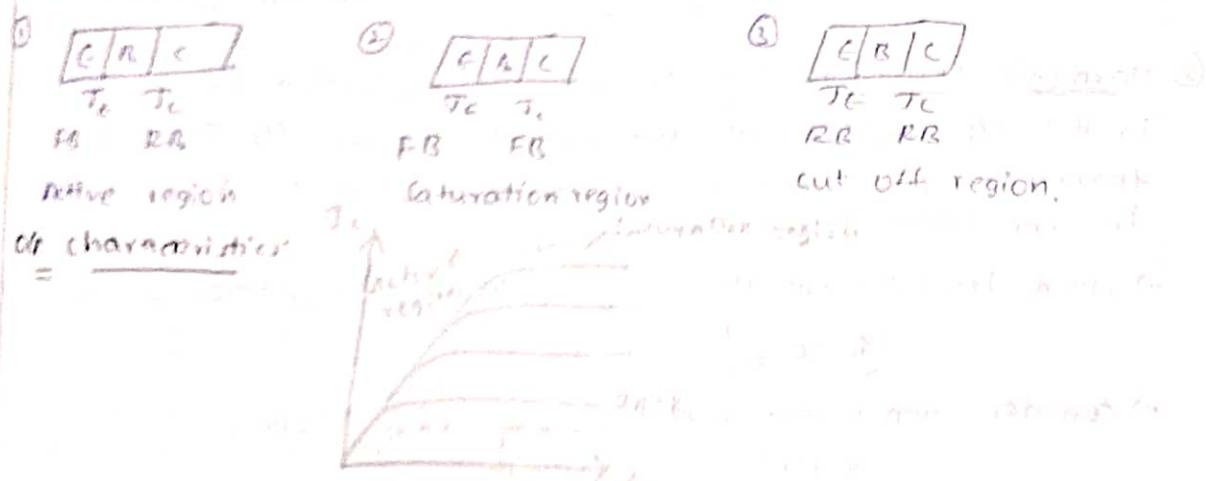

Operating point:

$$Q \left( I_c, V_{ce} \right)$$

Voltage & current amplification

- operation, Active (in linear region)

- Power Amplifier - linear & non-linear region.

① Class A Amplifier: position of the operating point at middle of AC load line.

→ Operates in linear region (active region).

② Class B Amplifier: operating point is moved either in upward direction (saturation region) / in downward direction (cut-off region)

→ Operates in non-linear region.


③ Class AB Amplifier: operating point is in slightly above cut-off / slightly below saturation.

→ Operates in non-linear region.


④ Class C Amplifier: operating point is in deep cut-off (no saturation). → Operates in non-linear region.

① RC

## DISTORTION IN POWER AMPLIFIER

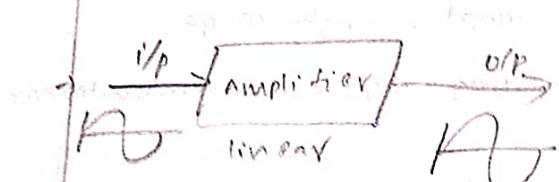

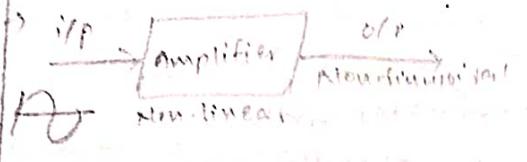- If it operates in linear region,  
then there will be no distortion.  
- Frequency does not change,  
i.e.,  $f_{out} = f_{in}$ .



### Frequency distortion

$f_1, f_2, f_3 \dots A_1, A_2, A_3$   
 $f_1 + f_2 + f_3$

- different gains.

② Phase distortion is also known as "delay distortion".

$$f_1, f_2, f_3 \quad \underline{\quad} \quad f_1 \quad f_2 \quad f_3 \\ \phi_1 \quad \phi_2 \quad \phi_3 \quad \text{different phases.}$$

③ Harmonic Distortion: This is due to production of new frequencies in the o/p, which are not present in the i/p. These new frequencies (or) harmonics are generated when transistor operates in non linear region.

→ when Transistor operates in linear region the relation ship b/w i<sub>c</sub> & i<sub>b</sub> is

$$i_c = R_i b$$

→ consider non linear region (a) Non linear function

$$y = f(x)$$

$$y = a_0 + a_1 x + a_2 x^2 + \dots$$

$$\text{ny} \quad i_c = I_c + a_1 i_b + a_2 i_b^2 + a_3 i_b^3 + \dots$$

↑  
DC current

Let  $i_b = C \cos \omega t$  - signal of fundamental frequency  $\omega$  in rad/s

$$i_c = I_c + a_1 \cos \omega t + a_2 \cos^2 \omega t + a_3 \cos^3 \omega t + \dots$$

$$i_c = I_c + a_1 \cos \omega t + a_2 \left( 1 + \frac{\cos 2\omega t}{2} \right) + \dots$$

$$i_c = I_c + \left[ \frac{a_2}{2} + \dots \right] + a_1 \cos \omega t + \frac{a_2}{2} \cos 2\omega t + \dots$$

$$\text{Actual harmonic} \quad i_c = I_c + \left[ \frac{a_2}{2} + \dots \right] + B_1 \cos \omega t + B_2 \cos 2\omega t + B_3 \cos 4\omega t + \dots$$

$\Rightarrow I_o$  = Average value due to distortion

$B_1$  = Amplitude of 1st fundamental component

$B_2$  = " 2nd harmonic component "

Amplification

$$D_2 = 2^{\text{nd}} \text{ harmonic distortion} = \left| \frac{S_2}{S_0} \right|$$

$$D_3 = 3^{\text{rd}} \text{ harmonic distortion} = \left| \frac{S_3}{S_0} \right|$$

Total Harmonic Distortion  $D = \sqrt{D_2^2 + D_3^2 + \dots + D_n^2}$

$$D = \sqrt{\frac{R_1^2 + R_2^2 + \dots + R_n^2}{R_1^2}}$$

fundamental AC power due to fundamental frequency

$$P_0 = P_{\text{fund}}$$

$$P_0 = \left( \frac{E_0}{Z_0} \right)^2 \times C_0 = \frac{E_0^2}{Z_0} C_0$$

$$P_T = \frac{E_0^2}{Z_0} C_0 + \frac{E_1^2}{Z_0} C_0 + \frac{E_2^2}{Z_0} C_0 + \dots$$

$$= \frac{E_0^2}{Z_0} C_0 \left[ 1 + \frac{E_1^2}{E_0^2} + \frac{E_2^2}{E_0^2} + \dots \right]$$

$$= \frac{E_0^2}{Z_0} C_0 \left[ 1 + D_2^2 + D_3^2 + \dots \right]$$

$$(P_T = P_0 (1 + D^2))$$

## CLIPPING AND DISTORTION:



(i)  $V_{IN} > 0.7V$

$\Rightarrow T_C = T_B$

$\Rightarrow V_{CE} < 0.0V$

$\Rightarrow T_C > T_B$

$\Rightarrow V_{CE} > 0.7V$



(ii)  $V_{IN} < -0.7V$

$\Rightarrow T_C = T_B$


$\Rightarrow V_{CE} < 0.0V$

$\Rightarrow T_C < T_B$

$\Rightarrow V_{CE} > -0.7V$

At midpoint of  $-0.7V < V_{IN} < 0.7V \Rightarrow T_C = T_B$

$T_C = 0.6V$

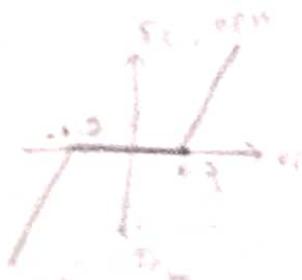


Under this condition there will not be any distortion  
 $\Rightarrow D = 0\%$

Dead Zone: The region of input voltage for which clipping occurs called as "dead zone".

Clipping and distortion are type of distortion, which is caused by switching time devices driving a load. It is most commonly seen in complementary half push-pull class B amplifiers.

③ RC

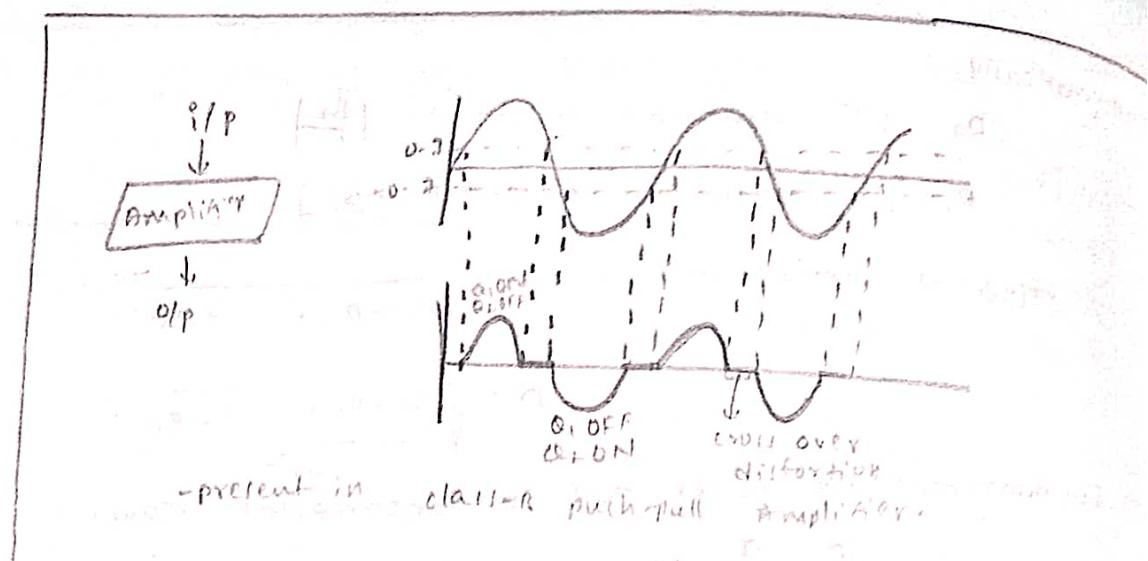

① -AU


② -AR

③ -FE
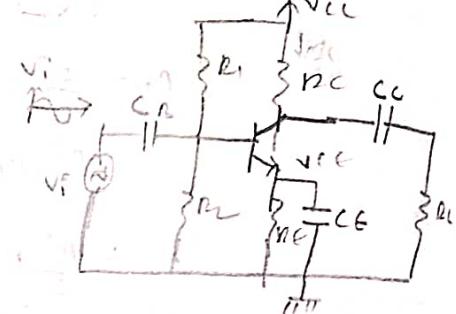
### \* CLASS A POWER AMPLIFIER

→ Direct coupled / series fed class A power Amplifier.

$$\begin{aligned} \text{At } V_{CE} &= V_{CC} - I_C R_C \\ &\rightarrow V_{CC} = I_C R_C + V_{CE} \\ &\rightarrow V_{CE} = V_{CC} - I_C R_C \end{aligned}$$



• Q-point is in center of load line

•  $V_i \rightarrow$  in order of volts

• BJT amplifier is in Active region / linear region

→ case-i:  $V_i + V_e$  cycle

→  $I_B$  increases

$$\rightarrow I_C = \beta I_B \Rightarrow I_C (\uparrow)$$

$$V_{CE} = V_{CC} - I_C R_C$$

$$I_C R_C (\uparrow) \therefore V_{CE} (\downarrow)$$

phase shift =  $180^\circ$

$$V_{CE} = V_{CC} - I_C R_C$$

$$V_{CE\max} = V_{CC}/I_C = 0$$

$$I_{C\max} = \frac{V_{CC}}{R_C} / V_{CE\min}$$

NOTE: If  $V_i = 0V$

→ Due to DC biasing, collector current =  $I_{CO}$

→ Collector to Emitter voltage =  $V_{CEQ}$



$$\therefore \text{Power dissipation} = I_{CO} \times V_{CEQ} \text{ (more)}$$

∴ power dissipation is more in power drain.

→ characteristics of class-A Amplifier:

• O/P current flows for entire cycle ( $0^\circ - 360^\circ$ )

• Does not have non linear distortion

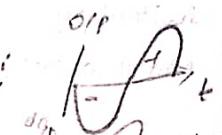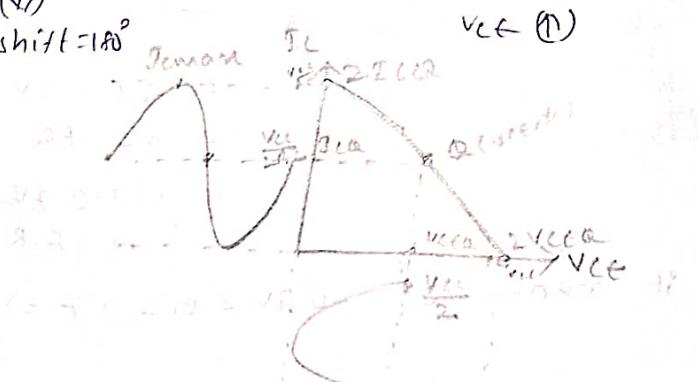


- Nature of o/p signal does not change at o/p.
- o point lies in the middle of load line. (Active region)
- low conversion efficiency  $\approx 25\%$ .

$P_{dc} = P_{ac}$  (low - 2.5W)

- power dissipation is high when i/p is not applied.

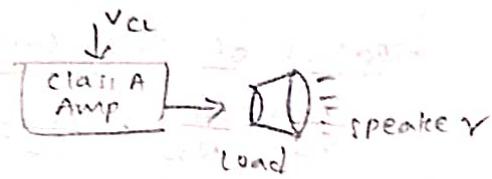- provides undistorted o/p (operates in linear region)
- conduction angle :  $360^\circ$



### Advantages

- No distortion
- No Thermal run away

### Disadvantages

- Low efficiency
- Power drain

### Efficiency in of class A Amplifier:

- efficiency,  $\eta = \frac{\text{o/p power}}{\text{i/p power}} = \frac{P_{ac}}{P_{dc}}$

$$\boxed{P_{dc} = V_{cc} \times I_{c(\alpha)}} = V_{cc} \cdot \frac{V_{cc}}{2R_c} = \frac{V_{cc}^2}{2R_c}$$

$$\rightarrow \text{o/p power } P_{ac} = V_{cc\text{rms}} \times I_{c\text{rms}}$$

From graph Ic peak to peak is  $I_{c(pp)} = \frac{V_{cc}}{R_c} - 0 = \frac{V_{cc}}{R_c}$

∴ peak value of  $I_c$   $I_{cp} = \frac{V_{cc}}{2R_c}$

$$V_{cc\text{rms}} = \frac{V_{cc(p)}}{\sqrt{2}} = \frac{V_{cc}}{2\sqrt{2}} \quad V_{cc\text{dc}} = \frac{V_{cc}}{2}$$

$$P_{ac} = \frac{V_{cc}}{2\sqrt{2}R_c} \cdot \frac{V_{cc}}{2\sqrt{2}} = \frac{V_{cc}^2}{8R_c}$$

$$V_{cc\text{rms}} = \frac{V_{cc}}{2\sqrt{2}}$$

$$\therefore \eta = \frac{P_{ac}}{P_{dc}} = \frac{\frac{V_{cc}^2}{8R_c}}{\frac{V_{cc}^2}{2R_c}} = \frac{1}{4}$$

$$\eta = 0.25$$

$$\boxed{\eta = 25\%}$$


$$\frac{P_{dc}}{10W} = \frac{P_{ac}}{2.5W}$$

7.5W dissipated.

→ A class-A power amplifier is one in which the o/p current flows for the entire cycle of AC input supply.
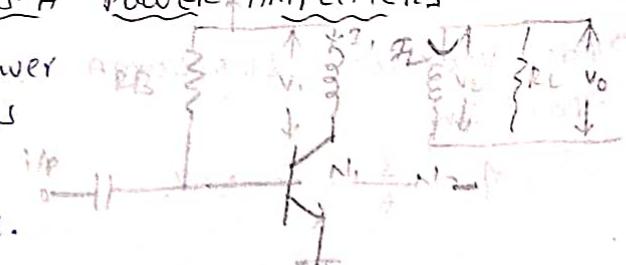
### TRANSFORMER COUPLED CLASS-A POWER AMPLIFIERS

- In direct coupled class A power Amplifier, with no i/p,  $I_c$  flows through  $R_L$  &  $R_C$ .



∴ power dissipation is more.

- In transformer coupled class A power amplifier with no i/p, dc current will not flow from primary to


④ RC F

secondary.  $\therefore$  No current through  $R_C$   
 $\Rightarrow$  No power dissipation.

$\rightarrow$  Basics of Transformer:

$$\frac{V_1}{V_2} = \frac{N_1}{N_2}, \quad \frac{I_1}{I_2} = \frac{N_2}{N_1}$$
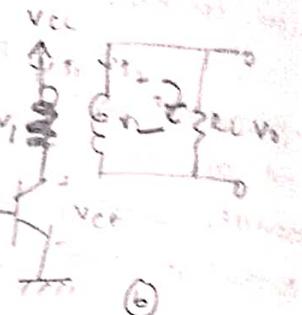
$$\rightarrow R_{LP} = \frac{V_2}{I_2}, \quad R_{LP} = \frac{V_1}{I_1} = \frac{V_2 \cdot N_1}{I_2 \cdot N_2}$$



① Au

② Ar

③ Fe

④ -

$$R_{LP} = \frac{V_2}{I_2} \cdot \left(\frac{N_1}{N_2}\right)^2 = R_L \cdot \left(\frac{N_1}{N_2}\right)^2; \quad \frac{N_1}{N_2} = \text{Turns Ratio}$$

$\therefore$  Transformer coupling will work by choosing turns ratio for impedance matching (to avoid loading effect).

- From fig ④ if no i/p,  $\therefore$  no drop across primary,  $V_{CC}$

$$- I_C(P-P) = 2 I_C; \quad V_{CE}(P-P) = 2 V_{CC}$$

$$- I_C(P) = I_C; \quad V_{CE}(P) = 2 V_{CC}$$

$$- I_{C\text{rms}} = \frac{I_C}{\sqrt{2}}; \quad V_{CE\text{rms}} = \frac{V_{CC}}{\sqrt{2}}$$

$$\therefore P_{AC} = V_{rms} \cdot I_{rms} = \frac{V_{CC} I_C}{2}$$

$\rightarrow$

$$P_{DC} = V_{CC} \times I_{CO} = V_{CC} I_C.$$

$$\therefore \eta \text{ of transformer coupled} = \frac{P_{AC}}{P_{DC}} = \frac{V_{CC} I_C / 2}{V_{CC} I_C} = \frac{1}{2}$$

$$\boxed{\eta = 50\%}$$

$\therefore$  DC power dissipation decreases and  $\eta$  increases.

① A T/F coupled class A power amplifier supplies 3W power to speaker. If supply voltage is 30V and  $I_{CO}$  is 200mA, then find  $\eta$  of this amplifier.

$$\text{sol: } \eta = \frac{P_{AC}}{P_{DC}}$$

$$\Rightarrow P_{DC} = V_{CC} \times I_{CO} = 30 \times 200 \text{ mA} = 6 \times 10^3 \text{ mA}^2 = 6 \text{ W}$$

$$\Rightarrow P_{AC} = 3 \text{ W}$$


$$\therefore \eta = \frac{3}{6} = \frac{1}{2} = 50\%.$$

- Q) If series fed direct coupled class A Amplifier supplies 0.8W power to speaker, if supply voltage is 30V &  $I_{CQ}$  is 200mA, find  $\eta$ .  
 $P_{AC} = 0.8W$ ,  $P_{DC} = V_{CC} \times I_{CQ} = 30 \times 200 = 6W$
- $$\therefore \eta = \frac{0.8}{6} = \frac{8}{60} = 0.13$$
- $\boxed{\eta = 13\%}$

- Q) single stage class-A has 20V ( $V_{CC}$ ),  $I_{CQ} = 600mA$ ,  $V_{CEO} = 10V$ ,  $R_L = 16\Omega$   
 AC o/p current varies by 300mA. find  
 i) Power supplied by DC source to Amplifier.  
 ii) Efficiency of Amplifier.

$$\text{Sol: } \eta = \frac{P_{AC}}{P_{DC}}$$
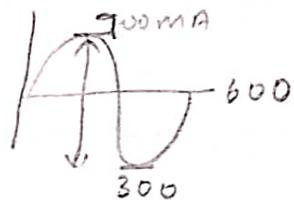
$$\begin{aligned} \rightarrow P_{AC} &= V_{rms} \cdot I_{rms} = I_{rms}^2 \times R_L \\ &= \left(\frac{300}{\sqrt{2}}\right)^2 \times 16 \times 10^6 \\ &= \frac{90000}{2} \times 16 \times 10^6 \\ &= 4.5 \times 16 \times 10^2 \\ &= 72 \times 10^2 \\ \boxed{P_{AC} = 0.72W} \end{aligned}$$



$$\begin{aligned} I_{C(p-p)} &= 900 - 300 = 600mA \\ I_{C(p)} &= \frac{600}{2} = 300mA \\ I_{Crms} &= \frac{300}{\sqrt{2}}mA \end{aligned}$$

$$\rightarrow P_{DC} = V_{CC} \times I_{CQ} = 20 \times 600 \times 10^{-3} = 12W$$



$$\therefore \eta = \frac{P_{AC}}{P_{DC}} = \frac{0.72}{12} = 6 \times 10^{-2}$$

$$\boxed{\eta = 6\%}$$
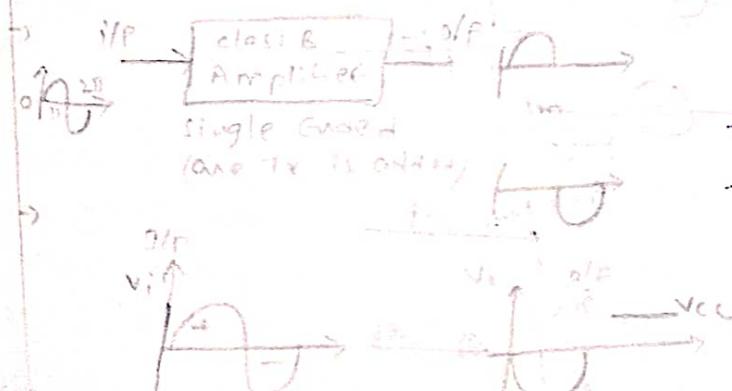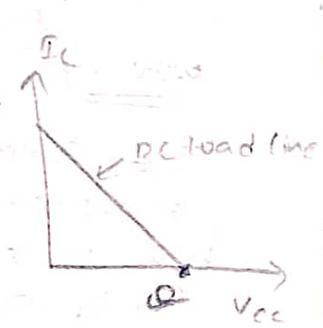
### Class B - Power Amplifier:

Q-point is in cut off region.


- No biasing is used ( $R_B$  &  $R_E$  are not used)
- $\eta$  is very high (78.5%)
- conduction angle is  $180^\circ$



- $\rightarrow$  No power drain  
 $\rightarrow$  It has lot of distortion  
 $\rightarrow$  Information at o/p: 50%.

⑤  $\text{RC } P$

### Single Ended class B Amplifier

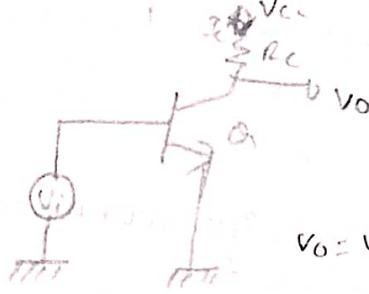

$$V_O = V_{CC} - I_C R_L$$

① - AW

② - AR

③ - FE

④ -

Case - 1:

During positive half cycle.

$Q_1$  = Emitter junction = FB  
- Collector junction -  $R_B$  { Active region

$$I_C R_C \uparrow \therefore V_O = V_{CC} - I_C R_C$$

⑤ - IP

$$V_O \downarrow$$

Case - 2:

- During -ve cycle

$Q_2$  = Emitter junction -  $R_E$   
- Collector junction -  $R_A$

$$I_C = 0 \therefore V_O = V_{CC}$$

$$\Rightarrow V_{CC} = V_O$$

∴ we get o/p with  $180^\circ$  phase shift

⑥ -


### PUSH PULL CLASS B POWER AMPLIFIER

- push pull circuit requires the two transistors:  
- idriver + transformer in, o/p transformer.

- Both the transistors are in CE configuration, if p is at primary of 1st transformer.  
- centre tapping at secondary of 1st transformer is under tapping at primary of 2nd transformer. P is connected to

working:

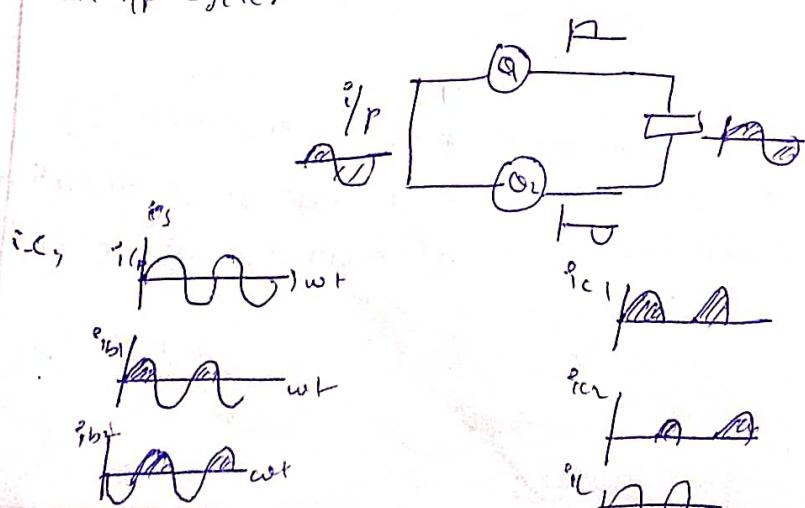→  $Q_1$  conducts for +ve half cycle producing the +ve half cycle across load &  $Q_2$  conducts for -ve half cycle producing -ve half cycle across load. Thus we get a full cycle for full i/p cycle.




## PUSH PULL CLASS B POWER AMPLIFIERS

- Two transistors used

(Q2-NPN  $\rightarrow$  push pull class B Amplifier)

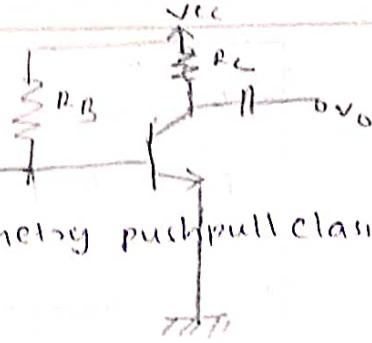(Q1-NPN & Q2-PNP  $\rightarrow$  complementary symmetry push-pull class Amplifier)



$\rightarrow$  push pull mode.




During +ve cycle: Q1 ON, Q2 OFF

During -ve cycle: Q1 OFF, Q2 ON

complete Input is processed.


working

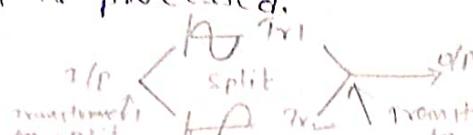

$\Rightarrow$  Q1 = Transistor one (Q1)

$\Rightarrow$  Q2 = Transistor two (Q2)

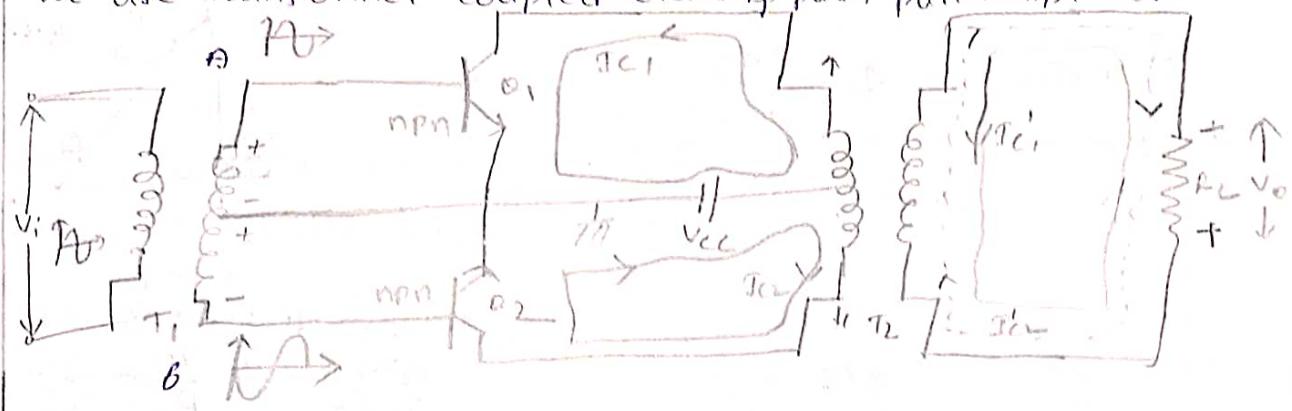$\rightarrow$  we use Transformer coupled class B push pull Amplifier.



$\rightarrow$  During +ve cycle - Q1 = Active

Q2 = OFF

$$I_{C1} \text{ across } R_L \text{ No: } \frac{1}{2} \frac{L}{R_L}$$




$\rightarrow$  During -ve cycle - Q2 = Active

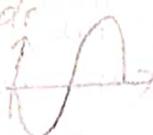Q1 = OFF

$$I_{C2} \text{ across } R_L, V_o: \frac{1}{2} \frac{L}{R_L}$$




$\rightarrow$  phase shift =  $180^\circ$



### EFFICIENCY:

- During +ve half cycle Q1 works

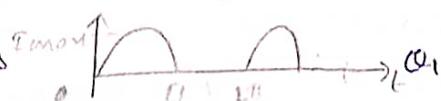

- During -ve half cycle Q2 works



$$\text{I}_{DCQ1} = \frac{I_{Cmax}}{\pi} \text{ (half cycle)}$$

$$\text{I}_{DCQ1} = \frac{1}{2\pi} \int_0^{\pi} I_{Cmax} \sin(\omega t) dt$$

$$\text{I}_{DCQ2} = \frac{I_{Cmax}}{\pi}$$

$$= \frac{1}{2\pi} \cdot I_{Cmax} \left[ \cos(\omega t) \right]_0^{\pi}$$

$$\text{I}_{DC}(Q1 \& Q2) = \frac{2I_{Cmax}}{\pi} \left[ \frac{I_{Cmax}}{\pi} + \frac{I_{Cmax}}{\pi} \right]$$

$$= \frac{1}{2\pi} I_{Cmax} [-(-1-1)]$$

$$= \frac{I_{Cmax}}{\pi}$$

$$V_o = V_{CC}$$

④ Q-  
Q-  
Q-

$$* P_{dc} = V_{DC} \times I_{DC}$$

$$P_{dc} = V_{DC} \times 2 \frac{I_{max}}{\pi}$$

$$* P_{AC} = V_{max} \times I_{max}$$

$$\rightarrow V_{P-P} = 2V_{DC} - 0 = 2V_{DC}$$

$$\rightarrow V_{peak} = V_{DC} \Rightarrow V_{rms} = \frac{V_{DC}}{\sqrt{2}} ; I_{rms} = \frac{I_{max}}{\sqrt{2}}$$

$$\rightarrow P_{AC} = V_{DC} \times \frac{I_{max}}{\sqrt{2}}$$

$$P_{AC} = \frac{V_{DC} \times I_{max}}{2}$$

$$* \text{efficiency, } \eta = \frac{P_{AC}}{P_{dc}}$$

$$= \frac{V_{DC} \times I_{max}}{2} \times \frac{\pi}{V_{DC} \times 2 I_{max}}$$

$$= \frac{\pi}{4}$$
  
$$= \frac{3.14}{4}$$

$$\eta = 0.785$$

$$(\% \eta = 78.5\%)$$

Let, if DC power = 100W

$$AC power = 28.5W$$

### HARMONIC DISTORTIONS

Due to nonlinear distortion, the collector current of the two transistors can be expressed in terms of harmonic components as:



$$i_{C1} = I_{C0} + B_0 \cos \omega t + B_1 \cos 2\omega t + B_2 \cos 3\omega t + B_3 \cos 4\omega t + \dots$$

The collector current for the second transistor can be obtained by replacing  $\omega t$  by  $\omega t \pm \pi$

$$\therefore i_{C2} = I_{C0} + B_0 \cos(\omega t + \pi) + B_1 \cos(2\omega t + 2\pi) + B_2 \cos(3\omega t + 3\pi) + B_3 \cos(4\omega t + 4\pi) + \dots$$

$$i_{C2} = I_{C0} + B_0 - B_1 \cos(\omega t) + B_2 \cos 2\omega t - B_3 \cos 3\omega t + \dots$$

$$\therefore P_L = i_{C1} \cdot i_{C2}$$

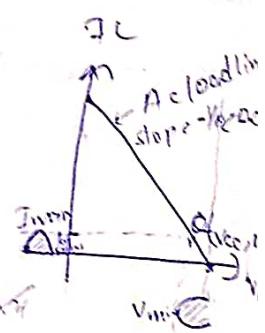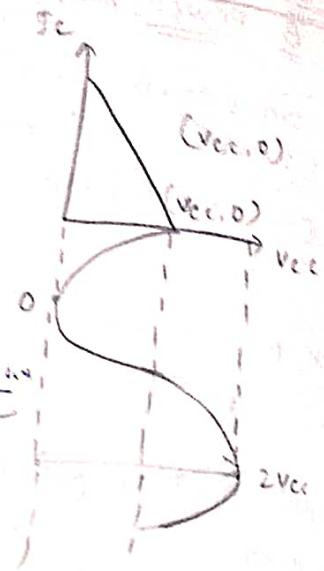

$\rightarrow$  Power dissipation:  
 $\frac{dV_L^2}{dt} = \frac{2}{\pi} \frac{V_{DC}}{R_L} - \frac{2V_{DC}}{2R_L}$

$$I_{max}^2 = \frac{V_{DC}^2}{R_L} \Rightarrow \frac{2}{\pi} \frac{V_{DC}}{R_L} = V_{DC} \Rightarrow V_{DC} = \frac{2}{\pi} I_{max}$$

Thus the minimum possible theoretical efficiency in case of push pull class B power amp is 78.5%, which is much higher than transformer coupled class B.

$$i_L = 2B_1 \cos(\omega t) + 2B_3 \cos(3\omega t) + \dots$$

here even harmonic i.e., 2nd, 4th, ... are eliminated.  
my DC component also get eliminated.

$\therefore$  Total distortion is less and D.C component flowing is zero.

$$\therefore D_3 = \left| \frac{B_3}{B_1} \right| \times \omega ; D_5 = \left| \frac{B_5}{B_1} \right| \times \omega$$

$$\therefore \text{total harmonic distortion } T.D = \sqrt{D_3^2 + D_5^2 + D_7^2 + \dots} \times \omega$$


### Advantages and Disadvantages:

- Transistor efficiency is much higher than class A power amplifier.
- No idc signal, the power dissipation is zero.
- Even harmonic gets cancelled, this reduces the harmonic distortion.
- Due to transformer coupling, impedance matching is possible.

### Disadvantages:

- Two centre tapped transformers are necessary.
- The transformers make the circuit bulky and hence costlier.
- Frequency response is poor.
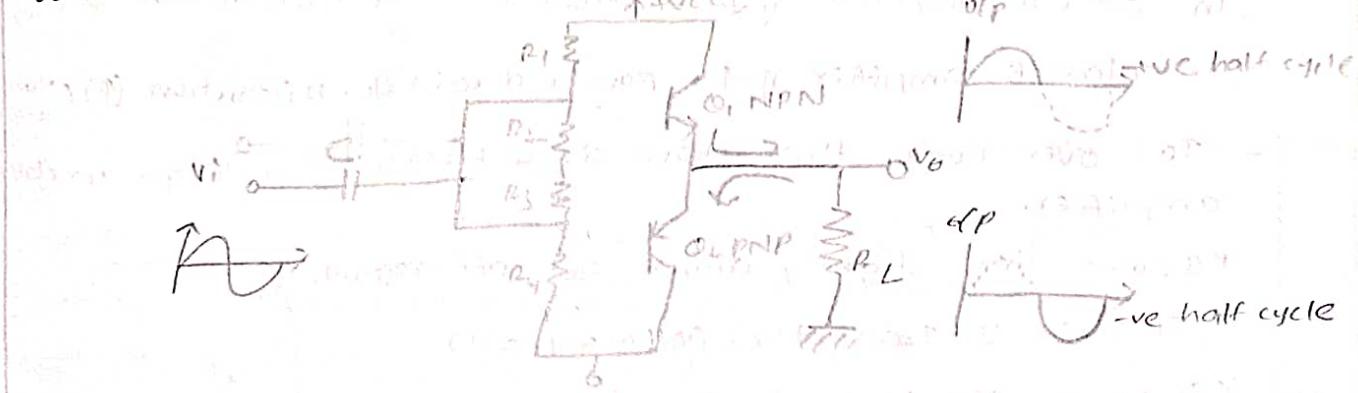
### \*COMPLEMENTARY SYMMETRY - PUSH PULL CLASS B POWER AMPLIFIER



- Q-point is in cut-off region.
- No biasing is used.
- $\eta = 78.57\%$ .
- Two transistors are used.
- One is NPN &
- One is PNP.

(1)  $\text{RC } 1$

$$\begin{aligned} P_{dc} &= V_{cc} \times I_{cm\max} / \pi \\ P_{ac} &= V_{cc} / \sqrt{2} \times I_{cm\max} / \sqrt{2} \\ \eta &= \frac{P_{ac}}{P_{dc}} = \frac{V_{cc} \times I_{cm\max}}{\sqrt{2} \times \sqrt{2}} \times \frac{\pi}{2 \times V_{cc} I_{cm\max}} = 0.785 \end{aligned}$$

$$\therefore \eta = 78.5\%$$

### Advantages:

- ① - AU
- ② - AI
- ③ - FE
- ④ - The circuit is transformer less, its weight, size and cost less.
- Due to common collector configuration impedance match is possible.
- The frequency response improves due to transformer less class B amplifier.

### Disadvantages:

- ⑤ - The circuit needs two separate voltage supplies.
- It is quite difficult to get a pair of transistors (NPN & PNP) that have similar characteristics.
- The harmonics will be unbalance in the two transistors, which results in the increase of distortion.

## ~~CLASS AB AMPLIFIER~~

In class-A Amplifier -  $\eta \downarrow$  - power drain ( $\uparrow$ ) - distortion ( $\downarrow$ ) (linearity region)

In class-B Amplifier -  $\eta \uparrow$  - power drain ( $\downarrow$ ) - distortion ( $\uparrow$ ) (Non-linearity region)

To overcome the above drawbacks, we will go for class AB amplifier.

\* Cut-off point lies slightly above cut off region.

\* It uses 2 Transistors (NPN & PNP)


\* Q point lies b/w class A & class B

\* It conducts in between  $180^\circ \rightarrow 360^\circ$


\* Biasing voltage keeps Transistor slightly above cut off region.



\* Biasing can be given with help

of  $R_1, R_2$  etc,

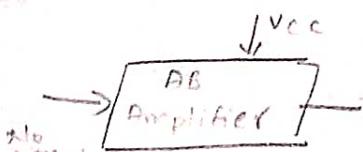

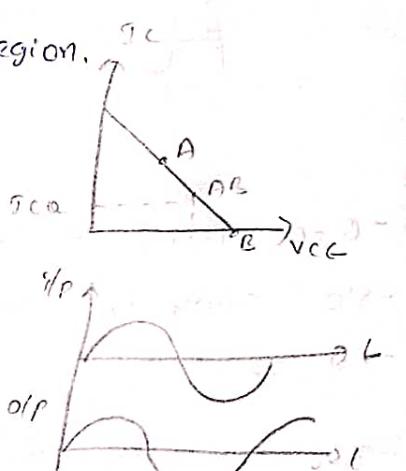with out i/p, due to  $V_{cc}$ , small amount of  $I_c$  flows through the circuit.




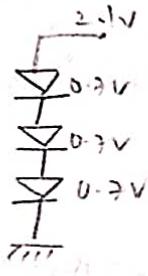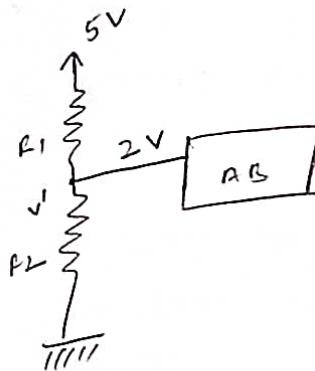

$$V_1 = \frac{R_2}{R_1 + R_2} \cdot 5V$$


- chose  $R_1, R_2$

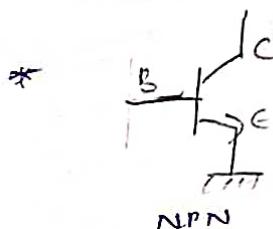- we get 2V at Base of Transistor.
- replace  $R_2$  by diodes to get 2V.



\* - if  $V_B \geq 0.7$   $\rightarrow$  Transistor conducts

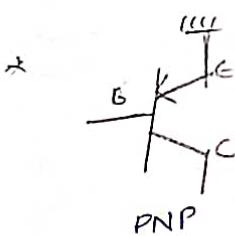
if  $V_B < 0.7$  Transistor does not conduct.



\* if  $V_B \leq -0.7$  Transistor conducts

if  $V_B > -0.7$  Transistor does not conduct.

- class AB uses both transistors.

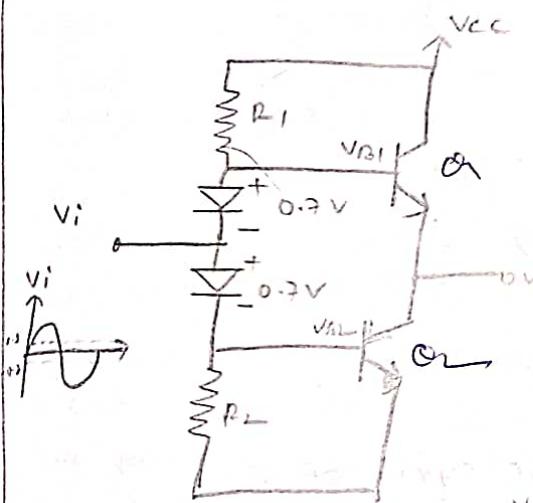

#### case-1:

- No input is applied,  
i.e.,  $V_{in}$  is grounded.

$V_{cc}$  is applied.

$$V_{B1} = 0.7V \quad Q_1 = ON, Q_2 = OFF$$

$$V_{B2} = -0.7V$$

#### case-2:

- along  $V_{cc}$ , during +ve cycle of  $Vi$

$$V_{B1} = 0.7 + Vi \text{ increases}$$

$\Rightarrow I_c$  increases (NPN)

and (PNP)

$$V_{B2} = -0.7 + Vi \text{ decreases}$$

$\Rightarrow Q_2$  does not conduct

$\therefore I_{c2} = 0$  (no current)

#### case-3:

along  $V_{cc}$ , During -ve cycle of  $Vi$

$V_{B1}$

$$+ 0.7V \quad V_{B1} = 0.7 - Vi \quad (\downarrow)$$

$I_{c1} = 0$  (no current)

$V_{B2}$

$$- 0.7V \quad V_{B2} = -0.7 - Vi \quad (\downarrow)$$

$\Rightarrow Q_2$  conducts

$\therefore I_{c2}$  increases

#### case-4:

if  $-0.7 < Vi < 0$  (during -ve cycle)

Ex:  $Vi = -0.5V$

$$V_{B1} = 0.7V - 0.5V = 0.2V, Q_1: OFF$$

$$V_{B2} = -0.7 - 0.5 = -1.2V, Q_2: ON$$

①

RC

### case - 5:

if  $0 < v_{in} < 0.7$

Ex:  $v_{in} = 0.5 \text{ V}$

$$V_B1 = 0.7 + 0.5 = 1.2 \text{ V} \Rightarrow Q_1 = \text{ON}$$

$$V_B2 = 0.7 - 0.5 = -0.2 \Rightarrow Q_2 = \text{OFF}$$

In class AB we will not come across dead zone.  
∴ cross over distortion is eliminated.

②-AU



③-AI

④-FC

⑤-

→ conduction angle

$$> 180^\circ \text{ & } < 360^\circ$$

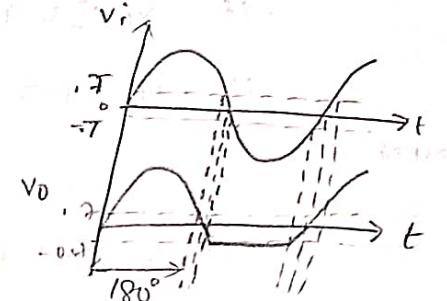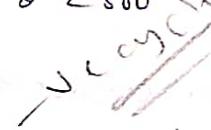


: phase is  $180 + \phi$


⑥-1.
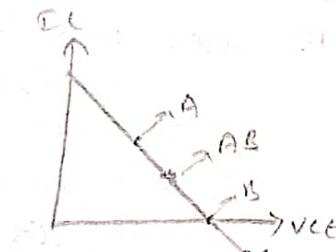
### class C Amplifier:

- It is deeply biased.
- Q<sub>point</sub> is below cutoff region.
- conduction angle is less than  $180^\circ$
- very high efficiency ( $\approx 90\%$ )
- high distortion, is due to non-linearity



### Circuit:

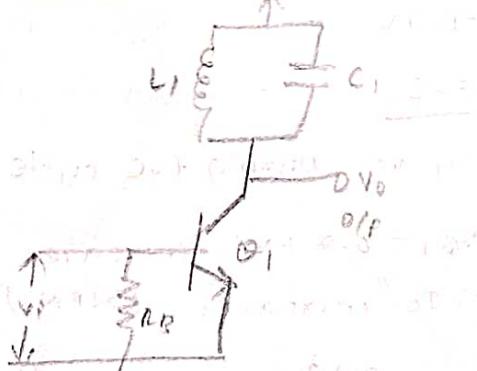


### case-i:

during +ve cycle of v\_i:

if  $v_i < 0.7 \text{ V}$   $v_B = v_i$ , Q<sub>1</sub> does not conduct

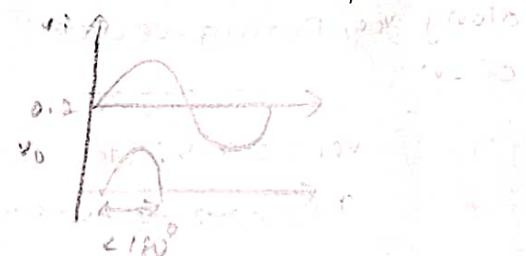$v_i \geq 0.7 \text{ V}$   $v_B = v_i \Rightarrow Q_1 \text{ conducts}$



### case-ii:

During -ve half cycle

$$V_B = -V_C$$

$\therefore Q_1 = \text{OFF}$

O/p = zero

### Advantages:

$$\eta = 90\% \text{ & } \text{less distortion}$$

- It can be used in RF application, high power O/p with small size.

### Disadvantages:

- Non linearity
- Audio frequency can't be generated
- Distortion is more

### Applications:

- RF Amplifier

- RF Oscillator

- Tuned amplifier


### Working: As shown in figure :-

- Resistor  $R_b$  connects to transistor Q1 base. This resistor try to pull the base of transistor further downwards and set the operating point dc bias point below cut-off point in dc load line.
- Here, the transistor will start conducting only after the input signal amplitude has risen above the base emitter voltage (0.7V).
- LC circuits are used either for generating signals at a particular frequency (or) picking out a signal at a particular frequency.
- A series of current pulses is produced by the transistor according to i/p.
- The tank circuit oscillates in the frequency of i/p signal by selecting proper value of L & C.
- For transferring the power to the load from the tank circuit, a coupling transformer is used.
- The operating point is placed some way below the cutoff point in the DC loadline and so only a fraction of the i/p waveform is available at o/p.

⑤ EC
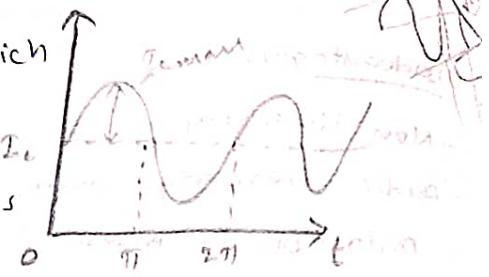
## class-A power Amplifier:

A class A amplifier is one in which the operating point and the input signal are such that the current in the o/p circuit flows at full times.



collector current waveform  
for Transistor operating in  
class A

① AU



② AI

③ FE

④ -

⑤ -

## class-B Amplifier:

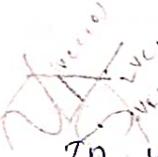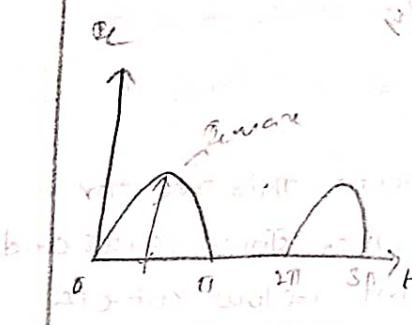


In which the operating point is at extreme end of Pts characteristic. It provides an o/p signal varying over one-half of the input signal cycle

(or for 180° of input signal, it has 50% of maximum power dissipation)
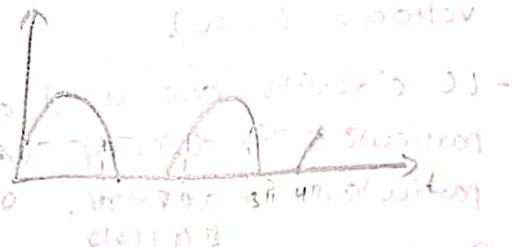
## class AB Amplifier:


Operating point is in biw

class A and class B. The o/p signal swing occurs b/w 180° and 360°


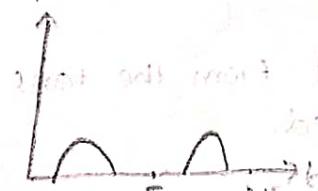
## class C Amplifier:

operating point is chosen so that o/p (below the cut off) so that o/p current is zero for more than one-half of o/p signal.



## summary of power Amplifier


	class A	class B	class AB	class C
power drain	YES	NO	NO	NO
Q point	Middle	cutoff	slightly above cutoff	deeper inside cutoff
conduction angle	0-360°	180°	180°-360°	<180°
efficiency	50%	78.5%	DA & LB	90%
Distortion	NO	CROSS OVER distortion	NO COD	High

## 5. OPERATIONAL AMPLIFIER

→ Operational Amplifier : +, -,  $\times$ ,  $\div$ , Log, AntiLog,  $\sqrt{ }$

→ 741 IC (Linear Integrated Circuit)

### Block Diagram:

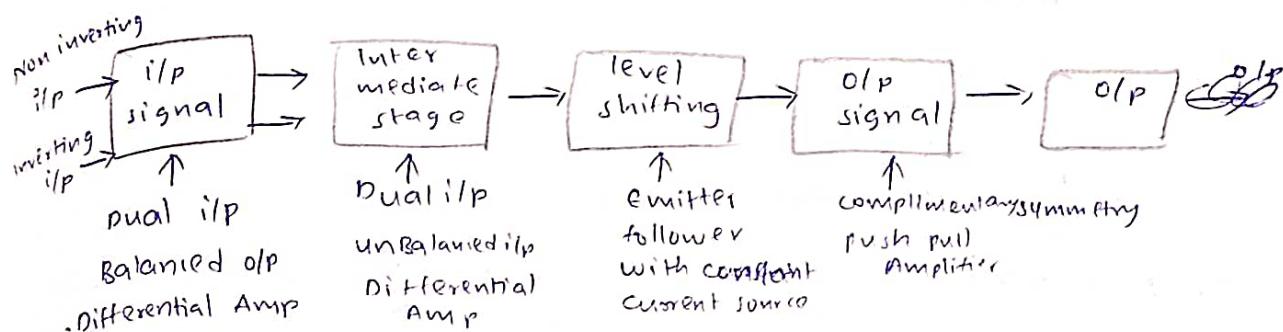

### Differential Amplifiers:

- Properties of both transistors must be same.

$$\text{i.e., } Q_1 = Q_2 \\ B_1 = B_2$$

$$B \text{-large} \Rightarrow I_B \downarrow \downarrow I_C \approx \text{const}$$

$$V_{BG} = V_{BQ_2} = V_{BE}$$

$$I_C = B I_B$$

on basis of i/p and o/p,


it has 4 mode of configurations.

① Dual i/p

Balanced o/p

② Dual i/p

unbalanced o/p

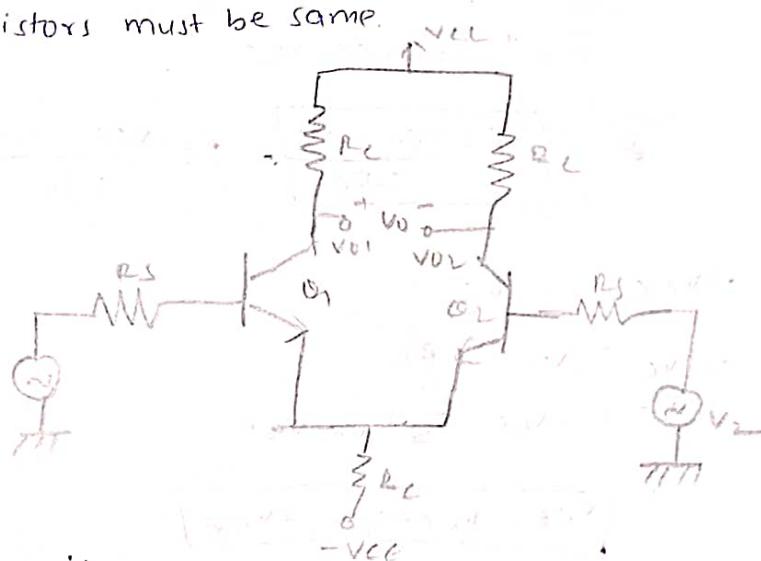

③ Single i/p

Balanced o/p

④ Single i/p


unbalanced o/p

### AC & DC analysis of differential amplifier:

→ AC analysis  $\Rightarrow A_V, R_i \& R_o$

→ DC analysis  $\Rightarrow Q$  point
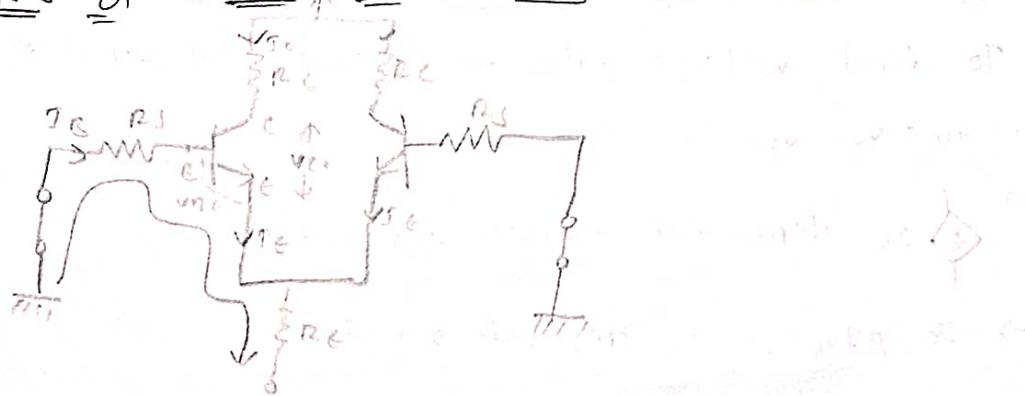
### \* DC analysis of differential amplifier:



ICL,

$$I_B R_S + V_{BE} + 2 I_E R_E - V_{CE} = 0$$

$\beta$  is very high

$$\Rightarrow I_C \approx I_E$$

$$\beta I_B \approx I_E$$

$$I_B \approx \frac{I_E}{\beta}$$

① AV

② A

③ FC

$$\therefore \frac{I_E}{\beta} R_S + V_{BE} + 2 I_E R_E - V_{CE} = 0$$

AS  $\beta$  is very high,  $\frac{I_E}{\beta}$  is very small  $\Rightarrow \frac{I_E}{\beta} R_S$  may be negligible

④

$$V_{BE} + 2 I_E R_E - V_{CE} = 0$$

$$2 I_E R_E = V_{CE} - V_{BE}$$

⑤

$$\boxed{I_E = \frac{V_{CE} - V_{BE}}{2 R_E}} \Rightarrow I_C = \frac{V_{CE} - V_{BE}}{2 R_E}$$


$$\Rightarrow V_{CE} = V_C - V_E$$

and  $V_C = V_{CC} - I_C R_C$

$$V_E = -V_{BE} - I_B R_S = -V_{BE}$$

$$\therefore \boxed{V_{CE} = V_{CC} - I_C R_C + V_{BE}}$$

As Q-point =  $f(V_{CE}, I_C)$

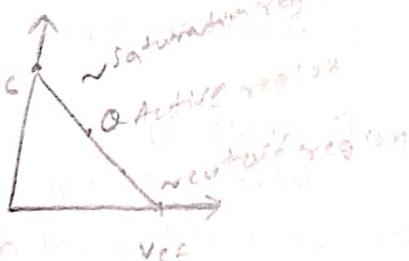



## AC ANALYSIS OF DIFFERENTIAL AMPLIFIER!

To find voltage gain, Input resistance & Output resistance.

$$\rightarrow V_O = V_{O2} - V_{O1}$$

$\rightarrow$    $I_C$  = dependent current generator
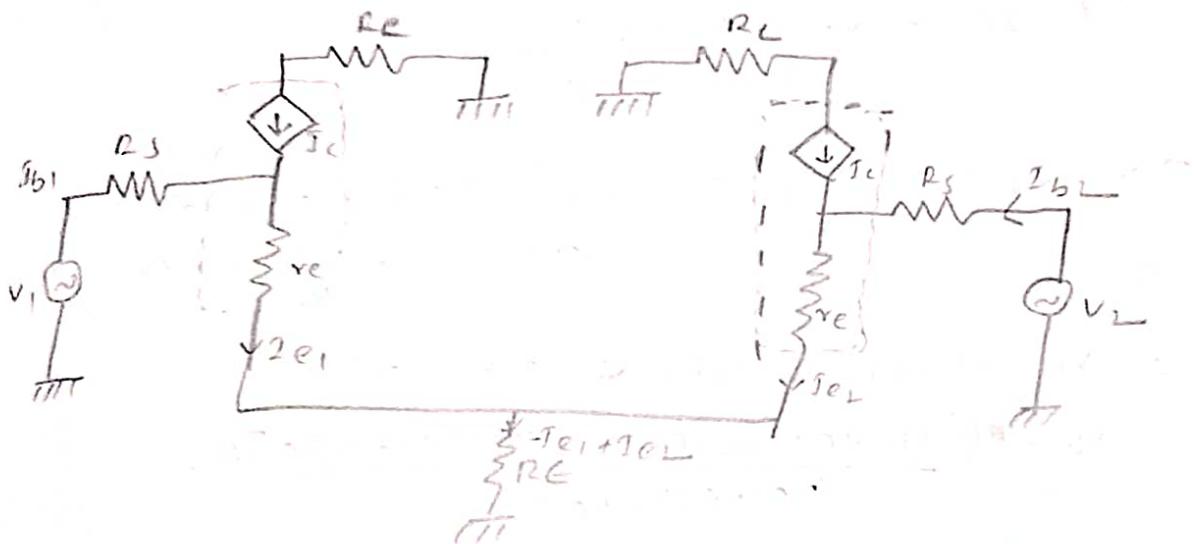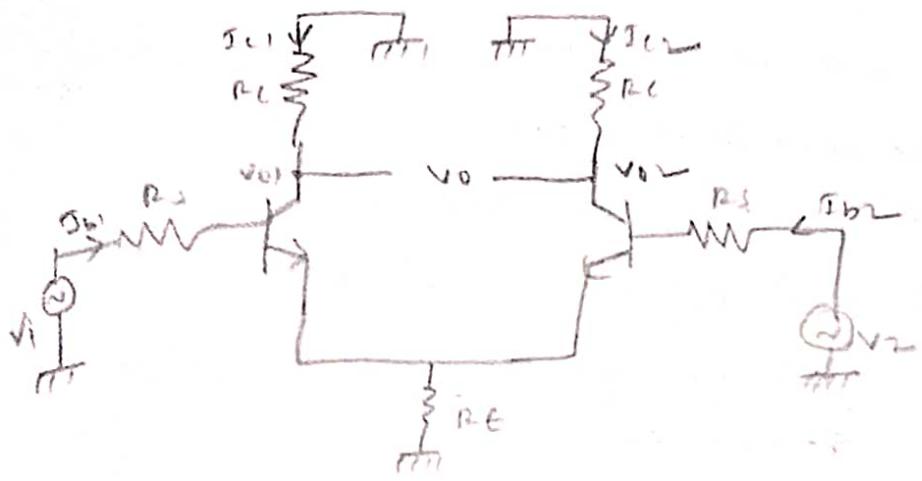
$$\rightarrow I_C = \beta I_B \quad \because I_C \text{ depends on } I_B$$



$$r_e = \frac{V_T}{I_E} \quad (I_E = \text{DC Emitter Current})$$

$$I_C = \beta I_B$$

$$V_1 = I_{B1} R_S + I_{E1} r_e + R_E (I_{C1} + I_{E2})$$

$$V_1 = \frac{I_{E1}}{\beta} R_S + I_{E1} (r_e + R_E) + I_{E2} R_E$$

neglect - i

$$V_1 = (r_e + R_E) I_{E1} + I_{E2} R_E \quad \boxed{1}$$

$$V_2 = I_{B2} R_S + I_{E2} r_e + (I_{E1} + I_{E2}) R_E$$

$$= \frac{I_{E1}}{\beta} R_S + I_C r_e + (I_{E1} + I_{E2}) R_E$$

$$V_2 = I_{E2} (r_e + R_E) + R_E I_{E1} \quad \boxed{2}$$

Solving eqs 1 & 2 we can get  $I_{E1}$  &  $I_{E2}$

$$R_E I_{E1} + (r_e + R_E) I_{E2} = V_2 \quad \boxed{3}$$

$$(r_e + R_E) I_{E1} + R_E I_{E2} = V_1 \quad \boxed{4}$$

**Submitting can be done online by clicking here.**

Can anything be seen above by RE

$$E \in \{e_2 - e_3\} \otimes e_1 + (e_2 + e_3)^2 \otimes e_2 = e_2(e_2 + 2e_3)$$

AS (WERS) TET- TET-TET = 875

$$\frac{d}{dt} \mathbb{E} e^{\lambda t} (\tilde{X}_t - \mu \epsilon)^2 = \mathbb{E} e^{2\lambda t} \leq M_2 (\lambda) (\tilde{X}_t - \mu \epsilon)^2 + V(\mu \epsilon)$$

$$E_2 = \frac{V_{2\pi} - V_{2\pi}^0}{(E_2 - E_2^0)^2 + E_2^0} \quad (5)$$

$$E_1 = \frac{w_1(\alpha + \beta) - w_2\beta}{(\alpha + \beta)^2 - \beta^2} - 6$$

$\Rightarrow$   $V_{\text{max}} = V_0$ , where  $V_0 = T_{\text{ext}}^2 - T_{\text{int}}^2$ .

$$V_{01} = -I_{01} R_E = -I_{C1} R_C$$

$$\therefore \text{Vol} = -I_{C2}R_C + I_{R1}R_C = R_C(I_{R1} - I_{C2})$$

$$v_0 = \frac{v_1(2\alpha + \beta) - v_2\beta}{(\alpha\alpha + \beta)^2 - \beta\alpha^2}$$

$$= \frac{v_1(\gamma_E + R_E - F_E) - v_2(\gamma_E + L_E)}{(\gamma_E + R_E + F_E)(\gamma_E + R_E - F_E)}$$

$$= \frac{(\bar{v}_1 - v_2)(\text{reg}(n))}{(\cancel{\text{reg}(n)})(v_2)}$$

$$v_0 = \underline{(c_1 - v_1) \rho_0}$$

$$= \frac{V_0}{V_0 - V_2} = \frac{R_L}{Z_0}$$

Differential voltage gain:  $\frac{V_o}{V_s}$

Voltage gain of dual op balanced op differential amplifier is


$$E_{\text{kin}} = \frac{m_0}{v_0 - v_m}$$

→ Input resistance and O/p resistance:

$$\text{Input resistance} = \frac{V_i}{I_{b_1}} \quad | \quad V_2 = 0$$


$$I_{ER} = \frac{V_1(T_{ER} + \Delta E) - V_2 \Delta E}{(V_{ER} + \Delta E)^2 - \frac{1}{4}}$$
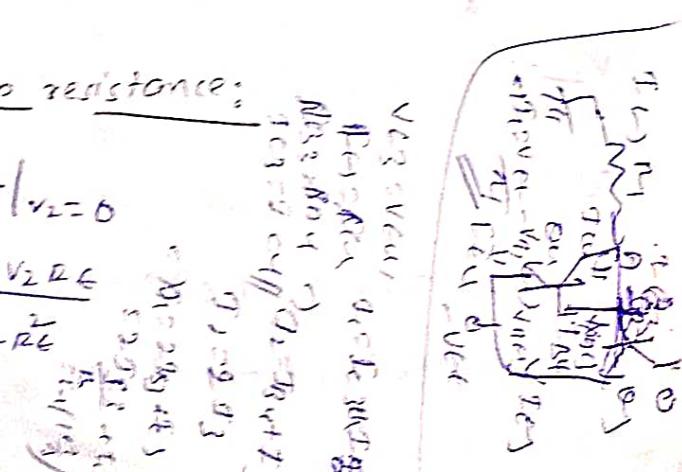
$$I_{C_1} = \frac{V_1(x_C + \Delta x)}{(x_C + \Delta x)^2 - a^2}$$



Q) AC power gain  $\rightarrow I_E = (\beta B) I_B$   
 \* operation in power region  
 \* increasing  $I_B$  increases  
 $\rightarrow \Delta$   $(\Delta I_B = B I_B)$

$\beta P > 1$

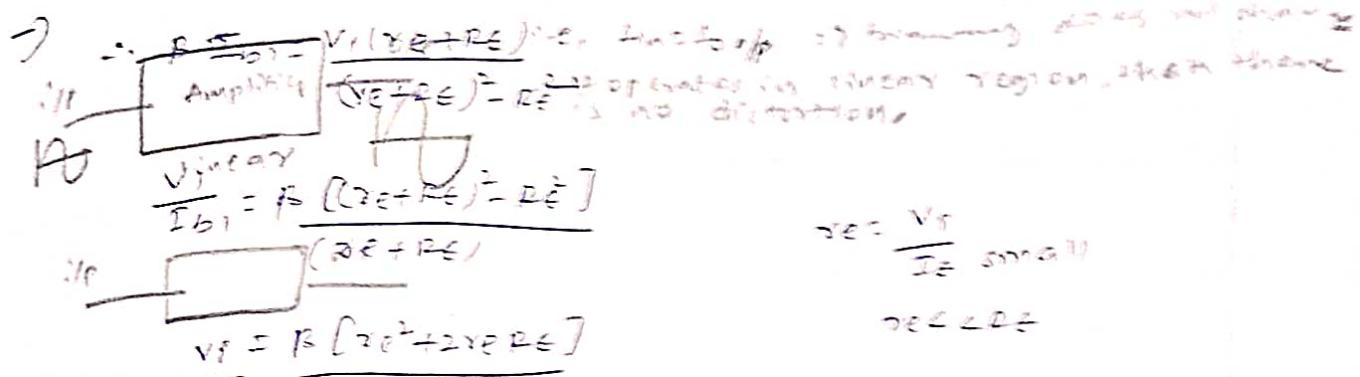

$$R_E = \frac{V_f}{I_E} \text{ small}$$

$\Delta I_E \ll I_E$

$\rightarrow$  high power  $\rightarrow$  class AB Amplifier


$\rightarrow$  complementary  $\frac{V_o}{I_E} = \frac{V_o}{R_E}$  full-pull class B power amplifiers

$\rightarrow$  class AB power Amplifier,

$$\text{use } R_E = 2R_{BE} \text{ for PNP transistors.}$$





similarly,  $R_{E2} = 2R_{BE}$

and o/p resistance,  $R_O = R_{Cff}$

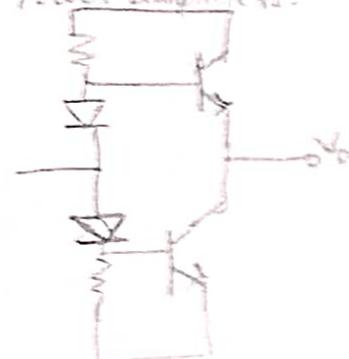

## Operational Amplifiers:

Block diagram:

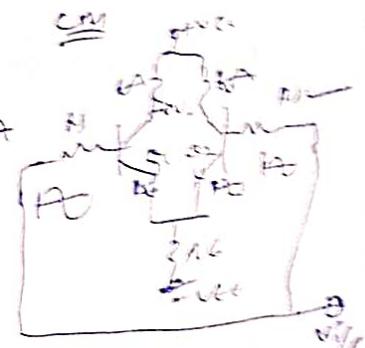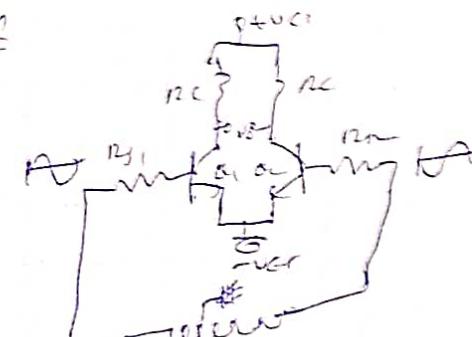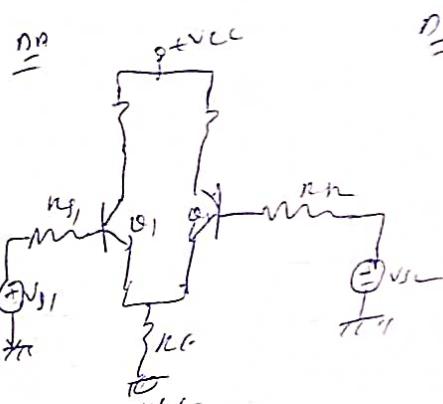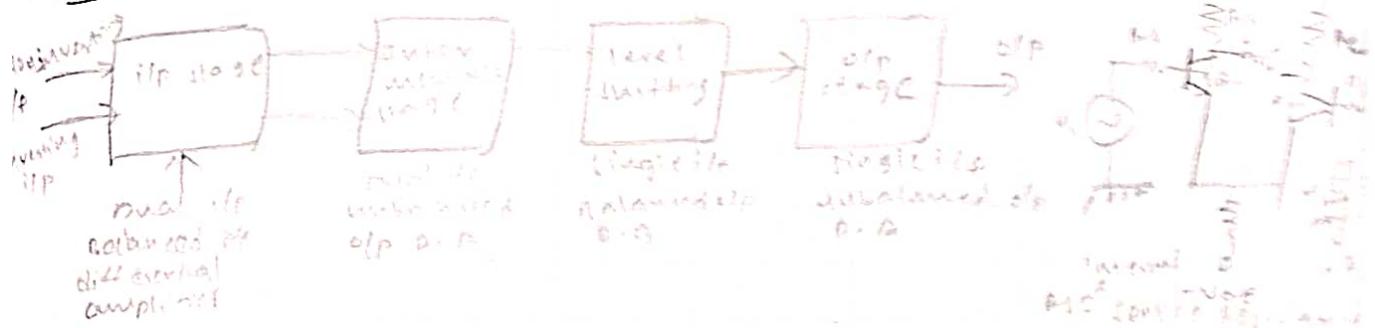

$$\begin{aligned} V_{BE} &= V_{B3} - V_{B2} + V_{ER} \\ &= V_{BE} - \frac{V_{BE}}{R_3 + R_2} + V_{ER} \end{aligned}$$

$$\begin{aligned} V_{BE} &= V_{B3} - V_{B2} + V_{ER} \\ &= V_{BE} - \frac{V_{BE}}{R_3 + R_2} + V_{ER} \end{aligned}$$

- ① aAI & fAI
- ② is harder D.T
- ③ AI learning  $\rightarrow$  repeated guesses
- ④ Dinner  $\rightarrow$  ⑤ evaluate / set weight  
choose which should be done
- ⑥ Open temperature  $\rightarrow$  logistic regression.
- ⑦ Advantage of ML  $\rightarrow$  modern laptop / small data  $\rightarrow$  ⑧
- ⑨ Rainfall  $\rightarrow$  classifies ON/N
- ⑩ Future of AI  $\rightarrow$  CS/Automation  $\rightarrow$  ⑪
- ⑫ ML is subset  $\rightarrow$  AI
- ⑬ fires  $\rightarrow$  sigmoid function
- ⑭ perceptron layer - nodes
- ⑮ game - unimpaired / unpermitted condition  $\rightarrow$  ⑯
- ⑯ region  $\rightarrow$  AF/HF
- ⑰ minimum of EC  $\rightarrow$
- ⑱ image recognition